

## Lecture – 11



Date: 15.09.2016

- MOS Differential Pair
- Quantitative Analysis – differential input
- Small Signal Analysis
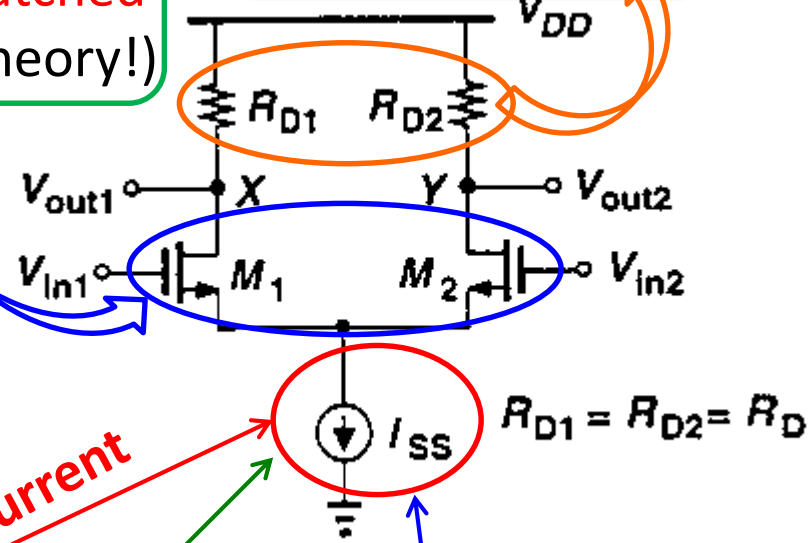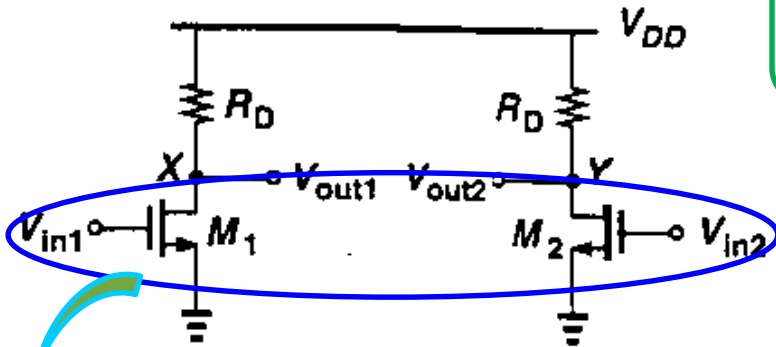
## MOS Differential Pair

$M_1$  and  $M_2$  are perfectly matched (at least in theory!)

ensures  $M_1$  and  $M_2$  in saturation



Variation of input CM level regulates the bias currents of  $M_1$  and  $M_2$  → Undesired!!!

Solution??

Need?


Current source is ideal: constant current, infinite output impedance

To overcome the issues emanating from non-ideal CM level

## MOS Differential Pair
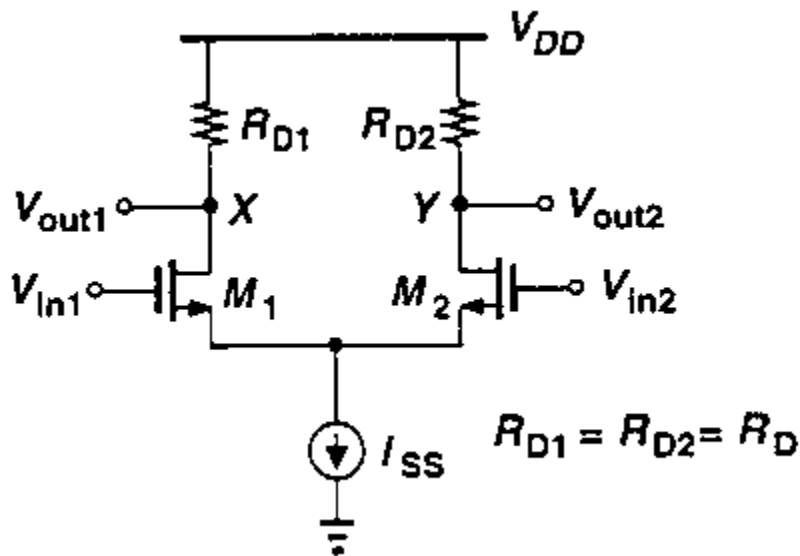
### Qualitative Analysis – differential input

- Let us check the effect of  $V_{in1} - V_{in2}$  variation from  $-\infty$  to  $\infty$




- $V_{in1}$  is much more **-ve** than  $V_{in2}$  then:
    - $M_1$  is OFF and  $M_2$  is ON
    - $I_{D2} = I_{SS}$
    - $V_{out1} = V_{DD}$  and  $V_{out2} = V_{DD} - I_{SS}R_D$
  - $V_{in1}$  is brought closer to  $V_{in2}$  then:
    - $M_1$  gradually turns ON and  $M_2$  is ON
      - Draws a fraction of  $I_{SS}$  and lowers  $V_{out1}$
    - $I_{D2}$  decreases and  $V_{out2}$  rises
  - $V_{in1} = V_{in2}$ 
    - $V_{out1} = V_{out2} = V_{DD} - I_{SS}R_D/2$

## MOS Differential Pair
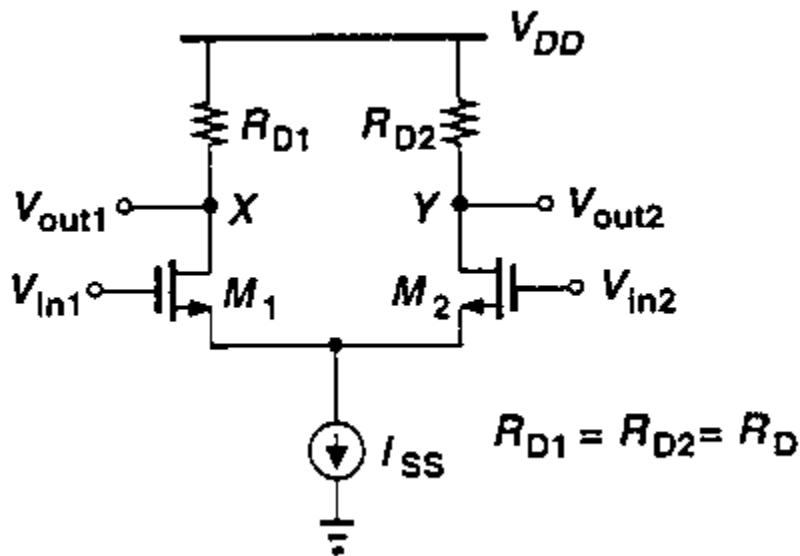
### Qualitative Analysis – differential input

- Let us check the effect of  $V_{in1} - V_{in2}$  variation from  $-\infty$  to  $\infty$



- $V_{in1}$  becomes more +ve than  $V_{in2}$  then:
  - $M_1$  is ON and  $M_2$  is OFF
  - $M_1$  carries greater  $I_{SS}$  than  $M_2$
- For sufficiently large  $V_{in1} - V_{in2}$ :
  - All of the  $I_{SS}$  goes through  $M_1 \rightarrow M_2$  is OFF
  - $V_{out1} = V_{DD} - I_{SS}R_D$  and  $V_{out2} = V_{DD}$



## MOS Differential Pair

### Qualitative Analysis – differential input

- Plotting  $V_{out1} - V_{out2}$  versus  $V_{in1} - V_{in2}$

Minimum Slope  $\leftrightarrow$  Minimum Gain

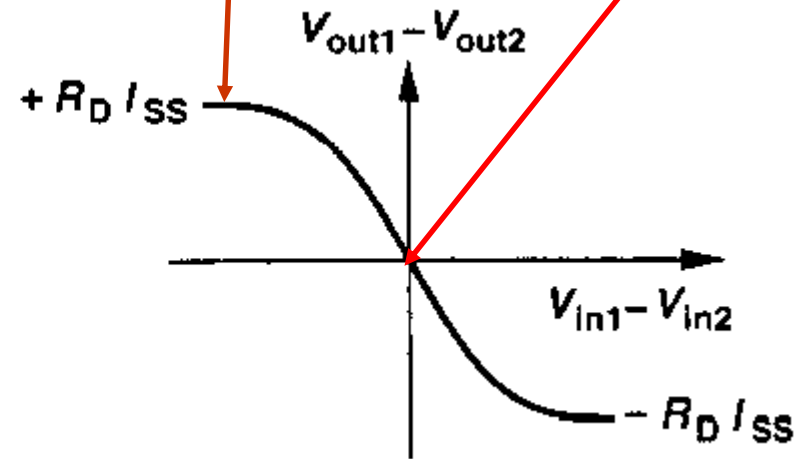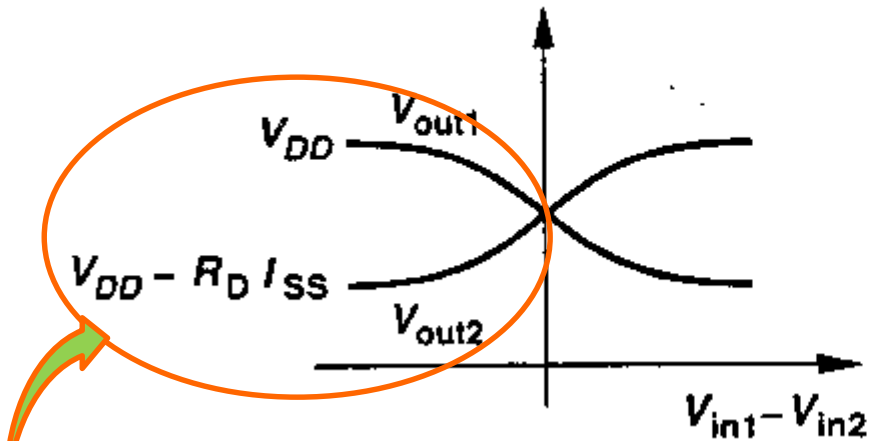Maximum Slope  $\leftrightarrow$  Maximum Gain



The maximum and minimum levels at the output are well defined and is independent of input CM level ( $V_{in,cm}$ )

The circuit becomes more nonlinear as the input voltage swing increases (i.e.,  $V_{in1} - V_{in2}$  increases)  $\leftrightarrow$  at  $V_{in1} = V_{in2}$ , the circuit is said to be in equilibrium

## MOS Differential Pair


### Qualitative Analysis – common mode input

- Now let us consider the common mode behavior of the circuit

As mentioned, the tail current source is used to suppress the effect of input CM level variation ( $V_{in,cm}$ )



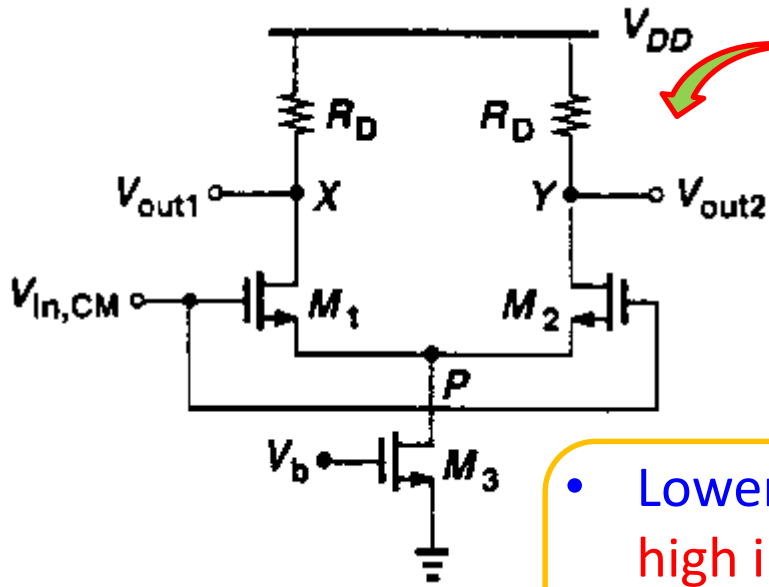Does this enable us to set any arbitrary level of input CM ( $V_{in,cm}$ )



### To understand this:


- Set  $V_{in1} = V_{in2} = V_{in,CM}$
- Then vary  $V_{in,CM}$  from 0 to  $V_{DD}$
- Also implement  $I_{SS}$  with an NFET

- Lower bound of  $V_{in,cm}$ :  $V_p$  should be sufficiently high in order for  $M_3$  to act as a current source.
- Upper bound of  $V_{in, cm}$ :  $M_1$  and  $M_2$  need to remain in saturation.

## MOS Differential Pair
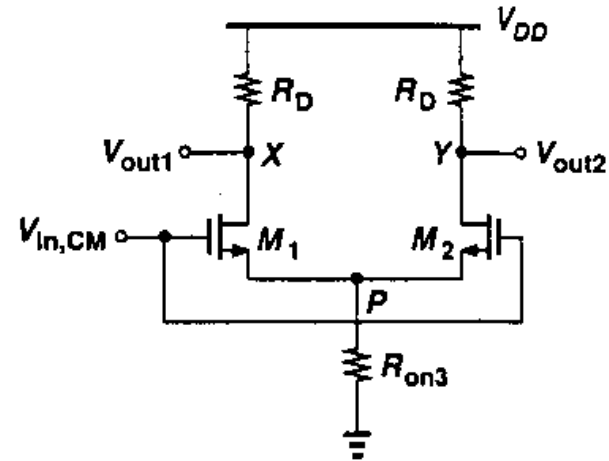
### Qualitative Analysis – common mode input

- What happens when  $V_{in,CM} = 0$ ?
  - $M_1$  and  $M_2$  will be OFF and  $M_3$  can be in triode for high enough  $V_b$
  - $I_{D1} = I_{D2} = 0$  ← circuit is incapable of amplification
- Now suppose  $V_{in,CM}$  becomes more +ve
  - $M_1$  and  $M_2$  will turn ON if  $V_{in,CM}$  exceeds  $V_T$
  - $I_{D1}$  and  $I_{D2}$  will continue to rise with the increase in  $V_{in,CM}$
  - $V_P$  will track  $V_{in,CM}$  as  $M_1$  and  $M_2$  work like a source follower
  - For high enough  $V_{in,CM}$ ,  $M_3$  will be in saturation as well
- If  $V_{in,CM}$  rises further
  - $M_1$  and  $M_2$  will remain in saturation if:



$$V_{in,CM} - V_T \leq V_{out1} \longrightarrow V_{in,CM} \leq V_{DD} - \frac{I_{SS}}{2} R_D + V_T$$

## MOS Differential Pair

### Qualitative Analysis – common mode input

- For  $M_1$  and  $M_2$  to remain in saturation:

$$V_{GS1,2} - V_T \leq V_{DS1,2} \quad \Rightarrow \quad V_{in,CM} - V_T \leq V_{DD} - \frac{I_{SS}}{2} R_D \quad \Rightarrow \quad V_{in,CM} \leq V_T + V_{DD} - \frac{I_{SS}}{2} R_D$$

$$\therefore (V_{in,CM})_{\max} = V_T + V_{DD} - \frac{I_{SS}}{2} R_D$$

- The lowest value of  $V_{in,CM}$  is determined by the need to keep the constant current source operational:

$$V_{in,CM} - V_{GS1,2} \geq V_{GS3} - V_T$$

$$\Rightarrow V_{in,CM} \geq V_{GS1,2} + (V_{GS3} - V_T)$$

$$V_{GS1,2} + (V_{GS3} - V_T) \leq V_{in,CM} \leq \min \left[ V_{DD} - \frac{I_{SS}}{2} R_D + V_T, V_{DD} \right]$$




## MOS Differential Pair

### Qualitative Analysis – common mode input

- Thus,  $V_{in,CM}$  is bounded as:

$$V_{GS1,2} + (V_{GS3} - V_T) \leq V_{in,CM} \leq \min \left[ V_{DD} - \frac{I_{SS}}{2} R_D + V_T, V_{DD} \right]$$


- Summary:

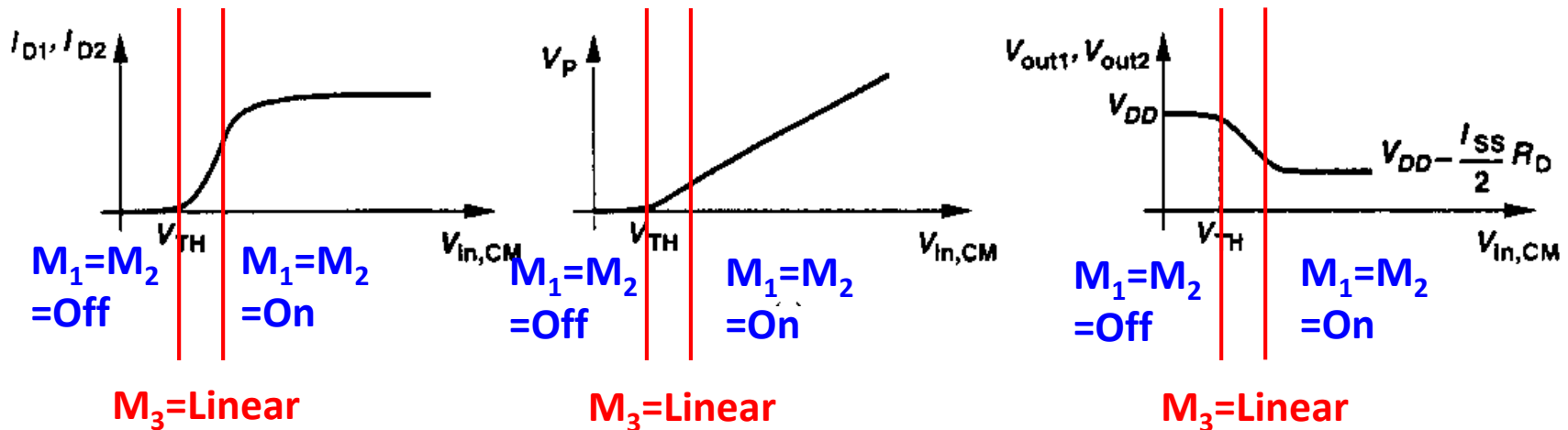

## MOS Differential Pair
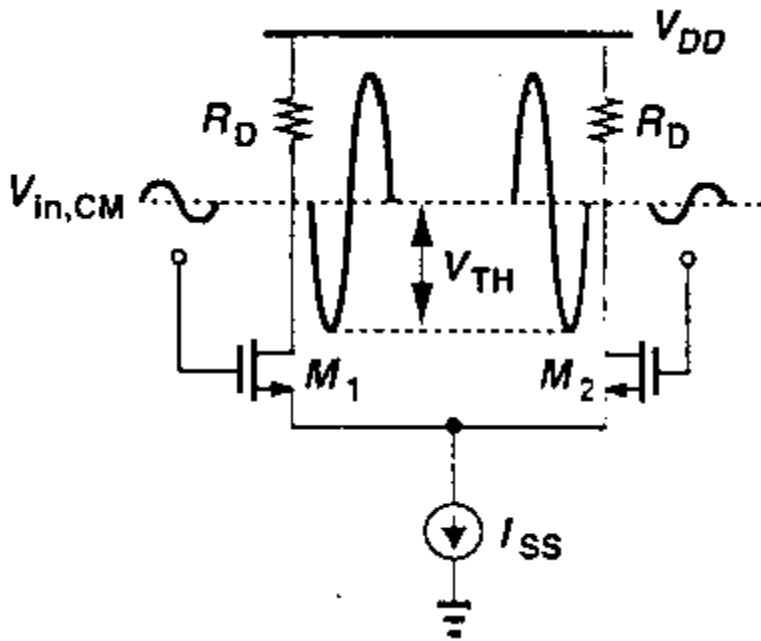
### Qualitative Analysis – common mode input

- How large can the output voltage swings of a differential pair be?




$$V_{out,max} = V_{DD}$$

$$V_{out,min} = V_{in,CM} - V_T$$

The higher the input CM level, the smaller the allowable output swings.

## MOS Differential Pair
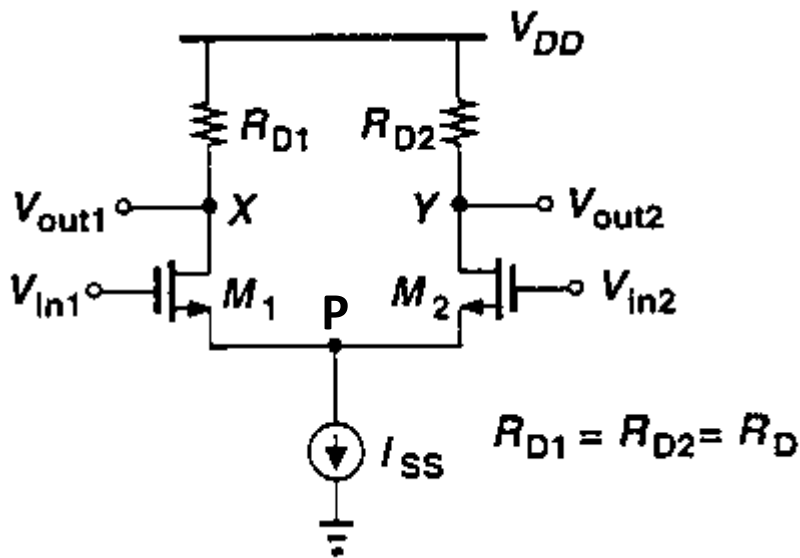
### Quantitative Analysis – differential input



For +ve  $V_{in1} \rightarrow V_{GS1}$  is greater than  $V_{GS2} \rightarrow$   
 $I_{D1}$  will be greater than  $I_{D2}$



$$V_{out2} (= V_{DD} - I_{D2}R_D) > V_{out1} (= V_{DD} - I_{D1}R_D)$$

For +ve  $V_{in2} \rightarrow V_{GS2}$  is greater than  $V_{GS1} \rightarrow$   
 $I_{D2}$  will be greater than  $I_{D1}$




$$V_{out1} (= V_{DD} - I_{D1}R_D) > V_{out2} (= V_{DD} - I_{D2}R_D)$$

It is thus apparent that the differential pair respond to differential-mode signals  $\rightarrow$  by providing differential output signal between the two drains

## Differential Pair – Large Signal Analysis

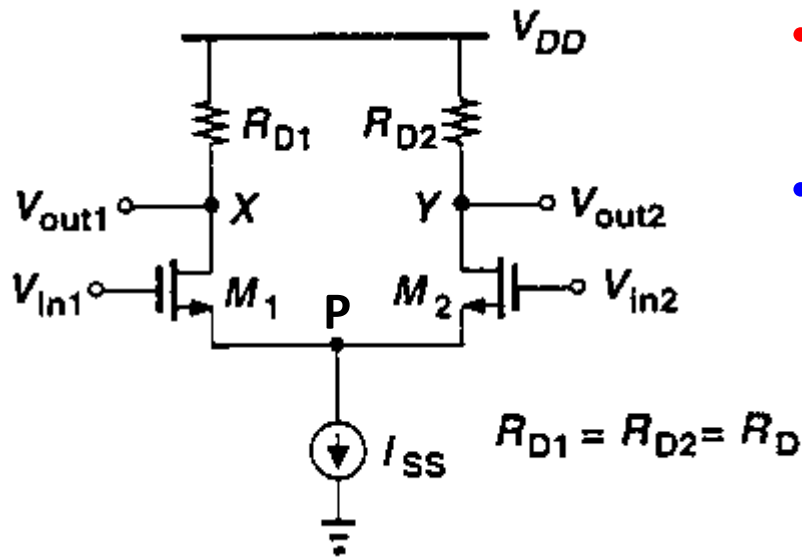
### Quantitative Analysis – differential input



- The idea is to define  $I_{D1}$  and  $I_{D2}$  in terms of input differential signal  $V_{in1} - V_{in2}$
- The circuit doesn't include connection details considering that these drain current equations do not depend on the external circuitries
- Assumptions:  $M_1$  and  $M_2$  are always in saturation; differential pair is perfectly matched; channel length modulation is not present

## Differential Pair – Large Signal Analysis
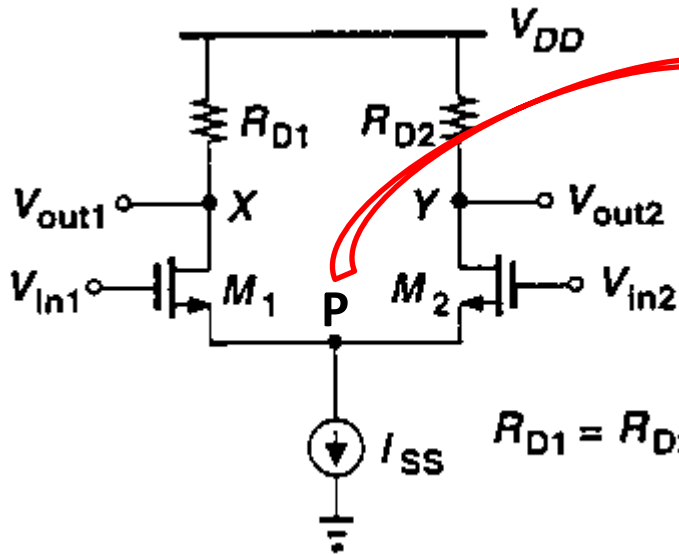
### Quantitative Analysis – differential input



$$V_P = V_{in1} - V_{GS1} = V_{in2} - V_{GS2}$$

$$\therefore V_{in1} - V_{in2} = V_{GS1} - V_{GS2}$$

We also know:

$$R_{D1} = R_{D2} = R_D \quad (V_{GS} - V_T)^2 = \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}} \quad \Rightarrow V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_T$$

Therefore:

$$V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

Squaring

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{D1} + I_{D2} - 2\sqrt{I_{D1}I_{D2}})$$

## Differential Pair – Large Signal Analysis

### Quantitative Analysis – differential input

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} \left( I_{D1} + I_{D2} - 2\sqrt{I_{D1}I_{D2}} \right)$$

$= I_{SS}$

$$\therefore (V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} \left( I_{SS} - 2\sqrt{I_{D1}I_{D2}} \right)$$

Squaring

$$\frac{1}{2} \left( \mu_n C_{ox} \frac{W}{L} \right) (V_{in1} - V_{in2})^2 - I_{SS} = -2\sqrt{I_{D1}I_{D2}}$$


$$\frac{1}{4} \left( \mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS}^2 - I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 = 4I_{D1}I_{D2}$$

$$\frac{1}{4} \left( \mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS}^2 - I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2$$

## Differential Pair – Large Signal Analysis
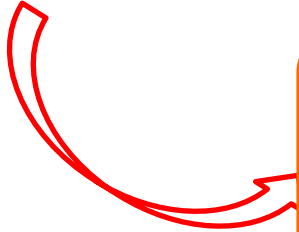
### Quantitative Analysis – differential input

$$(I_{D1} - I_{D2})^2 = -\frac{1}{4} \left( \mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2$$



$$I_{D1} - I_{D2} = \frac{1}{2} \left( \mu_n C_{ox} \frac{W}{L} \right) (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

### Observations

- $I_{D1} - I_{D2}$  falls to zero for  $V_{in1} = V_{in2}$  and  $|I_{D1} - I_{D2}|$  increases with increase in  $|V_{in1} - V_{in2}|$
- Therefore,  $I_{D1} - I_{D2}$  is an odd function of  $V_{in1} - V_{in2}$
- Its important to notice that  $I_{D1}$  and  $I_{D2}$  are even functions of their respective gate-source voltage

## Differential Pair – Large Signal Analysis

### Quantitative Analysis – differential input

- Equivalent  $G_m$  of  $M_1$  and  $M_2 \rightarrow$  its effectively the slope of the characteristics

Lets denote:  $I_{D1} - I_{D2} = \Delta I_D$

$$V_{in1} - V_{in2} = \Delta V_{in}$$

$$\Delta I_D = \frac{1}{2} \left( \mu_n C_{ox} \frac{W}{L} \right) \Delta V_{in} \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - \Delta V_{in}^2}$$

$$\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \frac{1}{2} \left( \mu_n C_{ox} \frac{W}{L} \right) \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - \Delta V_{in}^2}}$$

**For  $\Delta V_{in} = 0$ :**  $G_m = \frac{\partial \Delta I_D}{\partial \Delta V_{in}} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$

**Furthermore:**  $V_{out1} - V_{out2} = R_D \Delta I = R_D G_m \Delta V_{in}$

$$\therefore |A_v| = \frac{V_{out1} - V_{out2}}{\Delta V_{in}} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS} R_D}$$



## Differential Pair – Large Signal Analysis



### Quantitative Analysis – differential input

$$G_m = \frac{1}{2} \left( \mu_n C_{ox} \frac{W}{L} \right) \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2\Delta V_{in}^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - \Delta V_{in}^2}}$$

$G_m$  falls to zero for

$$\Delta V_{in} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

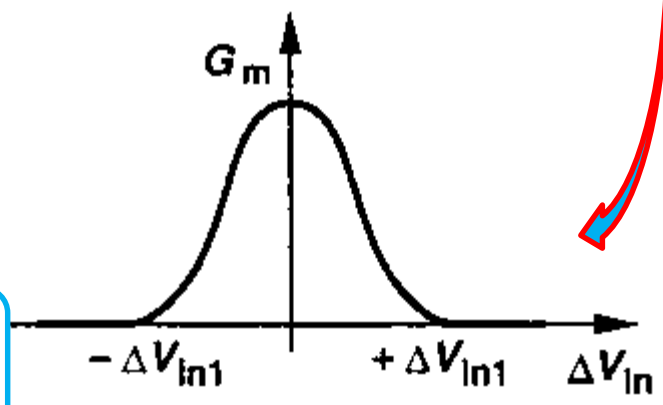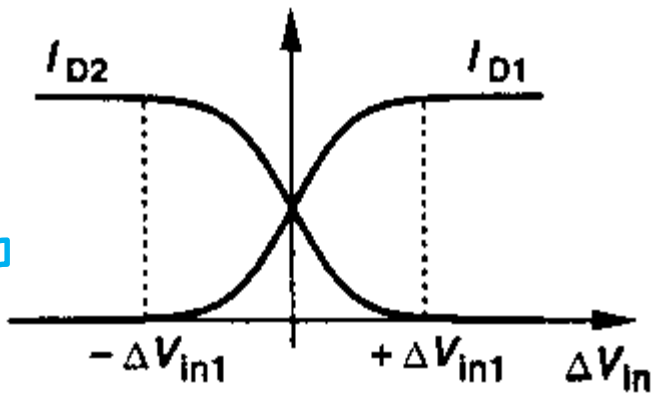
$\Delta V_{in1}$  represents the maximum differential signal a differential pair can handle.



Beyond  $|\Delta V_{in1}|$ , only one transistor is ON and therefore draws all of the  $I_{SS}$

## Differential Pair – Large Signal Analysis
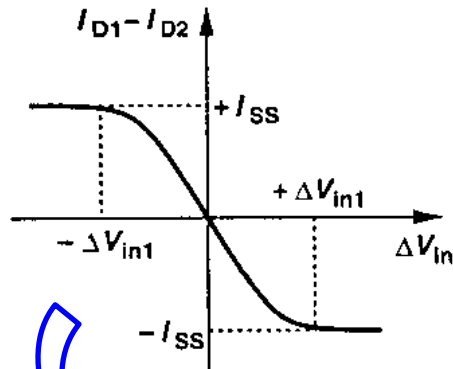
### Quantitative Analysis – differential input




**W/L Constant**


Increase  $\Delta V_{in1} \rightarrow$  by increasing  $I_{SS}$

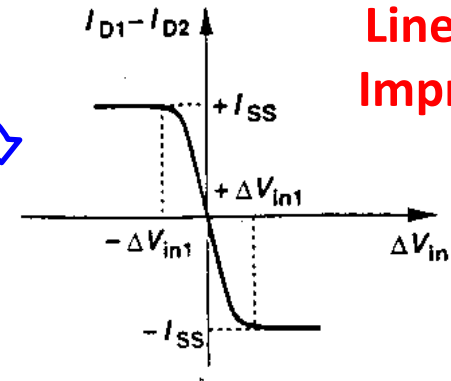**$I_{SS}$  Constant**

Reduce  $\Delta V_{in1} \rightarrow$  by increasing W/L



**Linearity Improves**

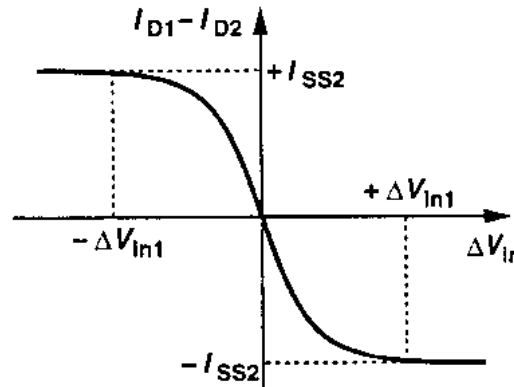

**Linearity Improves**

Linearity of a differential pair can be improved by decreasing W/L and/or increasing  $I_{SS}$

## MOS Differential Pair – small signal analysis

### Quantitative Analysis – differential input

- From large signal analysis we achieved:


$$\therefore |A_v| = \frac{V_{out1} - V_{out2}}{\Delta V_{in}} = g_m R_D$$

$$\therefore |A_v| = \frac{V_{out1} - V_{out2}}{\Delta V_{in}} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} R_D$$

At equilibrium, this is  $g_m$


- How to arrive at this result using small signal analysis?
  - Two techniques
    - Superposition method
    - Half-circuit concept

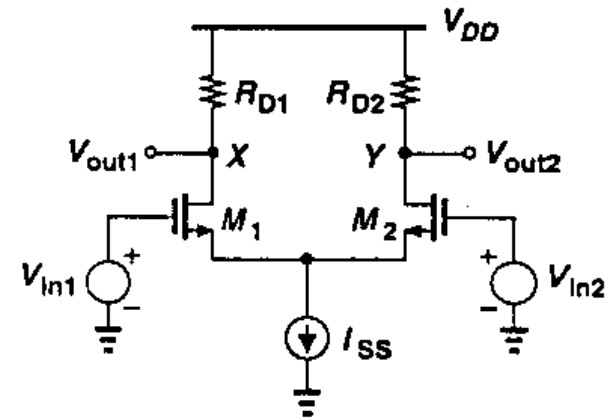- We apply **small signals** to  $V_{in1}$  and  $V_{in2}$  and assume  $M_1$  and  $M_2$  are already operating in saturation.


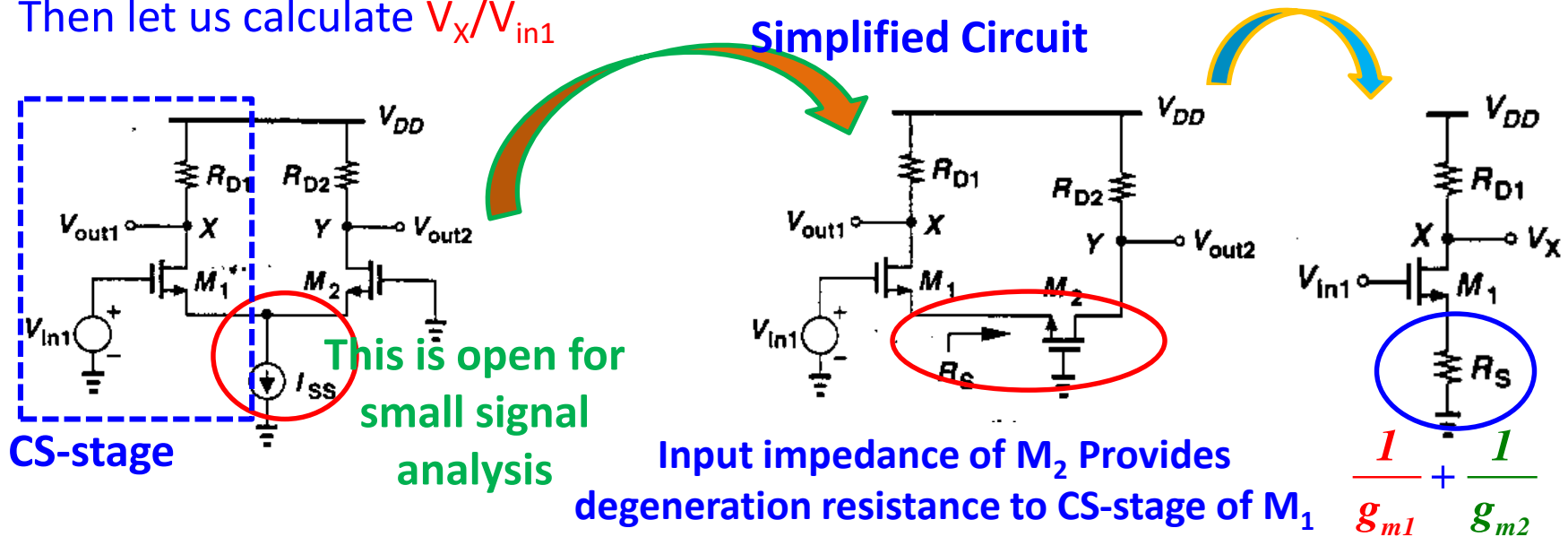
## MOS Differential Pair – small signal analysis

- Method-I: Superposition technique – the idea is to see the effect of  $V_{in1}$  and  $V_{in2}$  on the output and then combine to get the differential small signal voltage gain
- First set,  $V_{in2} = 0$
- Then let us calculate  $V_X/V_{in1}$




$$\therefore \frac{V_X}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$\frac{V_X}{V_{in1}} = \frac{-R_{D1}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$
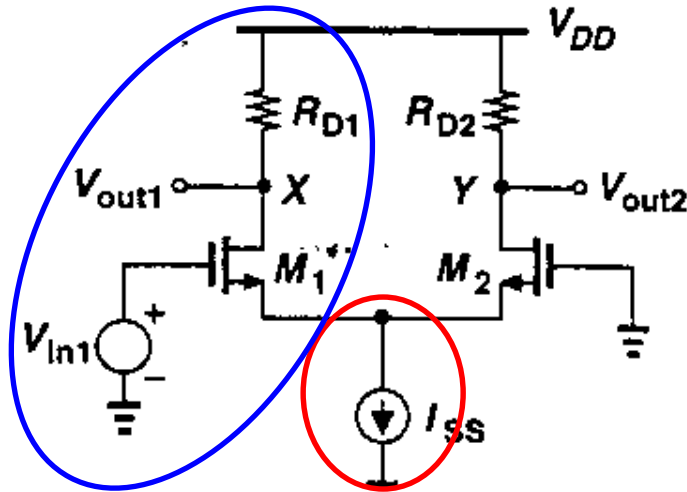
## MOS Differential Pair – small signal analysis


- Superposition technique
  - Now calculate  $V_Y/V_{in1}$



Replace  $M_1$  by its  
Thevenin Equivalent  
Circuit

This is open for  
small signal  
analysis

Simplified Circuit

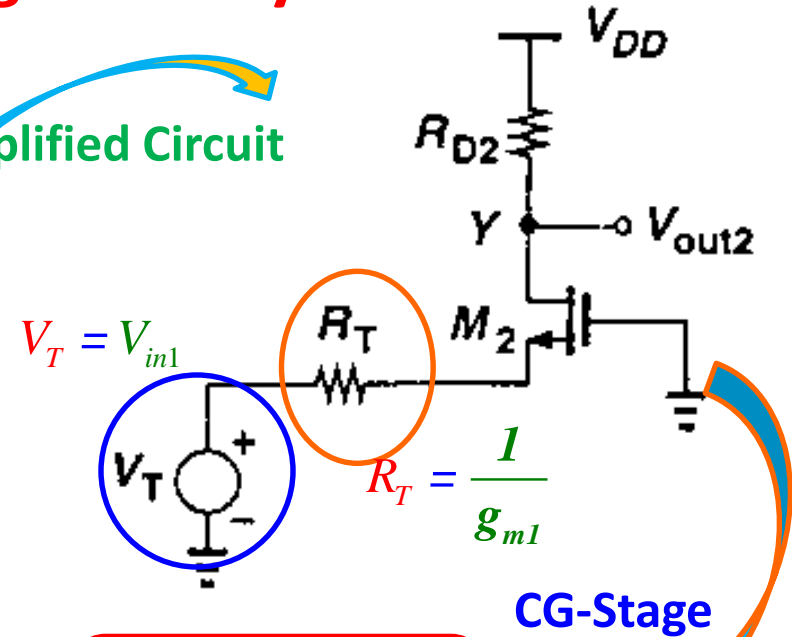

CG-Stage

$$\therefore \frac{V_Y}{V_{in1}} = \frac{R_D}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$

- combine the expressions to calculate small signal voltage only due to  $V_{in1}$

$$\frac{(V_X - V_Y)|_{due\_to\_V_{in1}}}{V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

## MOS Differential Pair – small signal analysis


For matched transistors:  $(V_X - V_Y)|_{due\_to\_V_{in1}} = -g_m R_D V_{in1}$

• Similarly:  $(V_X - V_Y)|_{due\_to\_V_{in2}} = g_m R_D V_{in2}$

• Superposition gives:  $A_v = \frac{(V_X - V_Y)_{total}}{V_{in2} - V_{in1}} = -g_m R_D$
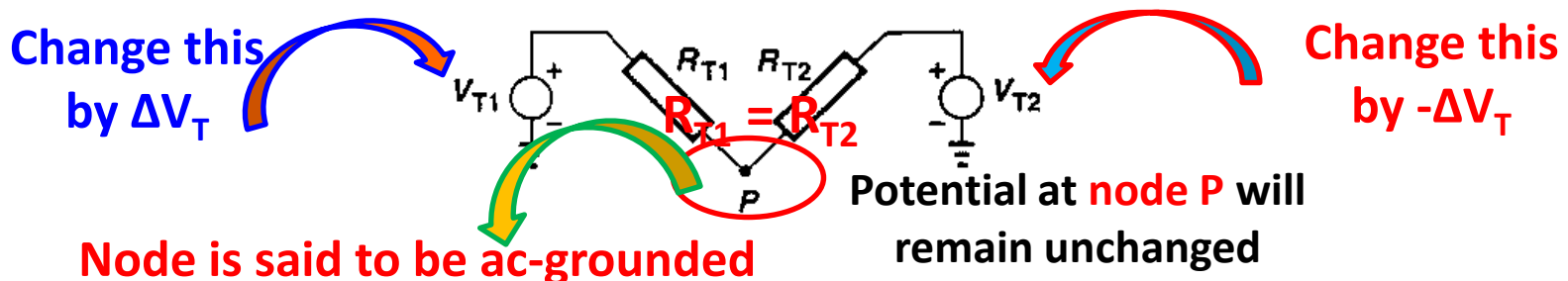
### • Half Circuit Approach


- If a fully symmetric differential pair senses differential inputs (i.e, the two inputs change by equal and opposite amounts from the equilibrium condition), then the concept of half circuit can be applied.



- The magnitude of differential gain is  $g_m R_D$  regardless of how the inputs are applied
- The gain will be halved if single ended output is considered

## MOS Differential Pair – small signal analysis

- Half Circuit Approach

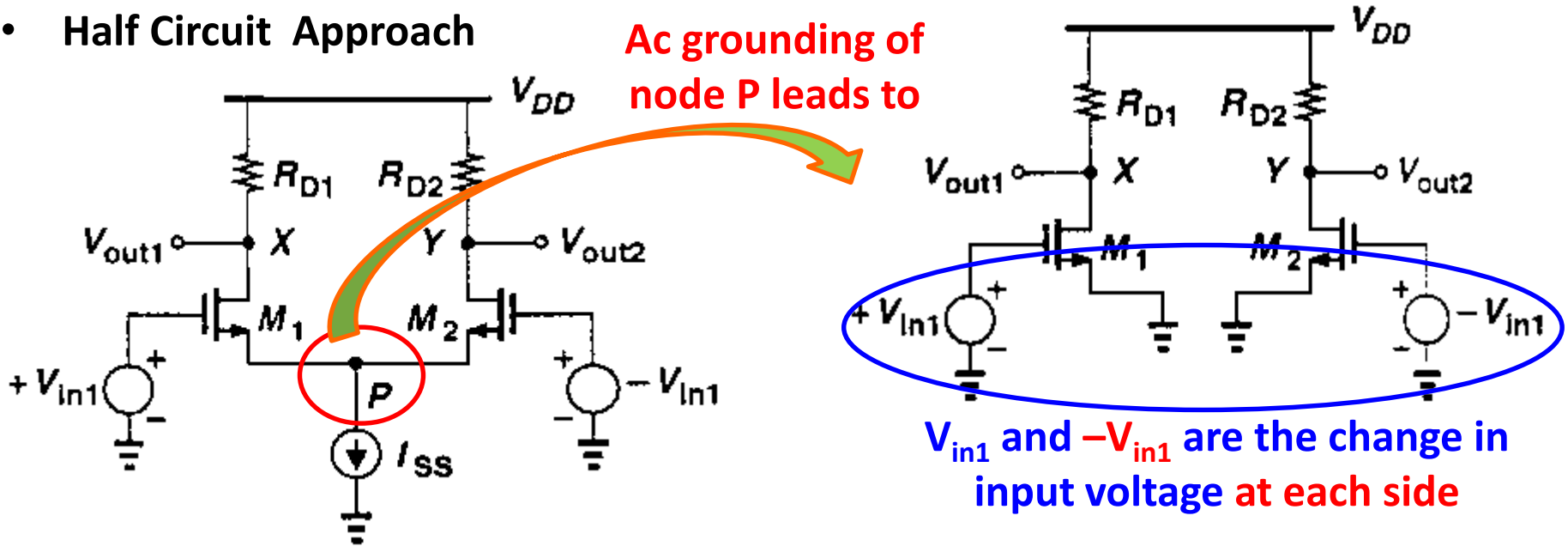

We can write:

$$\frac{V_X}{V_{in1}} = -g_m R_D$$

$$\frac{V_Y}{-V_{in1}} = -g_m R_D$$

Therefore the differential output can be expressed as:

$$V_X - V_Y = 2V_{in1}(-g_m R_D)$$

Thus the small signal voltage gain is:

$$A_v = \frac{V_X - V_Y}{2V_{in1}} = -g_m R_D$$


## MOS Differential Pair – small signal analysis

- How does the gain of a differential amplifier compare with a CS stage?
  - For a given total bias current  $I_{SS}$ , the value of equivalent  $g_m$  of a differential pair is  $1/\sqrt{2}$  times that of  $g_m$  of a single transistor biased at the  $I_{SS}$  with the same dimensions. Thus the total gain is proportionally less.
  - Equivalently, for given device dimensions and load impedance, a differential pair achieves the same gain as a CS stage at the cost of twice the bias current.
- What is the advantage of differential stage then?
  - Definitely the noise suppression capability. Right?


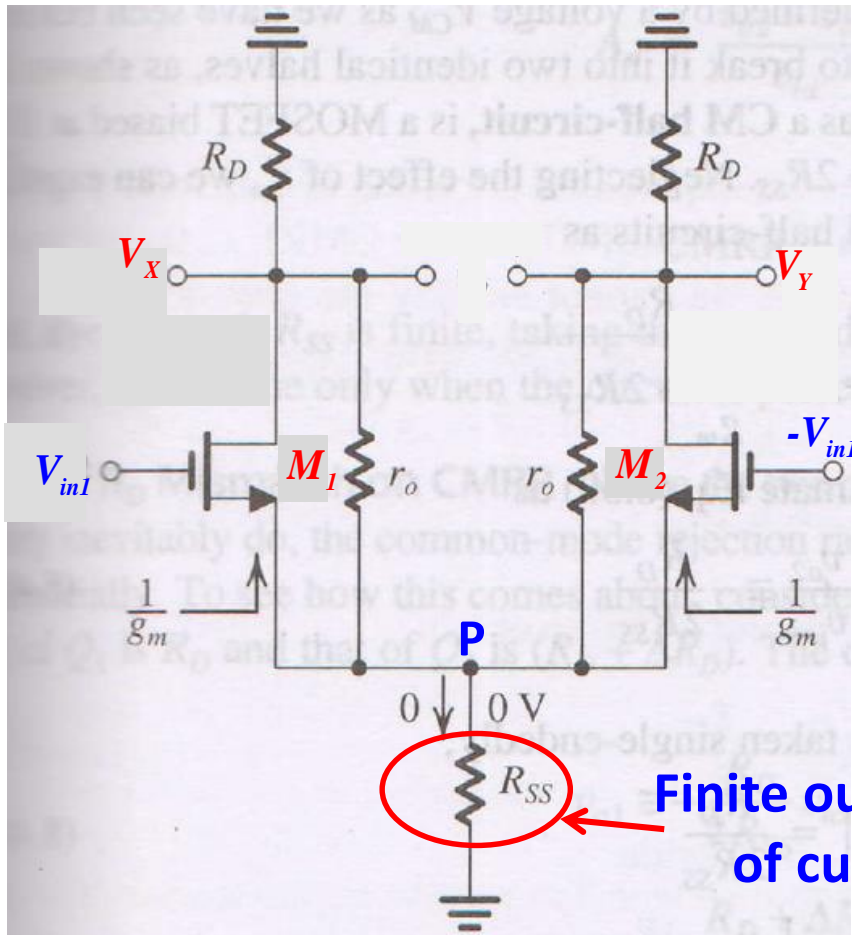
## MOS Differential Pair – small signal analysis

- How is gain affected if channel length modulation is considered?



- Effect of  $r_o$  on the gain

→ the circuit is still symmetric → the voltage at node P will be zero



No current through  $R_{SS}$




$R_{SS}$  plays no role in differential gain

Finite output resistance of current source
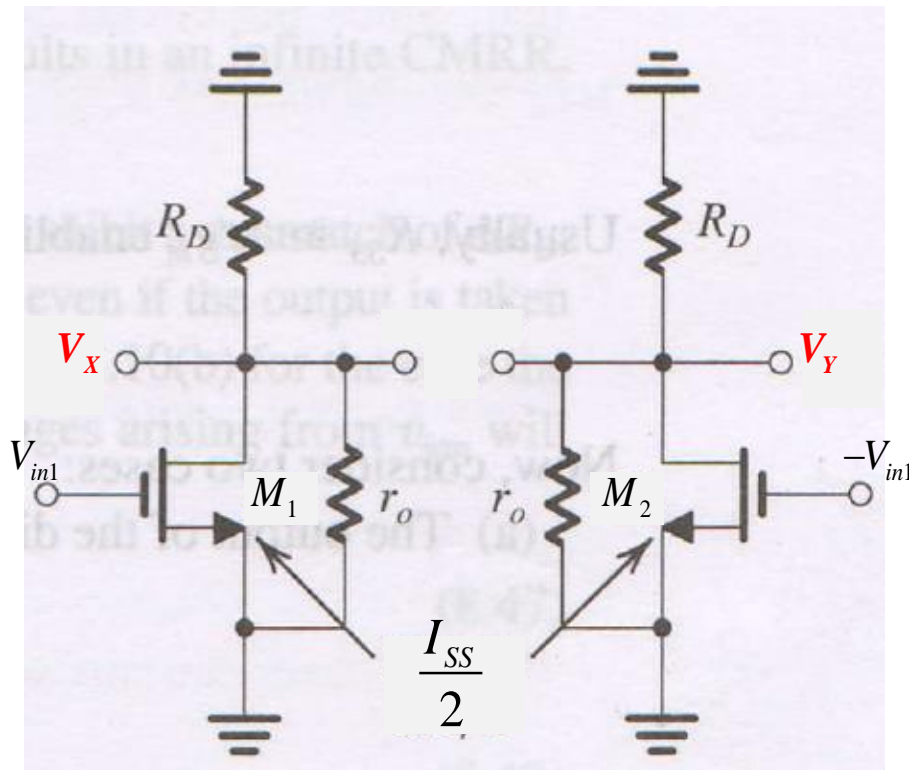
## MOS Differential Pair – small signal analysis

- The virtual ground on the source allows division of two identical CS amplifiers: → differential half circuits




$$V_X = -g_m V_{in1} (R_D \parallel r_o)$$

$$V_Y = g_m V_{in1} (R_D \parallel r_o)$$


$$\Rightarrow V_X - V_Y = -g_m (2V_{in1}) (R_D \parallel r_o)$$

$$\therefore A_v = \frac{V_X - V_Y}{2V_{in1}} = -g_m (R_D \parallel r_o)$$

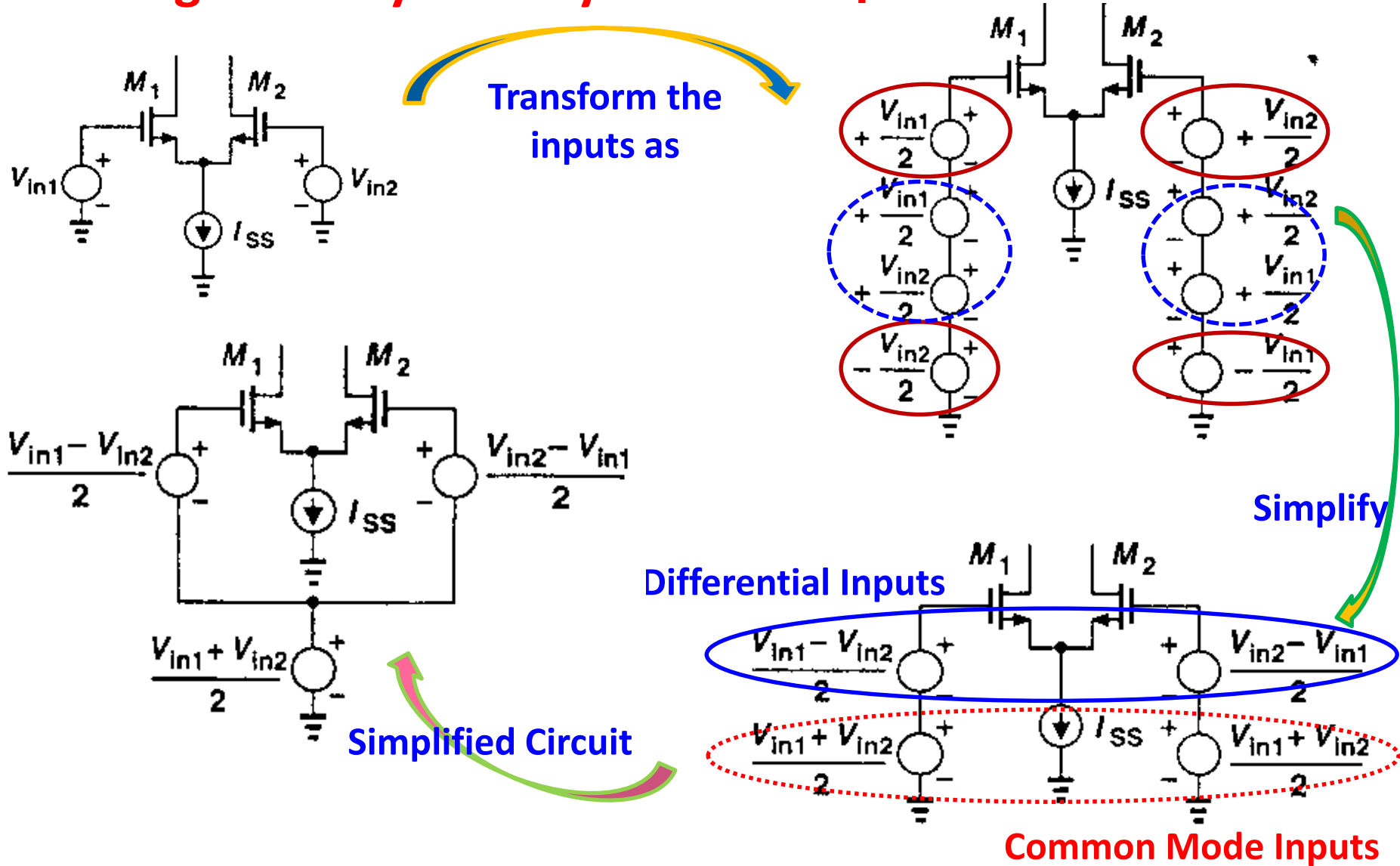
## Small signal analysis – asymmetric inputs


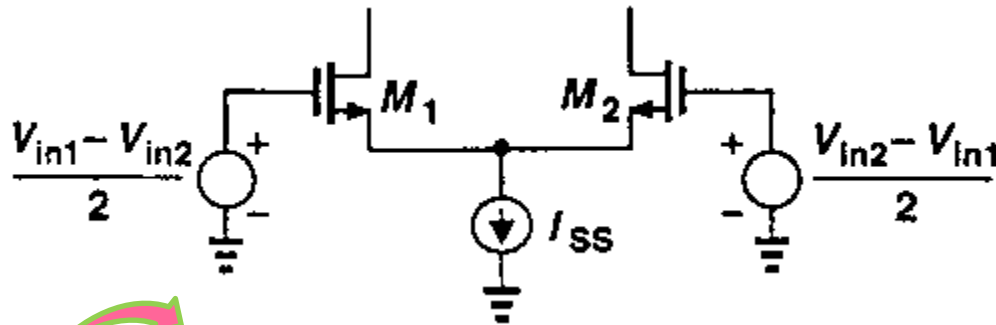
## Small signal analysis – asymmetric inputs



Circuit for Differential Mode

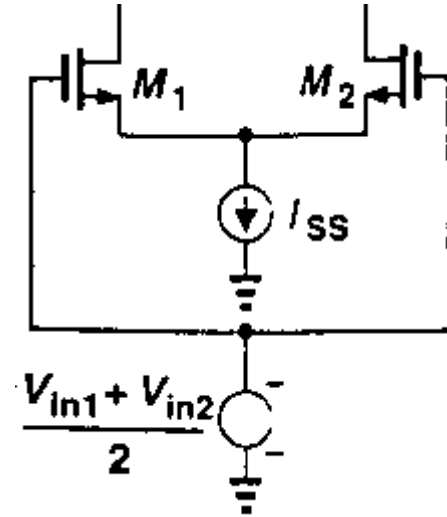

Circuit for Common Mode

$$V_X - V_Y = -g_m (R_D \parallel r_o) (V_{in1} - V_{in2})$$

If the circuit is fully symmetric and  $I_{SS}$  is ideal current source, then  $M_1$  and  $M_2$  draws half of  $I_{SS}$  and is independent of  $V_{in,CM}$ . The  $V_X$  and  $V_Y$  experience no change as  $V_{in,CM}$  varies. In essence, the circuit simply amplifies the difference between  $V_{in1}$  and  $V_{in2}$  while eliminating the effect of  $V_{in,CM}$ .