

Lecture – 13


Date: 29.09.2016

- Common Mode Rejection Ratio
- Non-Idealities in Differential Amplifier


Common Mode Rejection Ratio (CMRR)

- Differential input amplifiers are devices/circuits that can input and amplify differential signals and suppress common-mode signals
 - This includes operational amplifiers, instrumentation amplifiers, and difference amplifiers


Operational
Amplifier

 

Difference
Amplifier

 


Instrumentation
Amplifiers

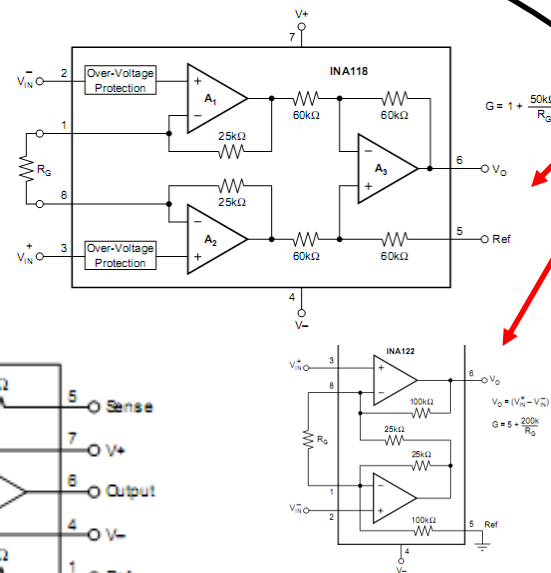


Common Mode Rejection Ratio (CMRR) (contd.)

 - For a differential input amplifier, common-mode voltage is defined as the average of the two input voltages.



Common Mode Rejection Ratio (CMRR) (contd.)

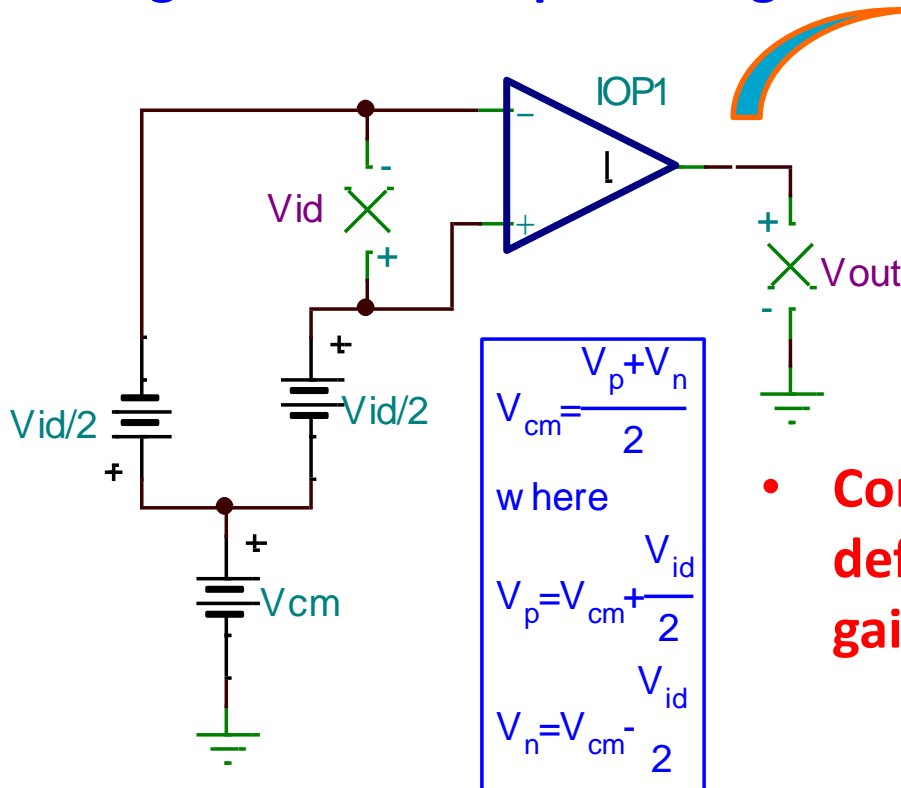- For a differential amplifier, common-mode voltage is defined as the average of the two input voltages.



$$V_{out} = A_{dm}(V_{id}) + A_{cm}(V_{cm})$$

where

A_{dm} = Differential - mode gain

A_{cm} = Common - mode gain

- Common-Mode Rejection Ratio is defined as the ratio of the differential gain to the common-mode gain.**


$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right|$$

- CMR is defined as:

$$CMR(dB) = 20 \log_{10}(CMRR)$$


Common Mode Rejection Ratio (CMRR) (contd.)

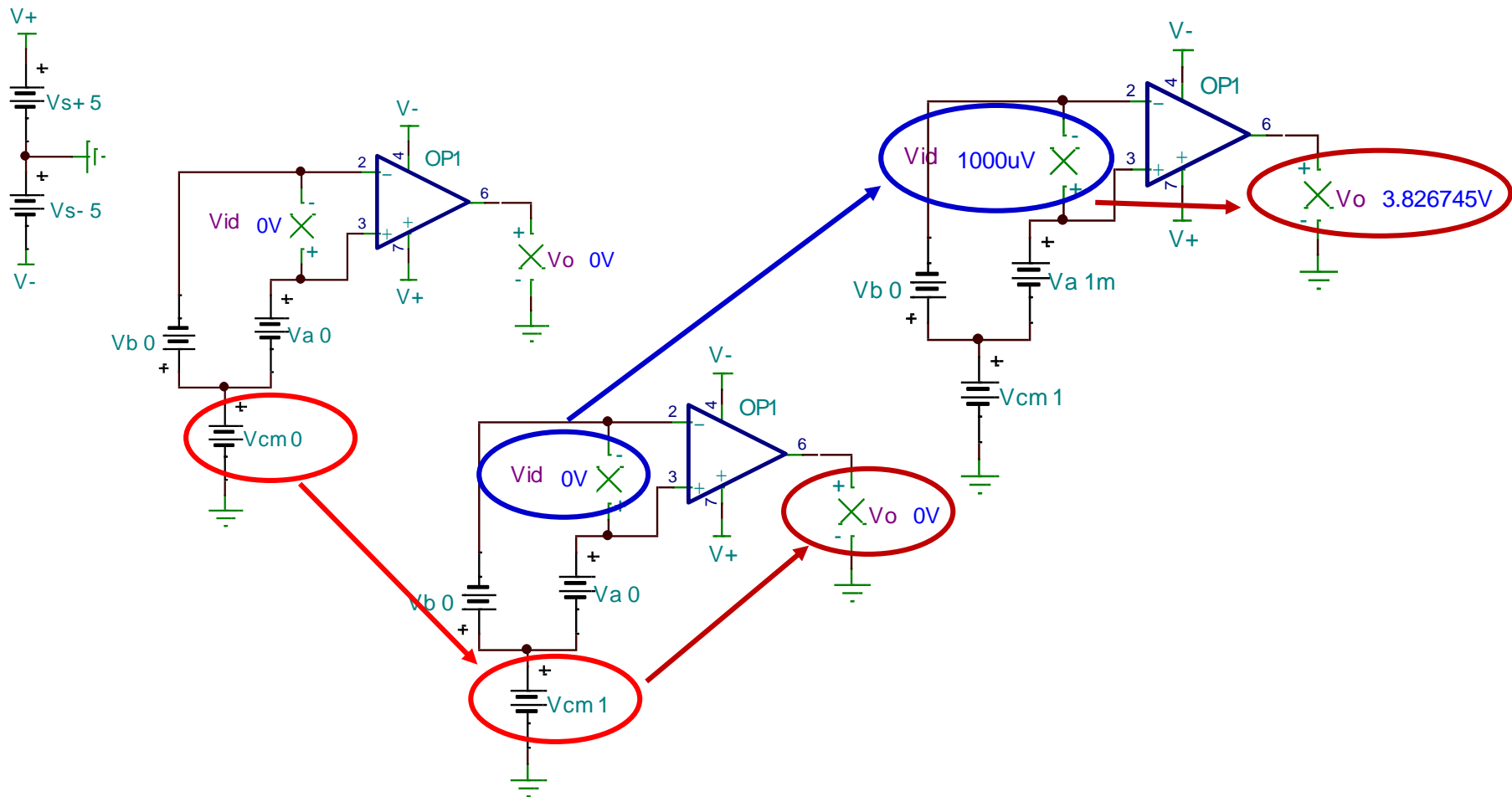- Ideally a differential input amplifier only responds to a differential input voltage, not a common-mode voltage.



Common Mode Rejection Ratio (CMRR) (contd.)

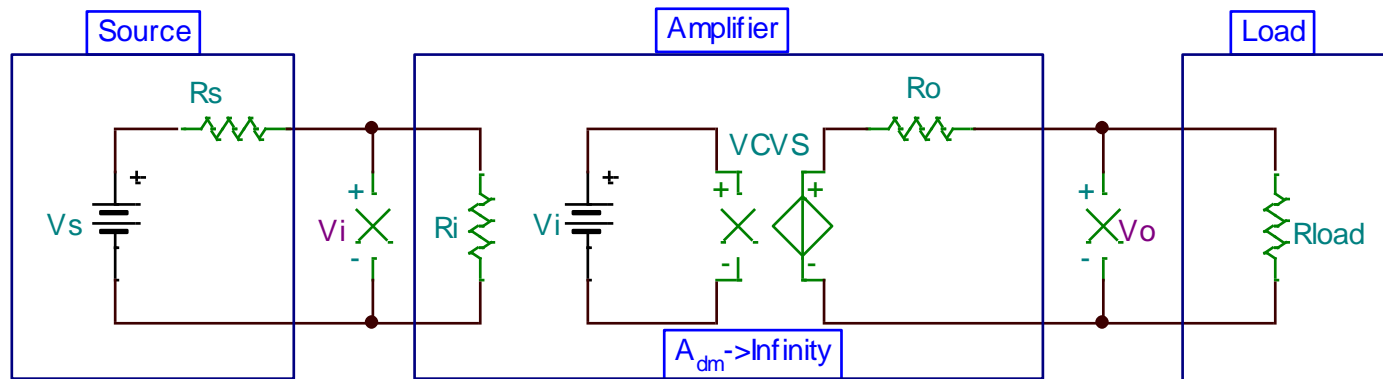- What is the CMRR of an ideal differential input amplifier (e.g. op-amp)?
- Recall that the ideal common-mode gain of a differential input amplifier is **ZERO**
- Voltage Amplifier Model:



- Also recall that the differential gain of an ideal op-amp is some high value.

• Therefore:

$$CMRR_{ideal-OA} = \frac{A_{dm}}{A_{cm}} = \frac{A_{dm} \rightarrow \infty}{A_{cm} \rightarrow 0} \rightarrow \infty$$

Common Mode Rejection Ratio (CMRR) (contd.)


Real Op-Amp CMRR

- There will be a common-mode gain due to the following
 - **Asymmetry in the circuit**
 - Mismatched source and drain resistors
 - Signal source resistances
 - Gate-drain capacitances
 - transconductances
 - Gate leakage currents
 - **Finite output impedance of the tail current source**
 - **Changes with frequency due to tail current source's shunt capacitance**
- These issues will manifest themselves through converting common-mode variations to differential components at the output and variation of the output common-mode level

Common Mode Rejection Ratio (CMRR) (contd.)

Modeling CMRR

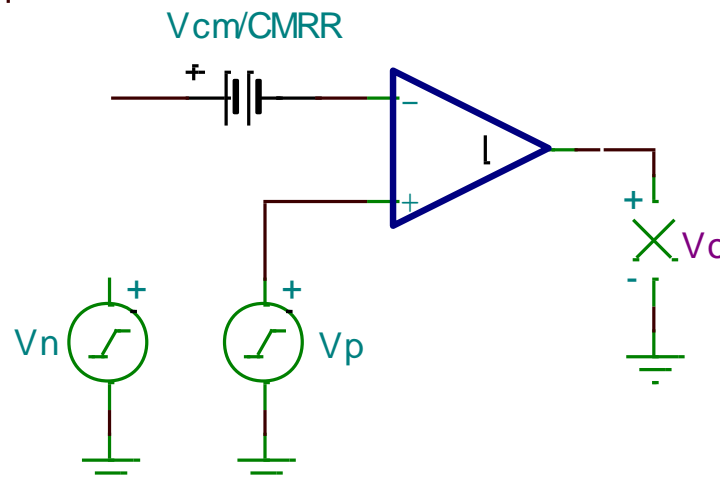
- Now that we understand what CMRR is and what affects it in operational amplifiers, let's see how it can affect a circuit.
- **First, however, we need to understand the model**
- **To be useful, CMRR needs to be referred-to-input (RTI)**
- **We can then represent it as a voltage source (aka offset voltage) in series with an input. The magnitude (RTI) is $V_{cm}/CMRR$.**



Common Mode Rejection Ratio (CMRR) (contd.)

OA CMRR Error

- Example: non-inverting buffer

 

$$V_o = A(V_p - V_n)$$

$$V_n = V_o \pm \frac{V_{cm}}{CMRR}$$

Note that $V_{cm} \approx V_p$

$$V_o = A\left(V_p - V_o \pm \frac{V_p}{CMRR}\right)$$

$$\frac{V_o}{V_p} = \frac{A\left(1 \pm \frac{1}{CMRR}\right)}{1 + A}$$

As $A \rightarrow \infty$


$$\frac{V_o}{V_p} \rightarrow 1 \pm \frac{1}{CMRR}$$

Clearly this factor
should be as small as
possible

Common Mode Rejection Ratio (CMRR) (contd.)

CMRR of Difference Amplifiers

 
- A difference amplifier is made up of a differential amplifier (operational amplifier) and a resistor network as shown below
- The circuit meets our definition of a differential amplifier
- The output is proportional to the difference between the input signals



Common Mode Rejection Ratio (CMRR) (contd.)

CMRR of Difference Amplifiers

 - Let's replace V_1 and V_2 with our alternate definition of the inputs (in terms of differential-mode and common-mode signals).



$$V_1 = V_{cm} - \frac{V_{dm}}{2}$$

$$V_2 = V_{cm} + \frac{V_{dm}}{2}$$

$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

$$V_o = \frac{R_2}{R_1} \left(\left(V_{cm} + \frac{V_{dm}}{2} \right) - \left(V_{cm} - \frac{V_{dm}}{2} \right) \right)$$


$$V_o = \frac{R_2}{R_1} (V_{dm})$$

- It is readily apparent that an ideal difference amplifier's output should only amplify the differential-mode signal...not the common-mode signal.

Common Mode Rejection Ratio (CMRR) (contd.)

CMRR of Difference Amplifiers

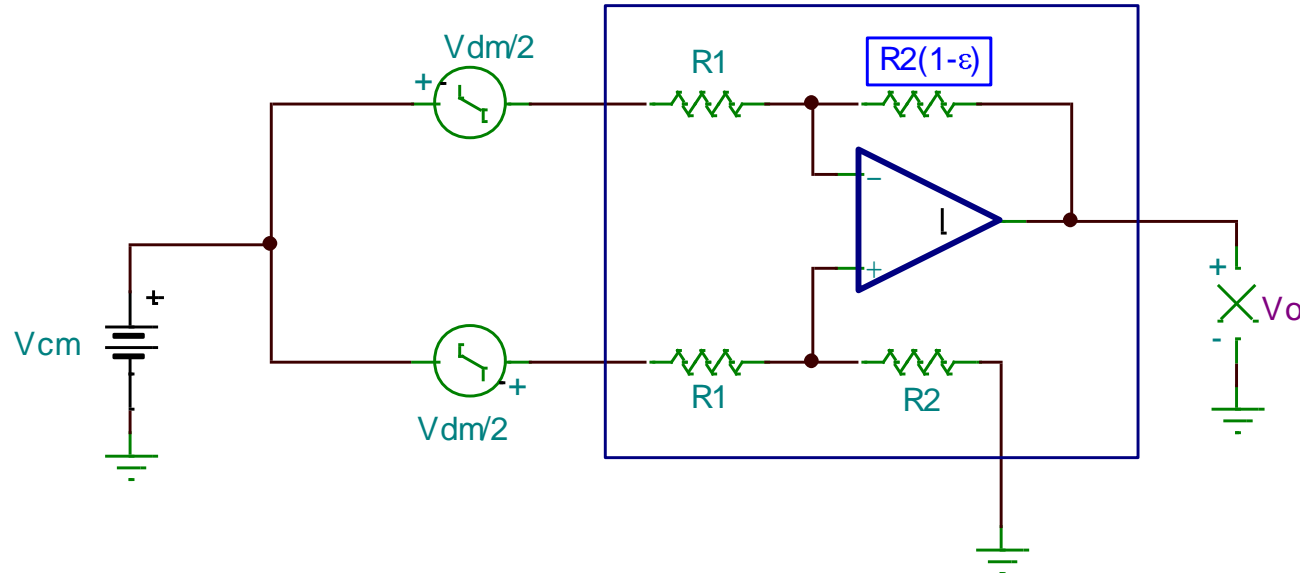- The last expression is based on the premise that the operational amplifier is ideal and that the resistors are balanced
- Keeping the assumption that the operational amplifier is ideal, let's see what happens when an imbalance factor (ϵ) is introduced



Common Mode Rejection Ratio (CMRR) (contd.)

CMRR of Difference Amplifiers

- Using superposition we find that:

$$V_o = \left(V_{cm} - \frac{V_{dm}}{2} \right) \left(-\frac{R_2(1-\varepsilon)}{R_1} \right) + \left(V_{cm} + \frac{V_{dm}}{2} \right) \left(\frac{R_2}{R_1 + R_2} \right) \left(1 + \frac{R_2(1-\varepsilon)}{R_1 + R_2(1-\varepsilon)} \right)$$

- After simplification we find that:

$$V_o = A_{dm} V_{dm} + A_{cm} V_{cm}$$

where

$$A_{dm} = \frac{R_2}{R_1} \left(1 - \frac{R_1 + 2R_2}{R_1 + R_2} \times \frac{\varepsilon}{2} \right)$$

$$A_{cm} = \frac{R_2}{R_1 + R_2} \times \varepsilon$$

As expected, an imbalance affects the differential and common-mode gains, which will affect CMRR!

As the error $(\varepsilon) \rightarrow 0$, $A_{dm} \rightarrow R_2/R_1$ and $A_{cm} \rightarrow 0$

Common Mode Rejection Ratio (CMRR) (contd.)

CMRR of Difference Amplifiers

- Since we have equations for A_{cm} and A_{dm} , let's look at CMR:

$$CMR(dB) = 20 \log_{10} \left(\frac{A_{dm}}{A_{cm}} \right) = 20 \log_{10} \left(\frac{\frac{R_2}{R_1} \left(1 - \frac{R_1 + 2R_2}{R_1 + R_2} \times \frac{\varepsilon}{2} \right)}{\frac{R_2}{R_1 + R_2} \times \varepsilon} \right)$$

- If the imbalance is sufficiently small we can neglect its effect on A_{dm}
- With that and some algebra we find:

$$CMR(dB) \cong 20 \log_{10} \left(\frac{1 + \frac{R_2}{R_1}}{\varepsilon} \right)$$

- This equation shows two very important relationships


- As the gain of a difference amplifier increases (R_2/R_1), CMR increases
- As the mismatch (ε) increases, CMR decreases

Please remember that this just shows the effects of the resistor network and assumes an ideal amplifier

Common Mode Rejection Ratio (CMRR) (contd.)

CMRR of Difference Amplifiers

 - Another possible source for CMRR degradation is the impedance at the reference pin.
- So far we have connected this pin to low-impedance ground.



- Placing an impedance here will disturb the voltage divider we come across during superposition analysis.
- This will negatively affect CMR

Common Mode Rejection Ratio (CMRR) (contd.)

CMRR of Difference Amplifiers

Pros:

- Difference amplifiers amplify differential signals and reject common-mode signals
- The common-mode rejection is based mainly on resistor matching
- Difference amplifiers can be used to protect against ground disturbances

Cons:


- Externally changing the gain of a difference amplifier is not worthwhile
- The input impedance is finite
 - This means that a difference amplifier will load the input signals
 - If the input signal source's impedances are not balanced, CMR could be degraded
- Is there a way we can amplify differential signals, change the gain, retain high CMR, and not load our source?
- Yes! Buffer the inputs...this creates an Instrumentation Amplifier (IA).

Common Mode Rejection Ratio (CMRR) (contd.)


Instrumentation Amplifiers

There are 2 common types of instrumentation amplifiers

2 op-amp (e.g. INA122)

 


3 op-amp (e.g. INA333)

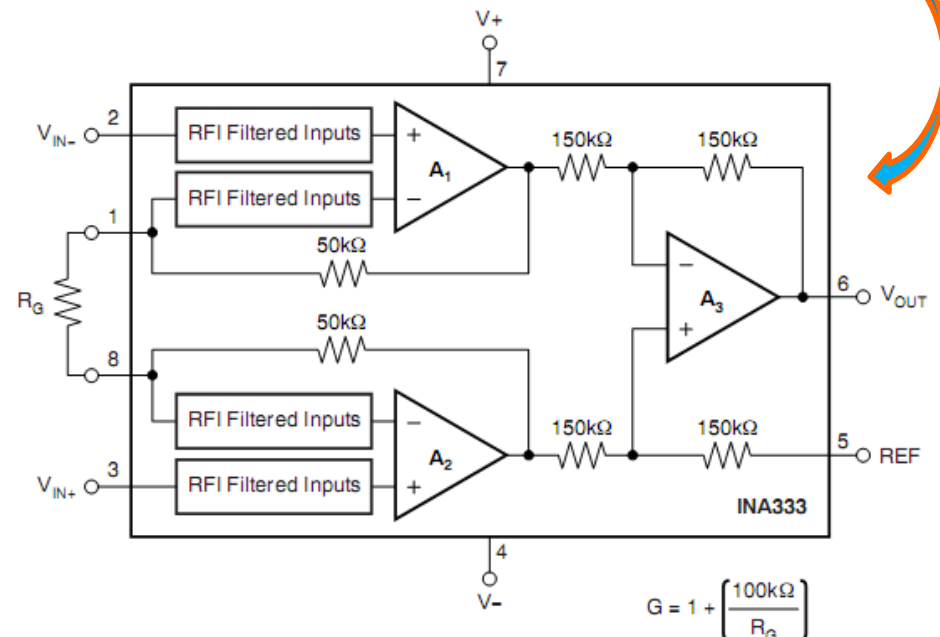

Common Mode Rejection Ratio (CMRR) (contd.)


Instrumentation Amplifiers

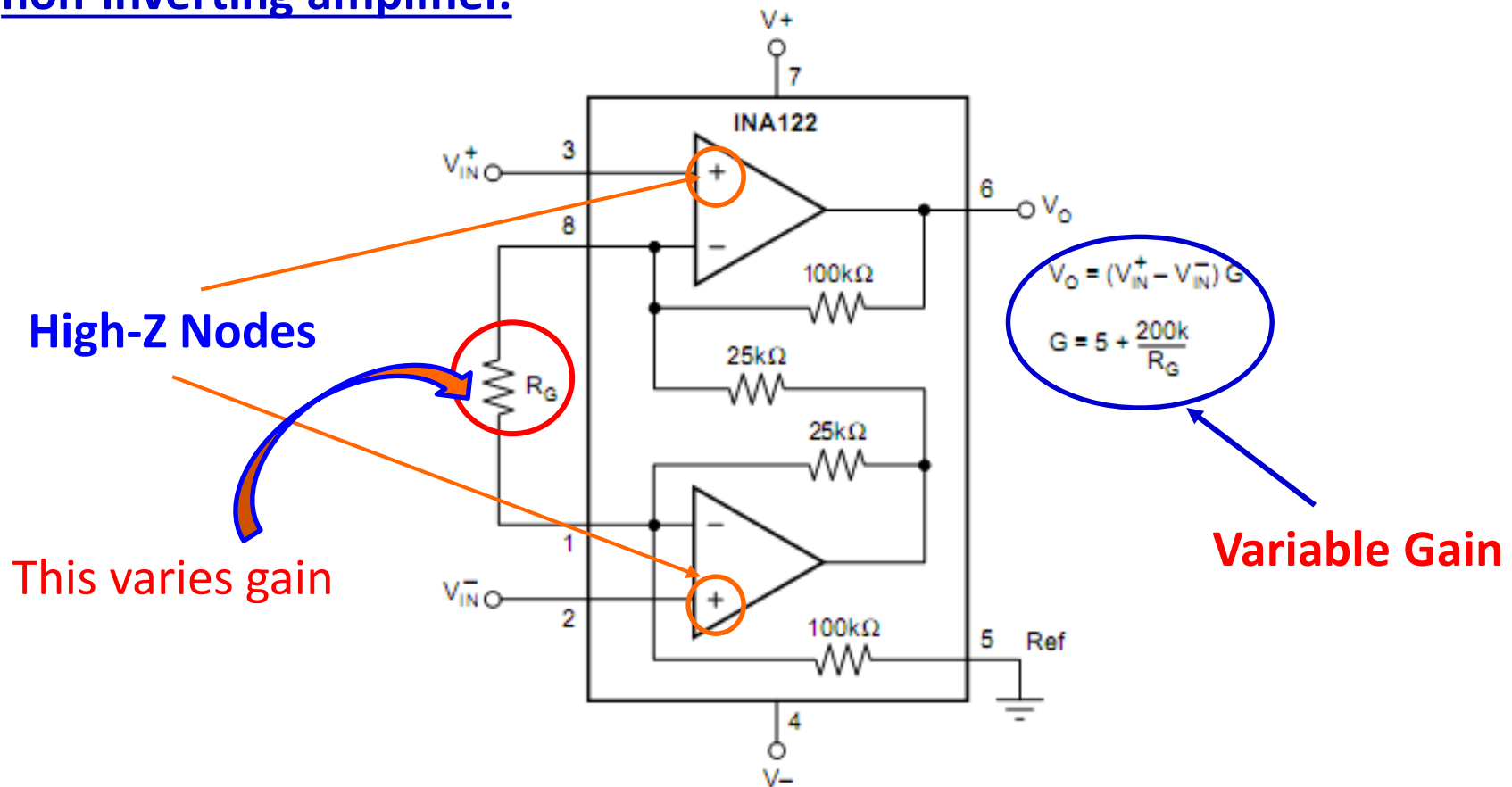- Notice both have gain equations so you can vary the gain.
- Notice the input impedance is that of the non-inverting terminal of a non-inverting amplifier.



Common Mode Rejection Ratio (CMRR) (contd.)

Instrumentation Amplifiers

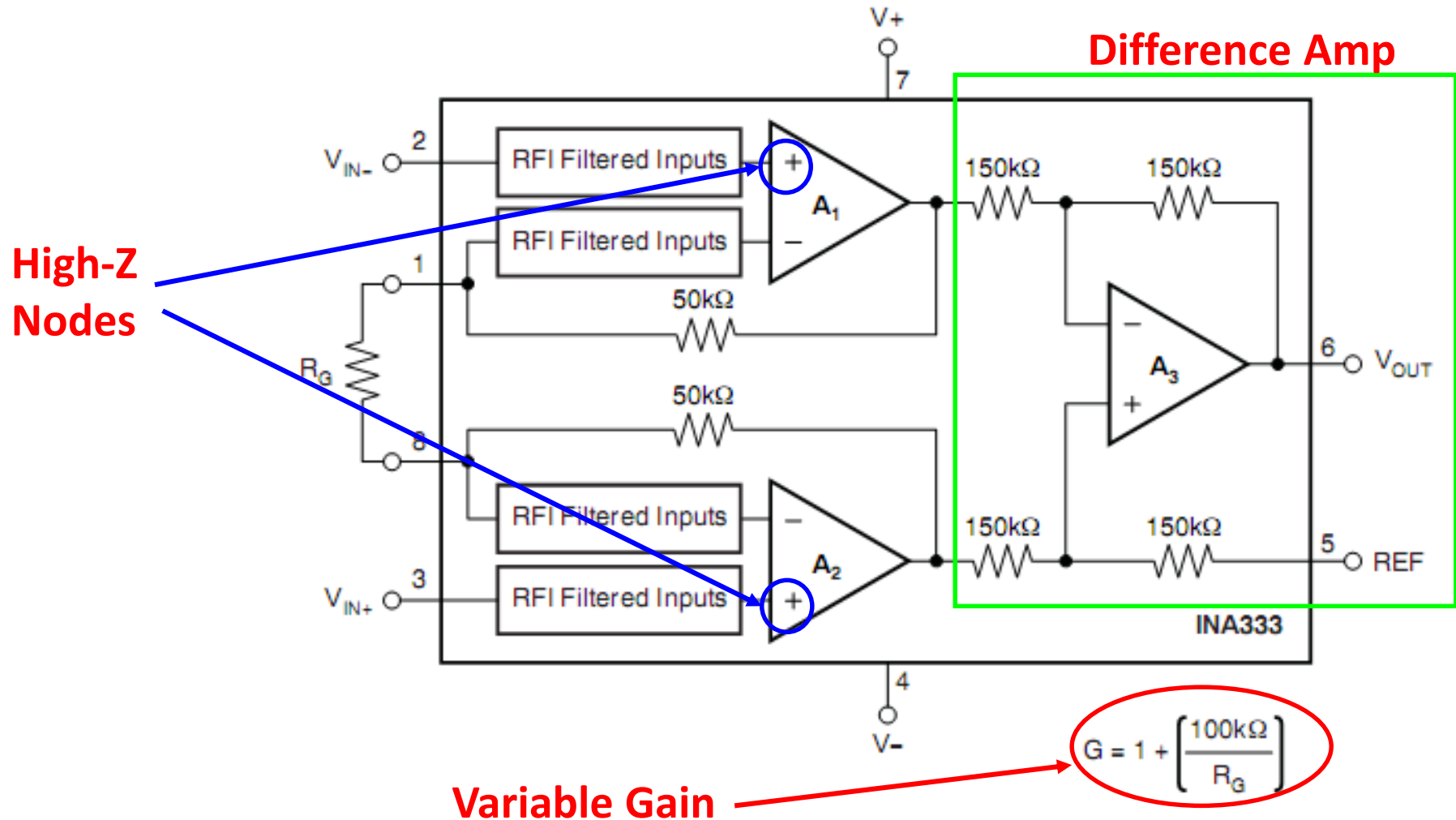

Common Mode Rejection Ratio (CMRR) (contd.)

Instrumentation Amplifiers


- So, what is the CMRR of an instrumentation amplifier?
- Instrumentation amplifiers reject common-mode signals ($A_{cm} \rightarrow 0$)

- Recall:
$$CMRR = \frac{A_{dm}}{A_{cm}}$$

CMRR is directly related to differential gain. Since we can change the differential gain of an IA, we also change the CMRR.

Non-ideal Characteristics of Differential Amplifier

 - DC Offset Problems
- Due to mismatch in load resistances, mismatch in W/L , and mismatch in V_T



- Mismatch in R_D

$$R_{D1} = R_D + \frac{\Delta R_D}{2} \qquad R_{D2} = R_D - \frac{\Delta R_D}{2}$$

$$V_{out1} = V_{DD} - \frac{I_{SS}}{2} \left(R_D + \frac{\Delta R_D}{2} \right)$$

$$V_{out2} = V_{DD} - \frac{I_{SS}}{2} \left(R_D - \frac{\Delta R_D}{2} \right)$$

- Therefore differential output:


$$V_o = V_{out2} - V_{out1} = \left(\frac{I_{SS}}{2} \right) \Delta R_D$$

Non-zero ← Unwanted ← polarity unknown a priori


- Offset signal appears due to mismatch → differential can overcome this offset problem

Differential Amplifier with Active Load

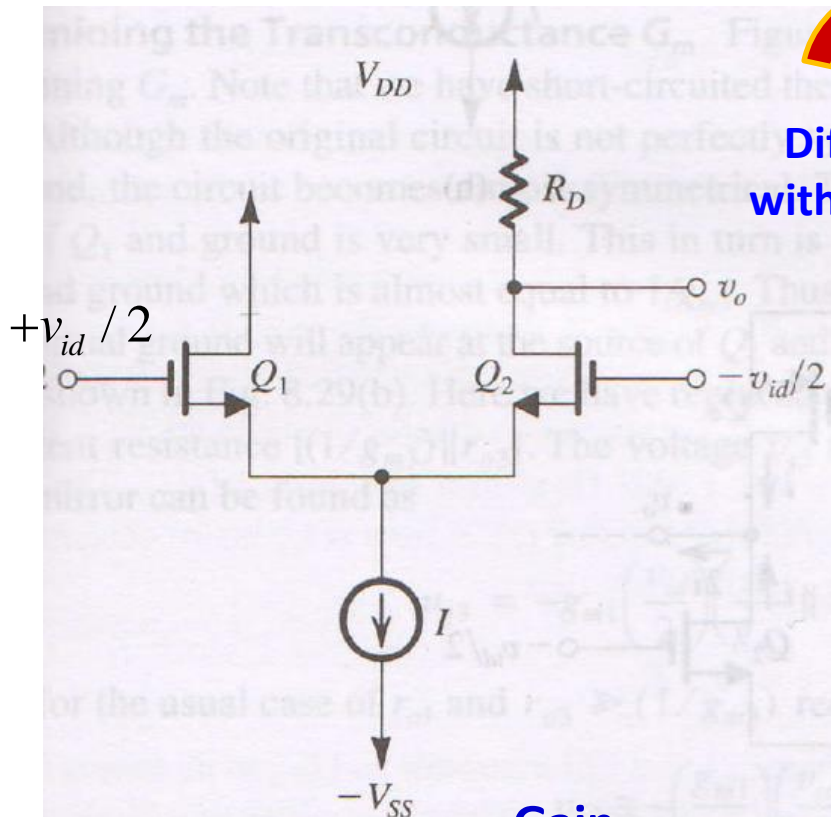- However most systems are single-ended \rightarrow require single ended signal \rightarrow what is the solution?



Differential pair with current mirror

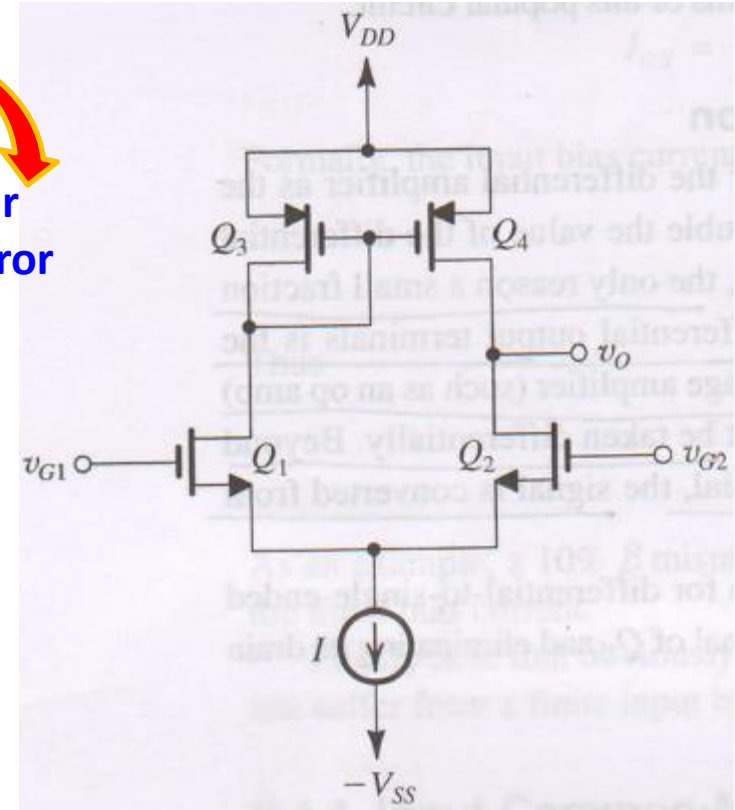

No. Why?




reduces to half

Gain


Although this solves the problem but any mismatch in Q_3 and Q_4 will cause variations in the eventual output

Differential Pair with Active Loads

 - It can help in mitigating the common-mode to differential conversion arising out from R_D mismatch.




 Its easier to define output
CM level as M_3/M_4 are in
saturation by default



M_3/M_4 are not in
saturation by default &
therefore output CM level
not well defined

 Differential Pair with Active Loads (contd.)



- Differential pair with ideal current source:

$$A_v = - \frac{\left(\frac{1}{g_{mP}} \right)}{\left(\frac{1}{g_{mN}} \right)} = - \frac{g_{mN}}{g_{mP}}$$

Dependence on
scaling factor and
process parameters


- Precision comes but with a price. What is that?
 - Reduced voltage swings

→ to increase gain → reduce $(W/L)_p$ → as a consequence V_{ov} of M_3/M_4 reduces → eventually lowers the CM level at the nodes X and Y → clipping in the negative cycle

Differential Pair with Active Loads (contd.)

Diode-connected Load:

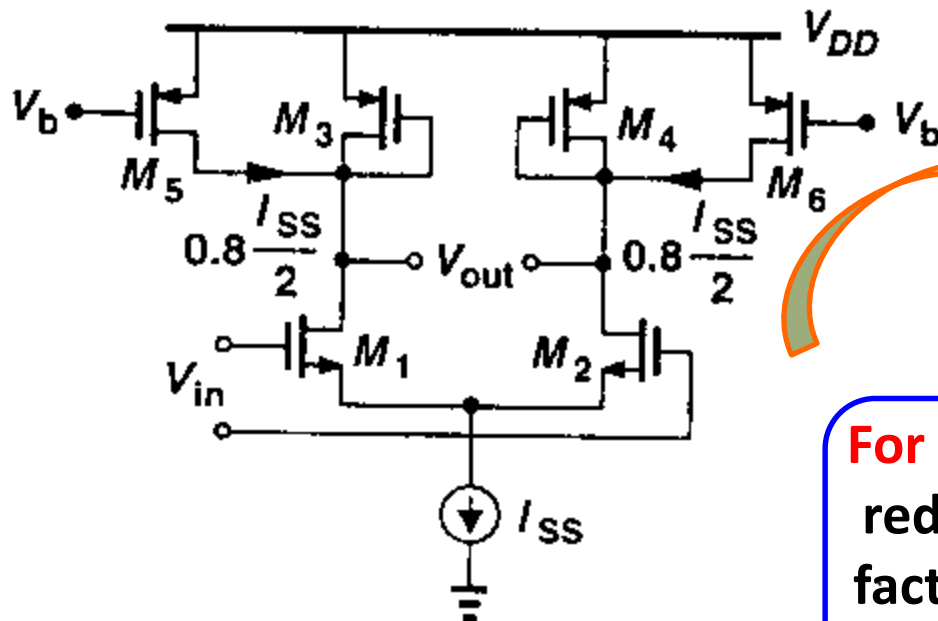- The output swing can be improved **IF** part of bias current to M_1 and M_2 can be provided by PMOS current sources
- The trick here is to reduce the g_m of M_3 and M_4 by lowering their **drain currents** instead of their aspect ratios



Here, M_5 and M_6 carry 80% of M_1 and M_2 → the current through M_3 and M_4 is reduced by a factor of 5

For a given $|V_{GSP} - V_{TP}|$, this allows reduction in g_m of M_3 and M_4 by a factor of 5 ← potentially enhances the gain by a factor of 5

Differential Pair with Active Loads (contd.)

Constant Current Sources:


- The small signal gain of differential pair with current source load is usually in the range of 10 – 20.
- How to increase the gain?
- Use Cascode structure both for NFET and PFET

Cascode will definitely enhance the small signal gain BUT at the cost of reduced voltage headroom


- By now we know, the load resistors in differential pair can be replaced by diode-connected or source-connected loads.
- It can help in mitigating the common-mode to differential conversion arising out from R_D mismatch.

Differential Pair with Active Load

- Using half-circuit approach:

 

 Differential pair with
ideal current source



$$A_v = -g_{mN} (r_{oN} \parallel r_{oP})$$

$$A_v = -g_{mN} (g_{mP}^{-1} \parallel r_{oN} \parallel r_{oP})$$

$$\therefore A_v \approx -\frac{g_{mN}}{g_{mP}} = -\sqrt{\frac{\mu_n (W/L)_N}{\mu_P (W/L)_P}}$$