




## Lecture – 7

Date: 01.09.2016

- CG Amplifier
- Examples
- Biasing in MOS Amplifier Circuits

## Common Gate (CG) Amplifier

 

- CG Amplifier- Input is applied at the Source and the output is sensed at the Drain.
- The Gate terminal is used for establishing appropriate bias conditions for the transistor.

- Its characteristic can be studied through large-signal behavior as well.

- For large  $V_{in}$  i.e. for  $V_{in} > V_b - V_T$ :  $M_1$  is off and therefore:  $V_{out} = V_{DD}$

- For lower  $V_{in}$ : 
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_T)^2$$

$$V_{out} = V_{DD} - I_D R_D = V_{DD} - \left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_T)^2 \right) R_D$$

- Then small signal gain is: 
$$\frac{\partial V_{out}}{\partial V_{in}} = - \left( \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_T) \left( -1 - \frac{\partial V_T}{\partial V_{in}} \right) \right) R_D$$



## Common Gate (CG) Amplifier (contd.)

- Since,  $\frac{\partial V_T}{\partial V_{in}} = \frac{\partial V_T}{\partial V_{SB}} = \eta$ :  $\frac{\partial V_{out}}{\partial V_{in}} = \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_T)(1 + \eta) R_D$

$$A_v = g_m (1 + \eta) R_D$$

Non-inverting Amplifier

Higher as compared to CS stage

  

**KVL in loop-1:**

$$V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0$$

**KVL in loop-2:**

$$V_{out} = r_o \left( \frac{-V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in}$$

$$\frac{V_{out}}{V_{in}} = A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D} R_D$$

## CG Amplifier (contd.)


$$\frac{V_{out}}{V_{in}} = A_v = \frac{(g_m + g_{mb})r_o + 1}{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D} R_D$$

Non-inverting with slightly higher value as compared to the CS stage → body effect is useful in this scenario

- If the resistor  $R_D$  is replaced by a current source then:  $\frac{V_{out}}{V_{in}} = A_v = (g_m + g_{mb})r_o + 1$

$R_D \rightarrow \infty$  for an ideal current source

 
- Let us look at small-signal model – without channel length modulation and biased with a constant current source



$$\Rightarrow A_v = \frac{V_{out}}{V_{in}} = (g_m + g_{mb})R_D = g_m(1 + \eta)R_D$$

## CG Amplifier (contd.)

- Input Impedance:

 


$$R_{in} = \frac{V_X}{I_X} = \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o} \approx \frac{R_D}{(g_m + g_{mb})r_o} + \frac{1}{(g_m + g_{mb})}$$

- Case-I:**  $R_D = 0 \rightarrow R_{in} = \frac{V_X}{I_X} = \frac{r_o}{1 + (g_m + g_{mb})r_o}$
- Case-II:**  $R_D$  is an ideal current source ie,  $R_D \rightarrow \infty \rightarrow R_{in} \rightarrow \infty$

It is apparent that the input impedance of common-gate stage is low only if the load impedance connected to the drain is low

## CG Amplifier (contd.)


- Output Impedance:

 

$$R_{out} = \left\{ \left[ 1 + (g_m + g_{mb})r_o \right] R_S + r_o \right\} \parallel R_D$$

 
### Example – 1

- Derive the small-signal voltage gain expression for this amplifier. Consider the cases when channel length modulation are absent and present.


 
## Example – 1 (contd.)

- **Case-I:**  $\lambda = 0$  both for  $M_1$  and  $M_2 \rightarrow$  In such a case  $M_2$  presents a degenerating impedance of  $1/g_{m2}$  to a single stage CS amplifier as shown below.




**Simplification gives:**  $V_{out} = -g_{m1} V_1 R_D$

$$\Rightarrow V_{out} = -g_{m1} R_D \cdot \frac{g_{m2} \cdot V_{in}}{g_{m2} + g_{m1}}$$

$$\therefore A_v = -\frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$
 
## Example – 1 (contd.)

- **Case-II:**  $\lambda = 0$  for  $M_1$  and  $\lambda \neq 0$  for  $M_2 \rightarrow$  In such a case  $M_2$  presents a degenerating impedance of  $(1/g_{m2} \parallel r_{o2})$  as shown below.




Simplification gives:

$$\therefore A_v = - \frac{R_D}{\frac{1}{g_{m1}} + \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

 
## Example – 1 (contd.)

- **Case-III:**  $\lambda = 0$  for  $M_2$  and  $\lambda \neq 0$  for  $M_1 \rightarrow$  In such a case the small signal model looks like:




 
## Example – 2

- Derive expression for the small-signal voltage gain of the following circuit. (Assume:  $\lambda \neq 0$  for both  $M_1$  and  $M_2$ . Neglect body effect)



  Gate and Source are fixed.  
Therefore this NMOS works as a constant current source with an impedance  $r_{o2}$  across its drain and source




$$g_{m1} (V_{in} - V_{out}) (r_{o1} \parallel r_{o2}) = V_{out}$$


$$\therefore A_v = \frac{V_{out}}{V_{in}} = \frac{(r_{o1} \parallel r_{o2})}{\left[ \frac{1}{g_{m1}} + (r_{o1} \parallel r_{o2}) \right]}$$
 
## Example – 3

- What is  $R_{out}$  in the following circuit. (Assume:  $\lambda \neq 0$  for both  $M_1$  and  $M_2$  and both are in saturation.)



 
Gate and Source are fixed. Therefore this NFET works as a constant current source with an impedance  $r_{o2}$  across its drain and source



$$\Rightarrow \frac{V_X}{I_X} = r_{o2} + r_{o1} + r_{o1} (g_{m1} r_{o2} + g_{mb1} r_{o2}) = R_{out}$$
 
## Biasing using Single Power Supply

- The general form of a **single-supply** MOSFET amplifier biasing circuit is:



- We typically attempt to satisfy three main bias design goals:

### 1) Maximize Gain

Typically, the small-signal **voltage gain** of a MOSFET amplifier will be proportional to transconductance  $g_m$ .

$$A_v \propto g_m$$

Thus, to maximize the amplifier voltage gain, we must **maximize** the MOSFET transconductance.

**Q:** What does this have to do with **D.C. biasing**?

**A:** Recall that the transconductance depends on the **DC excess gate voltage**:

$$g_m = 2K(V_{GS} - V_T)$$

- Another way to consider transconductance is to express it in terms of DC drain current  $I_D$ .

## Biasing using Single Power Supply (contd.)

- Recall this DC current is related to the DC excess gate voltage (in saturation!) as:

$$I_D = K(V_{GS} - V_T)^2 \quad \Rightarrow \quad (V_{GS} - V_T) = \sqrt{\frac{I_D}{K}}$$

- And so transconductance can be alternatively expressed as:

$$g_m = 2K(V_{GS} - V_T) = 2K\sqrt{\frac{I_D}{K}} = 2\sqrt{KI_D}$$

- Therefore, the amplifier voltage gain is typically **proportional** to the square-root of the DC drain current:

$$A_v \propto \sqrt{I_D}$$

To maximize  $A_v$ , maximize  $I_D$

## 2) Maximize Voltage Swing

Recall that if the DC drain voltage  $V_D$  is biased too close to  $V_{DD}$ , then even a small **small-signal** drain voltage  $v_d(t)$  can result in a **total** drain voltage that is too **large**, i.e.:

$$v_D(t) = V_D + v_d(t) \geq V_{DD}$$

In other words, the MOSFET enters **cutoff**, and the result is a **distorted** signal!

## Biasing using Single Power Supply (contd.)

- To avoid this (to allow  $v_d(t)$  to be as large as possible without MOSFET entering cutoff), we need to bias our MOSFET such that the DC drain voltage  $V_D$  is as **small** as possible.
- Note that the drain voltage is:  $V_D = V_{DD} - R_D I_D$
- Therefore  $V_D$  is minimized by designing the bias circuit such that the DC drain current  $I_D$  is as **large** as possible.
- However, we must **also** consider the signal distortion that occurs when the MOSFET enters **triode**. This of course is avoided if the total drain-to-source voltage remains greater than the excess gate voltage, i.e.:

$$v_{DS}(t) = V_{DS} + v_{ds}(t) > (V_{GS} - V_T)$$

- Thus, to avoid the MOSFET triode mode—and the resulting signal distortion—we need to bias our MOSFET such that the DC voltage is as **large** as possible.


To minimize signal distortion, maximize  $V_{DS}$

## Biasing using Single Power Supply (contd.)

### 3) Minimize Sensitivity to changes in $K, V_T$

- We find that MOSFETs are **sensitive** to temperature—specifically, the value of  $K$  is a function of temperature.
- Likewise, the values of  $K$  and  $V_T$  are not particularly constant with regard to the manufacturing process.
- Both of these facts lead to the requirement that our bias design be **insensitive** to the values of  $K$  and  $V_T$ . Specifically, we want to design the bias network such that the DC bias current does **not** change values when  $K$  and/or  $V_T$  does.
- **Mathematically**, we can express this requirement as minimizing the value:  $\frac{dI_D}{dK}$  and  $\frac{dI_D}{dV_T}$
- These derivatives can be minimized by maximizing the value of **source resistor  $R_S$** .
- So, let's **recap** what we have learned about designing our bias network:
  1. Make  $I_D$  as large as possible.
  2. Make  $V_{DS}$  as large as possible.
  3. Make  $R_S$  as large as possible.
 
## Biasing using Single Power Supply (contd.)



$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

or


$$I_D R_D + V_{DS} + I_D R_S = V_{DD}$$

Maximize  $A_v$  by **maximizing** this term.


Minimize distortion by **maximizing** this term.

Minimize sensitivity by **maximizing** this term.

 But the **total** of the three terms must equal this!




## Example – 1

 

- If the MOSFET has device values  $K = 1.0 \text{ mA}/V^2$  and  $V_T = 1.0V$ , determine the resistor values to bias this MOSFET with a DC drain current of  $I_D = 4.0mA$ .

## The MOSFET Current Mirror

- Consider the following MOSFET circuit:

 

- Note  $V_D = V_G$ , therefore:  $V_{DS} = V_{GS}$

- and thus:  $V_{DS} > V_{GS} - V_T$

- The MOSFET is in saturation if  $V_G > V_T$ .

- We know that for a MOSFET in saturation, the drain current is:  $V_{DS} = V_{GS}$

Say we want this current  $I_D$  to be a **specific** value—call it  $I_{ref}$ .

- Since  $V_S = 0$ , we find that from the above equation, the drain voltage must be:

$$V_D = \sqrt{\frac{I_{ref}}{K}} + V_T$$

- Likewise, from KVL we find that:

$$I_{ref} = \frac{V_{DD} - V_D}{R}$$

- And thus the **resistor** value to achieve the desired drain current  $I_{ref}$  is:

$$R = \frac{V_{DD} - V_D}{I_{ref}}$$

## The MOSFET Current Mirror (contd.)

**Q:** Why are we doing this?

**A:** Say we now add another component to the circuit, with a second MOSFET that is **identical** to the first :

**Q:** So what is current  $I_L$ ?


**A:** Note that the gate voltage of each MOSFET is the **same** (i.e.,  $V_{GS1} = V_{GS2}$ ), and if the MOSFETS are the **same** (i.e.,  $K_1 = K_2, V_{T1} = V_{T2}$ ), and if the second MOSFET is likewise in **saturation**.

$$\begin{aligned}
 I_L &= K_2 (V_{GS2} - V_{T2})^2 \\
 &= K_1 (V_{GS1} - V_{T1})^2 = I_{ref}
 \end{aligned}$$

• The drain current  $I_L$  is:

Therefore, the drain current of the **second** MOSFET is **equal** to the current of the **first**!

  $I_{ref} = I_L$

 


## The MOSFET Current Mirror (contd.)

**Q:** Wait a minute! You mean to say that the current through the resistor  $R_L$  is **independent** of the value of resistor  $R_L$ ?

**A:** Absolutely! As long as the second MOSFET is in **saturation**, the current through  $R_L$  is equal to  $I_{ref}$ —**period**.

 - The current through  $R_L$  is independent of the value of  $R_L$  (provided that the MOSFET remains in saturation). Think about what this means—this device is a **current source** !



- Remember, the second MOSFET **must** be in saturation for the current through  $R_L$  to be a constant value  $I_{ref}$ . As a result, we find that:

$$V_{DS2} > V_{GS2} - V_{T2}$$

- For this example:  $V_{D2} > V_{G2} - V_{T2}$


## The MOSFET Current Mirror (contd.)

- Since  $V_{D2} = V_{DD} - R_L I_{ref}$ , we find that the MOSFET will be in saturation if:

$$V_{DD} - R_L I_{ref} > V_{G2} - V_{T2} = V_{G1} - V_{T1}$$

- Alternatively, we find the limitation on the load resistor  $R_L$ :
 
$$R_L < \frac{V_{DD} - V_{G1} + V_{T1}}{I_{ref}}$$



- We know that:  $V_{G1} = V_{DD} - R I_{ref}$


- Thus we can alternatively write the above equation as:

$$R_L < R + \frac{V_{T1}}{I_{ref}}$$

- If the **load** resistor becomes **larger** than  $R + \frac{V_{T1}}{I_{ref}}$ , the voltage  $V_{DS2}$  will drop **below** the excess gate voltage  $V_{GS2} - V_{T2}$ , and thus the second MOSFET will enter the **triode** region. As a result, the drain current will **not** equal  $I_{ref}$ —the current source will **stop working!**
 
## The MOSFET Current Mirror (contd.)

Although the circuit is sometimes referred to as a current sink, understand that the circuit is clearly a way of designing a current source.




- We can also use **PMOS** devices to construct a current mirror!
 
## MOSFET Biasing using Current Mirror

- We can bias a MOSFET amplifier using a **current source** as:


It is evident that the DC drain current  $I_D$ , is equal to the current source  $I$ , **regardless** of the MOSFET values  $K$  or  $V_T$ !



Thus, this bias design maximizes drain current **stability**!
 
## MOSFET Biasing using Current Mirror (contd.)

- We now know how to implement this bias design with MOSFETs—we use the **current mirror** to construct the current source!



- Since  $I_D = I$ , it is evident that  $V_{GS}$  **must** be equal to:

$$V_{GS} = \sqrt{\frac{I}{K}} + V_T$$

- Since the DC **gate** voltage is:

$$V_G = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right)$$

- Therefore:

$$\begin{aligned} V_S &= V_G - V_{GS} \\ &= V_{DD} \left( \frac{R_2}{R_1 + R_2} \right) - \left( \sqrt{\frac{I}{K}} + V_T \right) \end{aligned}$$

## MOSFET Biasing using Current Mirror (contd.)

- Since we are biasing with a current source, we do **not** need to worry about drain current **stability**—the current source will determine the DC drain current for **all** conditions (i.e.,  $I_D = I$ ).
- We might conclude, therefore, that we should make DC source voltage  $V_S$  as **small** as possible. After all, this would allow us to **maximize** the output voltage swing (i.e., maximize  $I_D R_D$  and  $V_{DS}$ ).
- Note however, that the **source** voltage  $V_S$  of the MOSFET is numerically equal to the **drain** voltage  $V_{D2}$  (and thus  $V_{DS2}$ ) of the second MOSFET of the **current mirror**.

**Q:** So what?!


**A:** The voltage must be **greater** than:

$$V_{GS2} - V_{T2} = V_{GS1} - V_{T1} \\ = (V_{DD} - I_{ref} R) - V_{T1}$$

in order for the **second** MOSFET to remain in **saturation**.

There is a **minimum voltage** across the current source in order for the current source to properly operate!
 
## MOSFET Biasing using Current Mirror (contd.)



- Thus, to maximize output swing, we **might** wish to set:

$$V_S = V_{GS1} - V_{T1}$$

(although to be practical, we should make  $V_S$  **slightly greater** than this to allow for some design **margin**).

**Q:** How do we “set” the DC **source** voltage  $V_S$ ??

**A:** By setting the DC **gate** voltage  $V_G$ !!

- Recall that the DC voltage  $V_{GS}$  is determined by the DC current source value  $I$ :

$$V_{GS} = \sqrt{\frac{I}{K}} + V_T$$

- and the DC gate voltage is determined by the **two** resistors  $R_1$  and  $R_2$ :

$$V_G = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right)$$

- Thus, we should **select** these resistors such that:

$$\begin{aligned} V_G &= V_{GS} + V_S \\ &= \left( \sqrt{\frac{I}{K}} + V_T \right) + (V_{GS1} - V_{T1}) \end{aligned}$$

## MOSFET Biasing using Current Mirror (contd.)

**Q:** So what should the value of resistor  $R_D$  be?

**A:** Recall that we should set the DC **drain** voltage  $V_D$  :

a) much **less** than  $V_{DD}$  to avoid **cutoff**.

b) much **greater** than  $V_G - V_T$  to avoid **triode**.

- Thus, we **compromise** by setting the DC drain voltage to a point **halfway** in between!


$$V_D = \frac{V_{DD} + (V_G - V_T)}{2}$$

- To achieve this, we must select the drain **resistor**  $R_D$  so that:

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{V_{DD} - (V_G - V_T)}{I_D}$$
 
## Example – 2

Let's determine the proper resistor values to DC bias this MOSFET. The current source is 5.0 mA and has a minimum voltage of 2.0 Volts in order to operate properly



- Since  $I = I_D = 5 \text{ mA}$ , we know that the value of  $V_{GS}$  should be:

$$\begin{aligned}
 V_{GS} &= \sqrt{\frac{I}{K}} + V_T \\
 &= \sqrt{\frac{5.0}{0.2}} + 1.0 \\
 &= 6.0 \text{ V}
 \end{aligned}$$

- Assuming that we want the DC source voltage to be the minimum value of  $V_S = 2.0 \text{ V}$ , we need for the DC gate voltage to be:

$$\begin{aligned}
 V_G &= V_{GS} + V_S \\
 &= 6.0 + 2.0 \\
 &= 8.0 \text{ V}
 \end{aligned}$$

## Example – 2 (contd.)

- Thus, we need to select resistors  $R_1$  and  $R_2$  so that:  $V_G = 8.0 = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right)$
- or in other words, we want:  $\left( \frac{R_2}{R_1 + R_2} \right) = \frac{8.0}{15.0}$
- Since we can make  $R_1$  and  $R_2$  large, let's assume that we want:  $R_1 + R_2 = 300K$

So that  $R_1 = 140 k\Omega$  and  $R_2 = 160 k\Omega$ .

- Finally, we want the DC drain voltage to be:  $V_D = \frac{V_{DD} + (V_G - V_T)}{2}$   
 $= \frac{15.0 + (8.0 - 1.0)}{2}$   
 $= 11.0V$
- So that the resistor is:  $R_D = \frac{V_{DD} - V_D}{I_D}$   
 $= \frac{15.0 - 11.0}{5.0}$   
 $= 0.8 K\Omega$

## Example – 2 (contd.)

