




Lecture – 8

Date: 05.09.2016

- CS Amplifier with Constant Current Source
- Current Steering Circuits
- CS Stage Followed by CG Stage
- Cascode as Current Source
- Cascode as Amplifier

 CS Amplifier with Constant Current Source



Transistors Q_2 , Q_3 , and Q_4 form the **current mirror** that acts as the **current source**. Note that transistor Q_4 is an **enhancement load**—it acts as the **resistor** in the current mirror circuit.

The important thing to realize when analyzing **this** circuit is that the gate-to-source voltage for transistors Q_2 , Q_3 , and Q_4 are **DC values!**

??

source resistance r_o of this current source → requires the **small-signal analysis** → there are **four** (count em') transistors in this circuit, determining the small-signal circuit must **take forever!** → the answer is actually a **NO.**

A: In other words, the small signal voltages v_{gs} for each transistor are equal to **zero**:

$$V_{gs2} = V_{gs3} = V_{gs4} = 0$$

CS Amplifier with Constant Current Source (contd.)


Q: But doesn't the small-signal source $v_i(t)$ **create** small-signal voltages and currents **throughout** the amplifier?

A: For **some** of the circuit yes, but for **most** of the circuit no!

Note that for transistor Q_1 there will be **small-signal** voltages $v_{gs1}(t)$ and $v_{ds1}(t)$, along with $i_{d1}(t)$. Likewise for transistor Q_2 , a **small-signal** voltage $v_{ds2}(t)$ and current $i_{d2}(t)$ will occur.

But, for the remainder of the voltages and currents in this circuit (e.g., V_{DS4} , V_{GS2} , I_{D3}), the small-signal component is **zero**!

 CS Amplifier with Constant Current Source (contd.)



Q: But wait! **How** can there be a small-signal **drain current** $i_{d2}(t)$ through transistor Q_2 , **without** a corresponding small-signal $v_{gs2}(t)$ **gate-to-source voltage**?


A: Transistor Q_2 is **the** important device in this analysis.

- Note its gate-to-source voltage is a **DC value** (no small-signal component, $v_{gs2}(t) = 0$), yet there **must** be (by KCL) a **small-signal** drain current!
- This is a case where we **must** consider the **MOSFET output resistance** r_{o2} . The small-signal drain current for a **PMOS** device is:


$$i_{d2} = g_{m2} v_{gs2} - \frac{v_{ds2}}{r_{o2}}$$
- Since $v_{gs2} = 0$, this equation **simplifies** to: $i_{d2} = -\frac{v_{ds2}}{r_{o2}}$

CS Amplifier with Constant Current Source (contd.)

 
- Equivalently, the **small-signal PMOS model** is:



 
- Thus for $v_{gs2} = 0$, the small-signal model becomes:



 - Thus, the small-signal model of the entire current mirror is simply the output resistance of the MOSFET Q_2 !




- Or, simplifying further:

 


CS Amplifier with Constant Current Source (contd.)

It is evident that the output resistance of the current mirror is simply equal to the output resistance of MOSFET Q_2 !!!!


$$r_o = r_{o2}$$

 

is equivalent to
this circuit

 

 - The resulting small-signal circuit of this amp is:



- the small signal **voltage gain** is:

$$A_v = -g_{m1} r_{o1} || r_{o2} = 2\sqrt{K_1} \sqrt{I_{ref}} r_{o1} || r_{o2}$$


CS Amplifier with Constant Current Source (contd.)

- Note **this** result is **far different** (i.e., larger) than the result when using the **enhancement load** for R_D :
- However, we find that the **output** and **input** resistances of this amplifier are the **same** as with the enhancement load:
- A current mirror may consist of **many** MOSFET current sources!

$$A_v = -\sqrt{\frac{K_1}{K_2}}$$

$$R_i = \infty$$

$$R_o = r_{o1} \parallel r_{o2}$$

 

This circuit is particularly useful in integrated circuit design, where **one** resistor R is used to make **multiple** current sources.

Q: What if we want to make the sources have **different** current values? Do we need to make **additional** current mirrors?

Current Steering Circuits

A: NO!!

- Recall that the current mirror simply ensures that the gate to source voltages of **each** transistor is **equal** to the gate to source voltage of the **reference**:

$$V_{GS}^{ref} = V_{GS1} = V_{GS2} = V_{GS3} = \dots$$

- Therefore, **if** each transistor is identical (i.e., $K_{ref} = K_1 = \dots$, and $V_T^{ref} = V_{T1} = V_{T2} = \dots$) then:

$$\begin{aligned} I_{ref} &= K_{ref} (V_{GS}^{ref} - V_T^{ref})^2 \\ &= K_n (V_{GSn} - V_{Tn})^2 = I_{Dn} \end{aligned}$$

In other words, **if** each transistor Q_n is **identical** to Q_{ref} , then each current I_{Dn} will **equal** reference current I_{ref} .

- But**, consider what happens if the MOSFETS are not identical. Specifically, consider the case where $K_n \neq K_{ref}$ (but $V_{Tn} = (V_T)^{Ref}$).


- In such a scenario the drain current I_{Dn} will now be:

$$\begin{aligned} I_{Dn} &= K_n (V_{GSn} - V_{Tn})^2 = K_n (V_{GS}^{ref} - V_T^{ref})^2 \\ &= K_n \left(\frac{I_{ref}}{K_{ref}} \right) = \left(\frac{K_n}{K_{ref}} \right) I_{ref} \end{aligned}$$

The drain current is a scaled value of I_{ref} !

Current Steering Circuits (contd.)

 For example, if K_1 is twice that of K_{ref} (i.e., $K_1 = 2K_{ref}$), then I_{D1} will be twice as large as I_{ref} (i.e., $I_{D1} = 2I_{ref}$).




$$\frac{K_n}{K_{ref}} = \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_{ref}}$$

From the standpoint of integrated circuit design, we can change the value of K by modifying the MOSFET channel **width-to-length ratio** (W/L) for each transistor.

 Example-1

- Determine all the currents in the following and find the value of R



$$I_{D2} = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$

$$= 25\ \mu\text{A} * \frac{10/1}{5/1} = 50\ \mu\text{A}$$

$$I_{D3} = I_{REF} \frac{(W/L)_3}{(W/L)_1} = 125\ \mu\text{A}$$

$$I_{D4} = I_{REF} = 25\ \mu\text{A}$$

$$I_{D5} = I_{D4} \frac{(W/L)_5}{(W/L)_4} = 25\ \mu\text{A}$$

Example-1 (contd.)


$$R = \frac{+5 - (-V_{GSP}) - V_{GSN} - (-5)}{I_{REF}}$$

$$\Rightarrow R = \frac{10 + V_{GSP} - V_{GSN}}{I_{REF}}$$

$$V_{GSP} = V_{TP} - \sqrt{\frac{2I_{D4}}{\mu_p C_{ox} (W/L)_4}}$$


$$V_{GSN} = V_{TN} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} (W/L)_1}}$$

 - The resistor R can be replaced by an active load such as the PFET shown here → what will be its W/L?



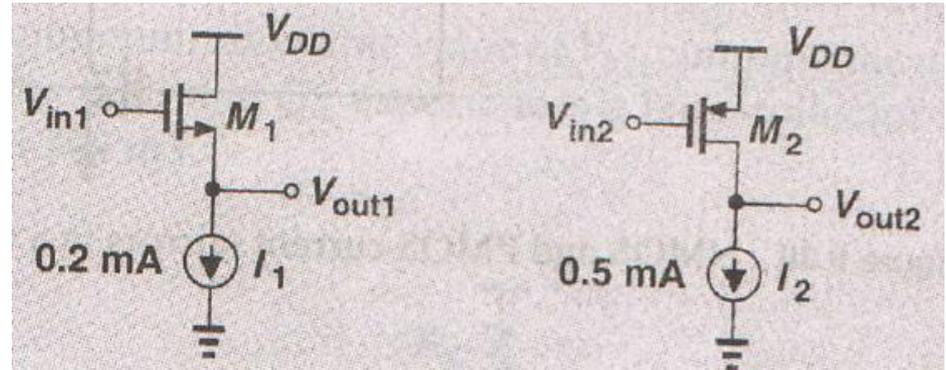Example-2


- An integrated circuit employs the following CD and CS stages. Design an NMOS type current mirror that produces I_1 and I_2 from a 0.8mA reference.




- Required current for CD stage is 0.2 mA, hence mirror equation gives:

$$\frac{I_{DMI1}}{I_{REF}} = \frac{(W/L)_{MI1}}{(W/L)_{REF}} \Rightarrow \frac{0.2}{0.8} = \frac{(W/L)_{MI1}}{(W/L)_{REF}} \rightarrow \text{They are in the ratio of 2 to 8}$$

 - Similarly, for CS stage the ratio is 5 to 8



Common Gate Stage

 

$$\therefore R_{in} = \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o} \approx \frac{R_D}{(g_m + g_{mb})r_o} + \frac{1}{(g_m + g_{mb})}$$


- **Case-I:** $R_D = 0$

$$R_{in} = \frac{V_X}{I_X} = \frac{r_o}{1 + (g_m + g_{mb})r_o}$$

- **Case-II:** R_D is an ideal current source ie, $R_D \rightarrow \infty$


$$R_{in} \rightarrow \infty$$

 the input impedance of common-gate stage is low only if the load impedance connected to the drain is low



$$R_{out} = \frac{V_X}{I_X} = \left\{ [1 + (g_m + g_{mb})r_o] R_S + r_o \right\} \parallel R_D$$

CS-stage followed by a CG-stage

 

- Use the CG stage expression to obtain the small signal voltage gain as:



$$\frac{V_{out}}{V_{in}} = A_v = \frac{(g_{m2} + g_{mb2})r_{o2} + 1}{r_{o2} + \left[1 + (g_{m2} + g_{mb2})r_{o2} \left(r_{o1} \parallel \frac{1}{g_{mb1}} \parallel \frac{1}{g_{m1}} \right) \right] + R_D} R_D \frac{r_{o1} \parallel \frac{1}{g_{mb1}}}{r_{o1} \parallel \frac{1}{g_{mb1}} + \frac{1}{g_{m2}}}$$

significantly larger gain when compared to CS stage

  Example – 3

The CS-stage in both the following circuits senses ΔV at node X and delivers a proportional current to a 50Ω transmission line.

- Calculate small signal gain at low frequencies.
- What condition is necessary to minimize wave reflections at node X




Cascode Stage

- **Terminology:** It stems from erstwhile vacuum tube in which cathodes were cascaded. In practice, the output of first tube (anode) feeds the input of second tube (cathode)
- **Configuration:** CG-stage in cascade with CS-stage → **actually CS-stage is called the main device** whereas CG is called the cascode device
- **Basic Idea:** **combines high input impedance** and large transconductance of CS **with the current buffering property** and the superior high frequency response of CG stage
- **Cascode Provides:** **wider bandwidth, increased small-signal gain,** high input impedance, **customized output impedance**
- **Applications:** Current Source, Small-Signal Amplifier


Cascode – as a current source

 - Current Source: requires very high output impedance



Cascode Transistor (CG Stage): always in saturation and is the main device that provides a constant current source

 Degeneration Transistor (CS Stage): in saturation and acts as a degeneration resistor for a fixed bias point → provides an impedance of r_{o2}



KVL in loop-1

$$V_1 = -I_X r_{o2}$$

KVL in loop-2

$$V_X = I_X r_{o2} + (I_X - g_{m1} V_1 - g_{mb1} V_1) r_{o1}$$

$$\Rightarrow \frac{V_X}{I_X}$$

$$= r_{o2} + r_{o1} + r_{o1} (g_{m1} r_{o2} + g_{mb1} r_{o2}) = R_{out}$$

Cascode – as a current source

$$\Rightarrow R_{out} = r_{o2} + r_{o1} + r_{o1}(g_{m1}r_{o2} + g_{mb1}r_{o2}) = r_{o2} + r_{o1}[1 + r_{o2}(g_{m1} + g_{mb1})]$$

$$R_{out} = r_{o1} + r_{o2}[1 + r_{o1}(g_{m1} + g_{mb1})]$$

However: $r_{o1}(g_{m1} + g_{mb1}) \gg 1$

$$r_{o1}(g_{m1}r_{o2} + g_{mb1}r_{o2}) \gg r_{o1}$$

$$\therefore R_{out} \approx (g_{m1} + g_{mb1})r_{o1}r_{o2}$$

Very High Output Impedance




M_1 already in saturation



Appropriate candidate for constant current source

In this case, M_1 boosts the output resistance of M_2 by a factor of $(g_{m1} + g_{mb1})r_{o1}$

Cascode – Amplifier

 

Cascode device (in CG) → in saturation → routes the current generated by main device to R_D


main device (in CS) → in saturation → converts and amplifies an input voltage signal into output current

Bias Conditions of Cascode:

- For M_1 to be in saturation: $V_X > V_{in} - V_{T1}$
 $\Rightarrow V_b - V_{GS2} > V_{in} - V_{T1} \quad \Rightarrow V_b > V_{in} + V_{GS2} - V_{T1}$
- For M_2 to be in saturation: $V_{out} - V_X \geq V_{GS2} - V_{T2}$

$$\Rightarrow V_{out} \geq \underbrace{V_{in} - V_{T1}}_{V_{OV1}} + \underbrace{V_{GS2} - V_{T2}}_{V_{OV2}}$$


 
Minimum output voltage equals overdrive voltage of M_1 and M_2 → addition of M_2 reduces the output voltage swing by $V_{GS2} - V_{T2}$




Cascode – Amplifier (contd.)

It is a CS stage and therefore generates:

$$V_X = -g_{m1}r_{o1}V_{in}$$

  

Small Signal Model of Cascode:

 

Cascode – Amplifier (contd.)

Simplification
gives:

$$\frac{V_{out}}{R_D} [R_D + r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o1}r_{o2}] = -[g_{m1}(g_{m2} + g_{mb2})r_{o1}r_{o2} + g_{m1}r_{o1}]V_{in}$$


$$\Rightarrow \frac{V_{out}}{V_{in}} = A_v = -\frac{[g_{m1}(g_{m2} + g_{mb2})r_{o1}r_{o2} + g_{m1}r_{o1}]}{[R_D + r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o1}r_{o2}]} R_D$$

Now: $g_{m1}(g_{m2} + g_{mb2})r_{o1}r_{o2} \gg g_{m1}r_{o1}$




$$\therefore A_v \approx -\frac{g_{m1}(g_{m2} + g_{mb2})r_{o1}r_{o2}}{[R_D + r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o1}r_{o2}]} R_D$$

 Output Impedance: ability to synthesize desired output impedance



$$R_{out} \approx (g_{m2} + g_{mb2})r_{o2}r_{o1}$$

Cascode – Amplifier (contd.)

 

the gain of
Cascode stage:

$$\Rightarrow A_v \approx - \frac{g_{m1}(g_{m2} + g_{mb2})r_{o1}r_{o2}}{[R_D + r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o1}r_{o2}]} R_D$$

A constant current source possesses very high output impedance ($R_D \rightarrow \infty$), therefore the gain equation changes to:

$$A_v \approx -g_{m1}(g_{m2} + g_{mb2})r_{o1}r_{o2} = -(g_{m1}r_{o1}) \cdot (g_{m2} + g_{mb2})r_{o2}$$


It is apparent that the maximum small-signal voltage gain is the multiplication of gains from CS and CG stages \rightarrow definitely a big plus!

$$R_{out} \approx (g_{m2} + g_{mb2})r_{o2}r_{o1}$$

Cascode – Amplifier (contd.)

Discussion with respect to alteration in dimension

 
What happens if Length (L) of the main device is quadrupled while the Width (W) remains same



$$A_v \approx -g_m r_o = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \frac{1}{\lambda I_D}$$


$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$
 
$$(V_{GS} - V_{TH})^2 = \frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}$$



$$A_{v1} = 2A_v$$

$$g_{m1} = \frac{g_m}{2}$$

 

$$A_{v2} = (A_v)^2$$

$$g_{m2} = g_m$$

Cascode more suited for noise applications


Quadruppling of Length (L) while keeping the Width (W) results in doubling of overdrive voltage

For **identical devices**, cascode also exhibits doubling of overdrive voltage

Shielding Property of Cascode

Cascode amplifier and Cascode current source → could be used in applications where the output varies drastically due to any reason! → This variation doesn't affect the subsequent sections greatly → shielding property of Cascode

 Example: Two identical NFETs are used to generate constant current sources. However, due to internal circuitry of the system, V_X is higher than V_Y by ΔV .



Q: determine the resulting difference between I_{D1} and I_{D2} if $\lambda \neq 0$


$$I_{D1} = \frac{1}{2} \mu_n C_{ox} (V_b - V_T)^2 (1 + \lambda V_{DS1})$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} (V_b - V_T)^2 (1 + \lambda V_{DS2})$$

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} (V_b - V_T)^2 (\lambda \Delta V)$$

Shielding Property of Cascode (contd.)

 Q: Add Cascode devices to M1 and M2 and then check the difference between I_{D1} and I_{D2} if $\lambda \neq 0$



Cascode devices

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} (V_b - V_T)^2 (\lambda \Delta V_{PQ})$$


$$\Delta V_{PQ} = \Delta V \frac{r_{o1}}{[1 + (g_{m3} + g_{mb3})r_{o3}]r_{o1} + r_{o3}} \approx \frac{\Delta V}{(g_{m3} + g_{mb3})r_{o3}}$$

$$\therefore I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} (V_b - V_T)^2 \left(\frac{\lambda \Delta V}{(g_{m3} + g_{mb3})r_{o3}} \right)$$

This is a large value and thus the Cascode structure gives smaller variation → perfect example of Shielding property!!!

Triple Cascode

 - Cascoding can be extended to **three or more devices** to achieve higher output impedance



It limits the voltage swing

Here the minimum output voltage equals the sum of three overdrive voltages

Folded Cascode

[Self Study](#)