


Lecture – 9

Date: 08.09.2016

- Non-idealities in Current Mirror
- Cascode Current Mirror
- Current Mirror Configurations
- Examples

Current Mirror

 - Now let us take the generic equations for the following current mirror:



$$I_{REF} = \frac{1}{2} \mu_{n1} C_{ox1} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{T1})^2$$

$$I_{out} = \frac{1}{2} \mu_{n2} C_{ox2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{T2})^2$$

Even if these transistors are identical and have been fabricated on the same chip [thus practically possessing similar parameters such as V_T , μ_n , C_{ox}], there are three effects that causes current mirror to be different from ideal situation

These effects are: (a) Channel Length Modulation, (b) V_T offset between the two transistors, (c) Imperfect Geometrical Matching

Current Mirror (contd.)

Channel Length Modulation Effect

- Assuming all other aspects of the transistor are ideal and the ratio of aspect ratios of both the transistors are unity then:


$$\frac{I_{out}}{I_{REF}} = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$

It is assumed that λ is the same for both M_1 and M_2

It is apparent that the difference in V_{DS} causes deviation from the ideal unity current gain or current mirroring

Current Mirror (contd.)

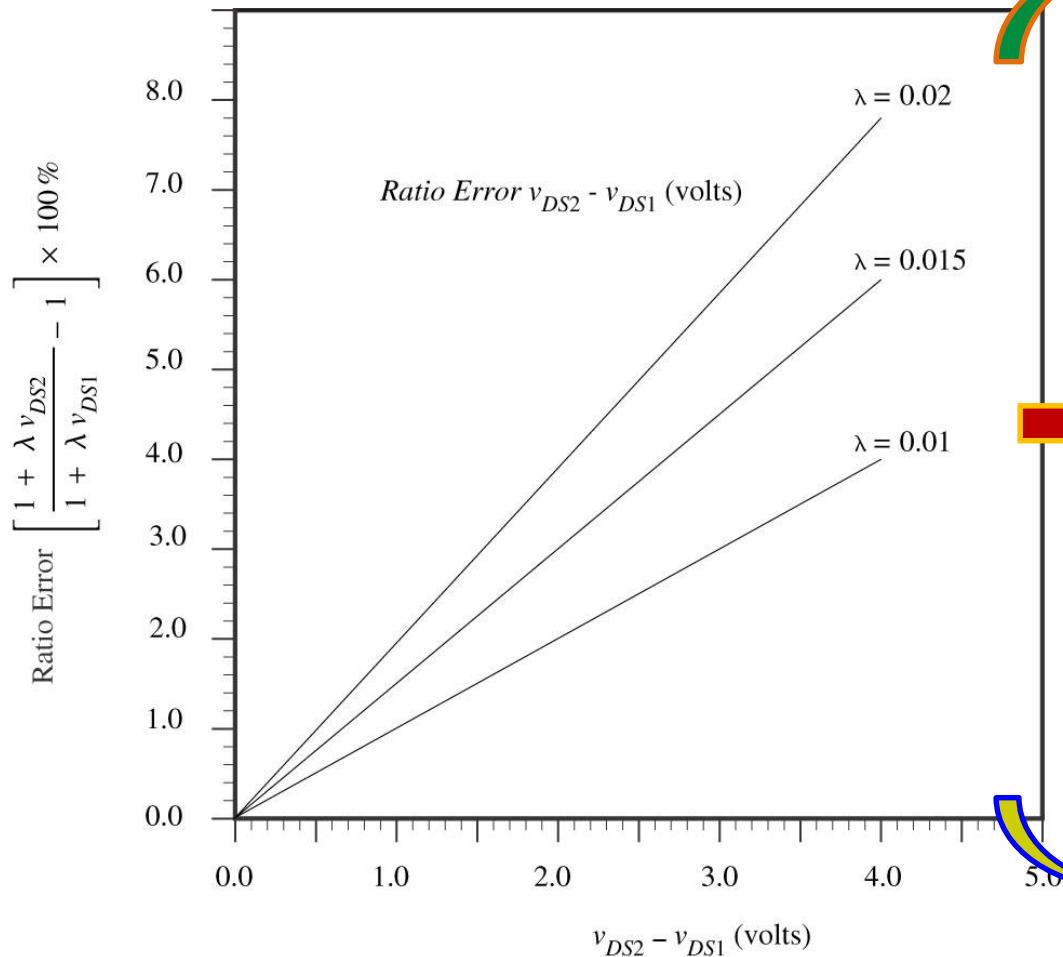Channel Length Modulation Effect (contd.)



Significant Ratio Error can exist when mirror transistors do not have the same V_{DS}

For a given V_{DS} , the ratio improves with decreasing λ (i.e, increasing output resistance)

Therefore, a good current mirror should have identical V_{DS} and high output resistance

Current Mirror (contd.)


Channel Length Modulation Effect (contd.)

- Therefore, the apparent solution seems the use of long channel device
 - however this also requires increase in width → results in problems for area and power constraint designs
 - furthermore, increase in width also increases the output capacitance → high frequency performance suffers
 - short channel devices are commonplace and therefore this solution is not appropriate

Cascode Current Mirror

- In order to overcome the error due to channel length modulation, **instead of a simple two transistor “current mirror”** it is recommended to use “cascode current mirror”

Cascode Stage

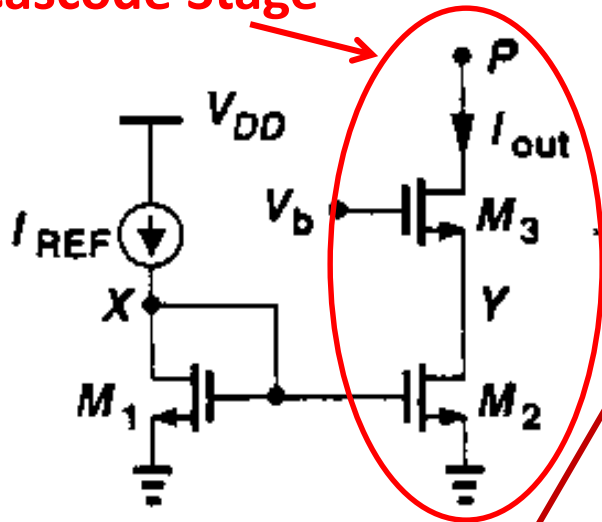

- In this architecture, **small changes in potential at node-P** does not have any effect on the potential at node-Y → **shielding property of Cascode.**
- Through some technique make $V_Y = V_X$ → then the effect of channel length modulation is insignificant as the mirror equation becomes:


$$I_{out} = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$

Once again only dependent on the scaling of devices

$$\Delta V_Y = \Delta V_P / [(g_{m3} + g_{mb3})r_{o3}]$$

Cascode Current Mirror (contd.)

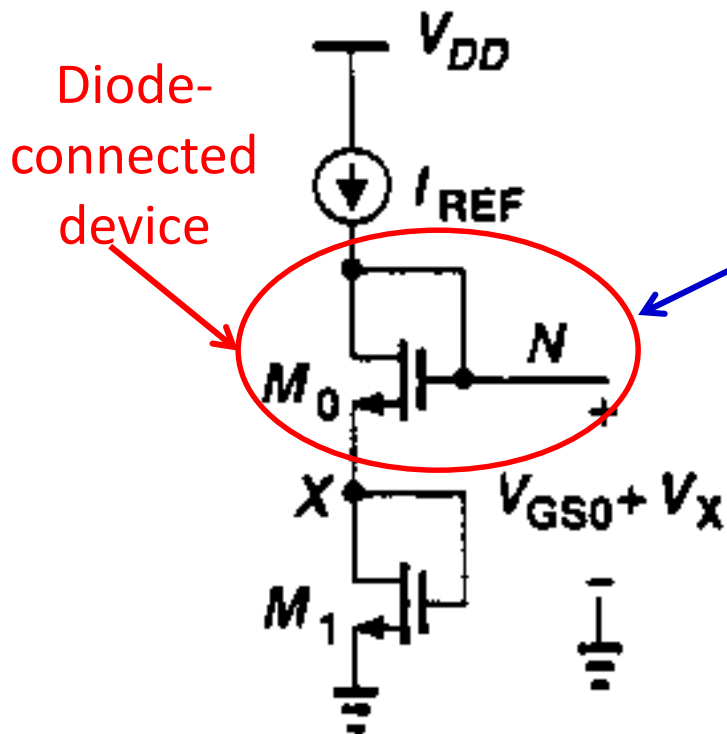- How do we generate the condition: $V_Y = V_X$
- For this to happen, we must guarantee $V_b - V_{GS3} = V_X \rightarrow$ It means one gate-source voltage should be added to achieve this \rightarrow this is easily achieved by placing a diode-connected device M_0 in series with M_1




Addition of this device will ensure fulfillment of:

$$V_b - V_{GS3} = V_X$$


Then proper choice of dimensions of M_0 and M_3 yields $V_{GS0} = V_{GS3}$

Cascode Current Mirror (contd.)

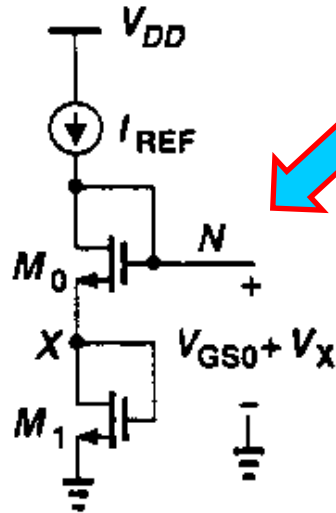

$$V_N = V_{GS0} + V_X$$

 The node N is then connected to the gate of cascode device



$$V_{GS0} + V_X + V_{GS1} = V_{GS3} + V_Y + V_{GS2}$$

$$\therefore V_{GS0} + V_X = V_{GS3} + V_Y$$

proper choice of dimensions of M_0 and M_3 yields $V_{GS0} = V_{GS3}$

- For this to happen: $\frac{(W/L)_3}{(W/L)_0} = \frac{(W/L)_2}{(W/L)_1}$

- Once $V_{GS0} = V_{GS3}$, we get: $V_X = V_Y$

Cascode Current Mirror (contd.)


- $V_X = V_Y$ leads to the condition:
 $V_{DS1} = V_{DS2} \rightarrow$ transforms the mirror equation:

$$I_{out} = I_{REF} \frac{(W/L)_2}{(W/L)_1}$$

Valid even when there exist body effect in transistors M_0 and M_3

- Cascode configuration improves the accuracy of current copying capability \rightarrow but what is the major drawback?
- As the cascode current mirror provides a constant current source, it should also possess very high output impedance

 - Consider once again the following configuration:




← What is R_{out} here?

$$R_{out} \approx g_{m3} r_{o3} r_{o2}$$


Cascode Current Mirror (contd.)

Accuracy and Voltage Swing Trade-off

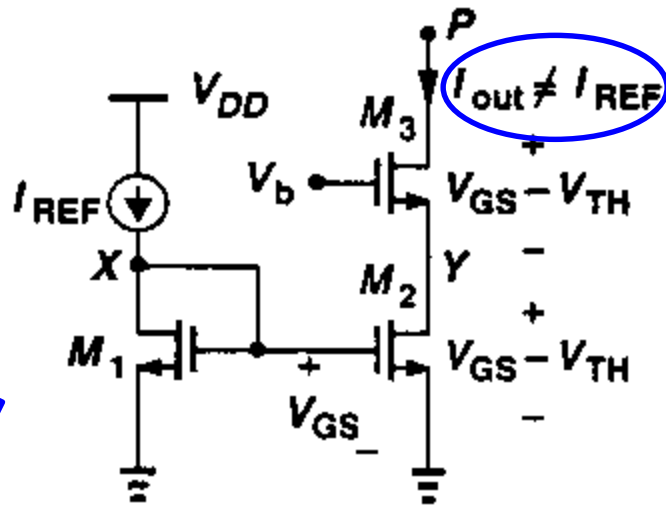

Standard Cascode
Current Mirror

 - V_b is chosen to allow minimum V_p
- Problem: $V_x \neq V_y$
- $I_{out} \neq I_{ref}$



Modified Cascode
Current Mirror

- V_b is chosen to allow $V_x = V_y$
- V_p is not minimum
- However, $I_{out} = I_{ref}$

Current Mirror (contd.)

Threshold Offset Effect


- The offset between the threshold voltage of two transistors also causes problems in the optimal operation of current mirror
- The threshold offset is typically less than 10mV for identical transistors → even this small offset causes substantial error!!!
- Let us now consider a current mirror configuration where both have the same V_{DS} and all other aspects of the transistors are equal except V_T . The expression simplifies to:

$$\frac{I_{out}}{I_{REF}} = \left(\frac{V_{GS} - V_{T2}}{V_{GS} - V_{T1}} \right)^2$$

Current Mirror (contd.)

Threshold Offset Effect (contd.)

 - The plot of ratio error **between ideal and imperfect current mirroring** as a function of $\Delta V_T = V_{T1} - V_{T2}$ results into:



Clearly identifies that better current mirroring is obtained for higher currents

Its due to the fact that V_{GS} is higher for higher currents \rightarrow ensures that ΔV_T is a smaller percentage of V_{GS}

Current Mirror (contd.)

Threshold Offset Effect (contd.)

- Sometimes it may happen that the factor $\mu_n C_{ox}$ (let us call it K') is also mismatched alongwith the offset in the threshold.
- The current mirror equation then transforms to:

$$\frac{I_{out}}{I_{REF}} = \frac{K'_2 (V_{GS} - V_{T2})^2}{K'_1 (V_{GS} - V_{T1})^2}$$

In this case its assumed that the aspect ratio is identical (considering that its designer driven!).

- Let us define:

$$\Delta K' = K'_2 - K'_1 \qquad K' = \frac{1}{2}(K'_2 + K'_1) \qquad V_T = \frac{1}{2}(V_{T1} + V_{T2})$$

- Then:

$$K'_1 = K' - 0.5\Delta K' \qquad K'_2 = K' + 0.5\Delta K' \qquad V_{T1} = V_T - 0.5\Delta V_T \qquad V_{T2} = V_T + 0.5\Delta V_T$$

Current Mirror (contd.)

Threshold Offset Effect (contd.)

- Let us substitute the mirror equation using these assumed parameters:

$$\frac{I_{out}}{I_{REF}} = \frac{(K' + 0.5\Delta K')(V_{GS} - V_T - 0.5\Delta V_T)^2}{(K' - 0.5\Delta K')(V_{GS} - V_T + 0.5\Delta V_T)^2}$$

- Factor out K' and $(V_{GS} - V_T)$ to get:

$$\frac{I_{out}}{I_{REF}} = \frac{\left(1 + \frac{\Delta K'}{2K'}\right) \left(1 - \frac{\Delta V_T}{2(V_{GS} - V_T)}\right)^2}{\left(1 - \frac{\Delta K'}{2K'}\right) \left(1 + \frac{\Delta V_T}{2(V_{GS} - V_T)}\right)^2}$$

- Assuming these quantities to be small, we get:

$$\frac{I_{out}}{I_{REF}} = \left(1 + \frac{\Delta K'}{2K'}\right) \left(1 + \frac{\Delta K'}{2K'}\right) \left(1 - \frac{\Delta V_T}{2(V_{GS} - V_T)}\right)^2 \left(1 - \frac{\Delta V_T}{2(V_{GS} - V_T)}\right)^2$$

Current Mirror (contd.)

Threshold Offset Effect (contd.)

- Retaining only the first order products gives:

$$\frac{I_{out}}{I_{REF}} \cong 1 + \frac{\Delta K'}{K'} - \frac{2\Delta V_T}{V_{GS} - V_T}$$

If the percentage change of K' and V_T are known a priori, then this expression can predict the worst-case error in the current mirroring capability of the current mirror

For example, if : $\frac{\Delta K'}{K'} = \pm 5\%$

and: $\frac{\Delta V_T}{V_{GS} - V_T} = \pm 10\%$

then: $\frac{I_{out}}{I_{REF}} \cong 1 \pm 0.05 \pm (-0.2) = 1 \pm (-0.15)$

In this example, the maximum error amounts to 15% provided the tolerances in K' and V_T are correlated

Current Mirror (contd.)

Mismatch in Aspect Ratio



- mismatches are commonly present even in identical transistors on the same die \leftarrow W and L are often mismatched due to mask, photolithography, and diffusion variations \rightarrow this can be significant even for two transistors placed side by side
- One way to overcome these effects is to make transistors much larger than these variations \rightarrow e.g., for transistors of identical size with W and L greater than $10\mu m$, the errors due to the mismatched aspect ratio will be insignificant \leftarrow when compared to errors contributed by offset V_T and Channel Length Modulation
- However, many applications (for high current gain applications!) require aspect ratio of transistor (M_2) to be much larger than the aspect ratio of the reference transistor (M_1) \leftarrow necessitates creativity in layout techniques !!!

Current Mirror (contd.)

Mismatch in Aspect Ratio (contd.)

  - Example: we see layout of one-to-four current amplifier below. Its assumed that the lengths are identical ($L_1 = L_2$). Find the ratio error if:

$$W_1 = 5 \pm 0.1 \mu m \quad W_2 = 20 \pm 0.1 \mu m$$



$$\frac{I_{out}}{I_{REF}} = \frac{W_2}{W_1} = \frac{20 \pm 0.1}{5 \pm 0.1} = 4 \left(\frac{1 \pm (0.1/20)}{1 \pm (0.1/5)} \right) \approx 4 \left(1 \pm \frac{0.1}{20} \right) \left(1 - \frac{\pm 0.1}{5} \right)$$


$$\Rightarrow \frac{I_{out}}{I_{REF}} = 4 \left(1 \pm \frac{0.1}{20} - \frac{\pm 0.4}{20} \right) \approx 4(1 - (\pm 0.06))$$

It is assumed that variations would have the same sign. In this case it is apparent that the ratio error is 1.5% of the desired current ratio

Current Mirror (contd.)

Mismatch in Aspect Ratio (contd.)

 - For large W , it's a good strategy to have W not much larger than L and to put equal transistors in parallel.
- A solution to this problem is to use appropriate layout technique. For example, use four duplicates of transistor M_1 to achieve one-to-four ratio. This way the tolerance on W_2 is multiplied by the nominal current gain.




$$\frac{I_{out}}{I_{REF}} = \frac{W_2}{W_1} = \frac{4(5 \pm 0.1)}{5 \pm 0.1} = 4$$

Here its assumed that ΔW should be the same for all the transistors


Current Mirror Configurations

 - It is a common practice to design current mirror circuits for high output impedance [for achieving near ideal current source!]
- No less important is the voltage headroom [specially for low voltage applications!!!]



Current Mirror Configurations (contd.)

- Wilson Current Mirror

 

$$V_{out.min} = V_{DSsat,3} + V_{GS2} > V_T + 2V_{Dsat}$$

Headroom is smaller

$$r_{out} \approx r_{o3} \frac{g_{m3}}{g_{m2}} g_{m1} (R_L \parallel r_{o1})$$

High Value

$$\frac{I_{out}}{I_{REF}} = \frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$$


$$\frac{I_{out}}{I_{REF}} = \frac{1 + \lambda V_{DS2}}{1 + \lambda (V_{DS2} + V_{GS3})}$$

R_L is reference current generator impedance

The dependence on V_{DS2}


Current Mirror Configurations (contd.)

- Improved Wilson Current Mirror

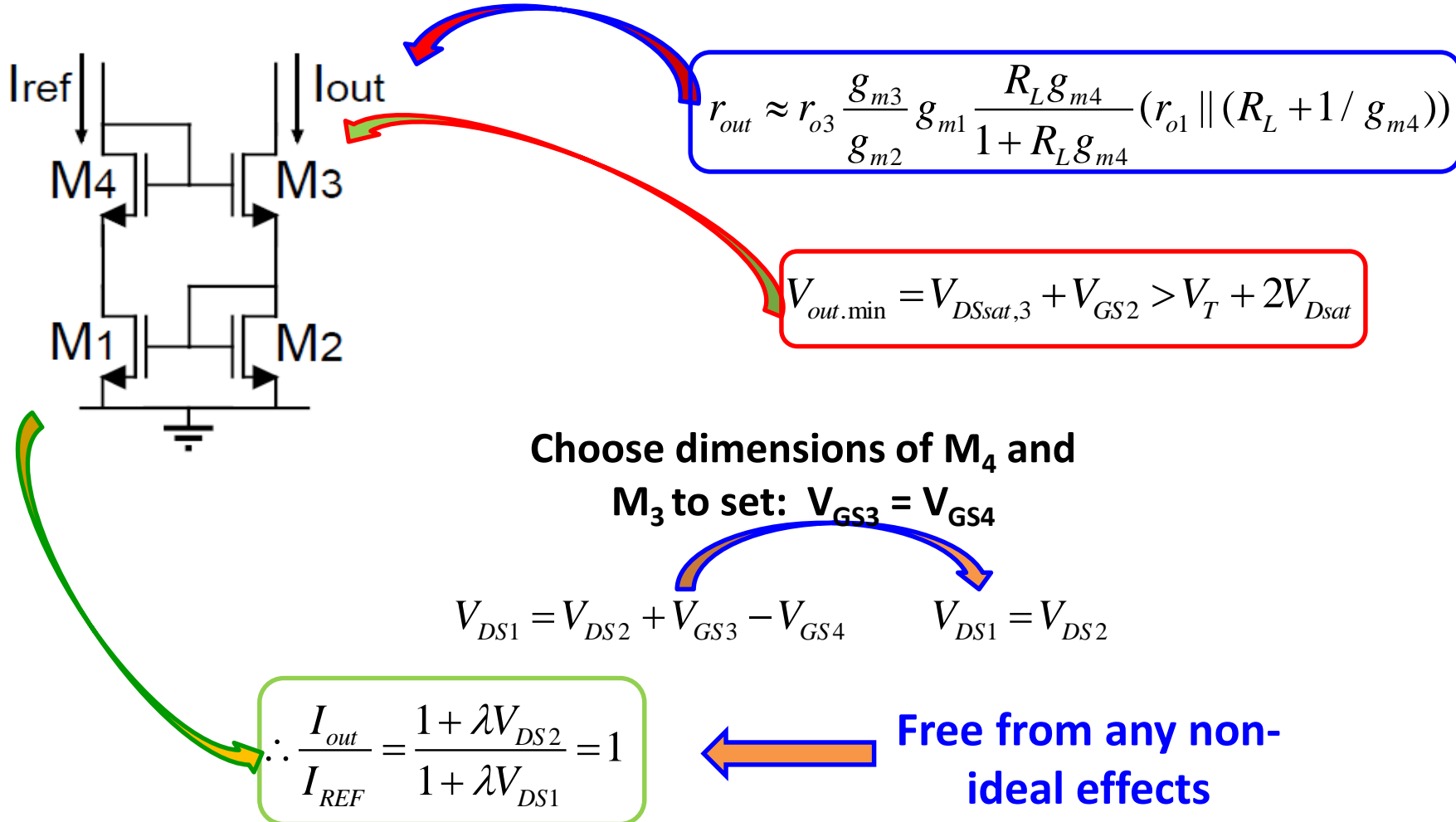

Current Mirror Configurations (contd.)

- Multiple Cascode

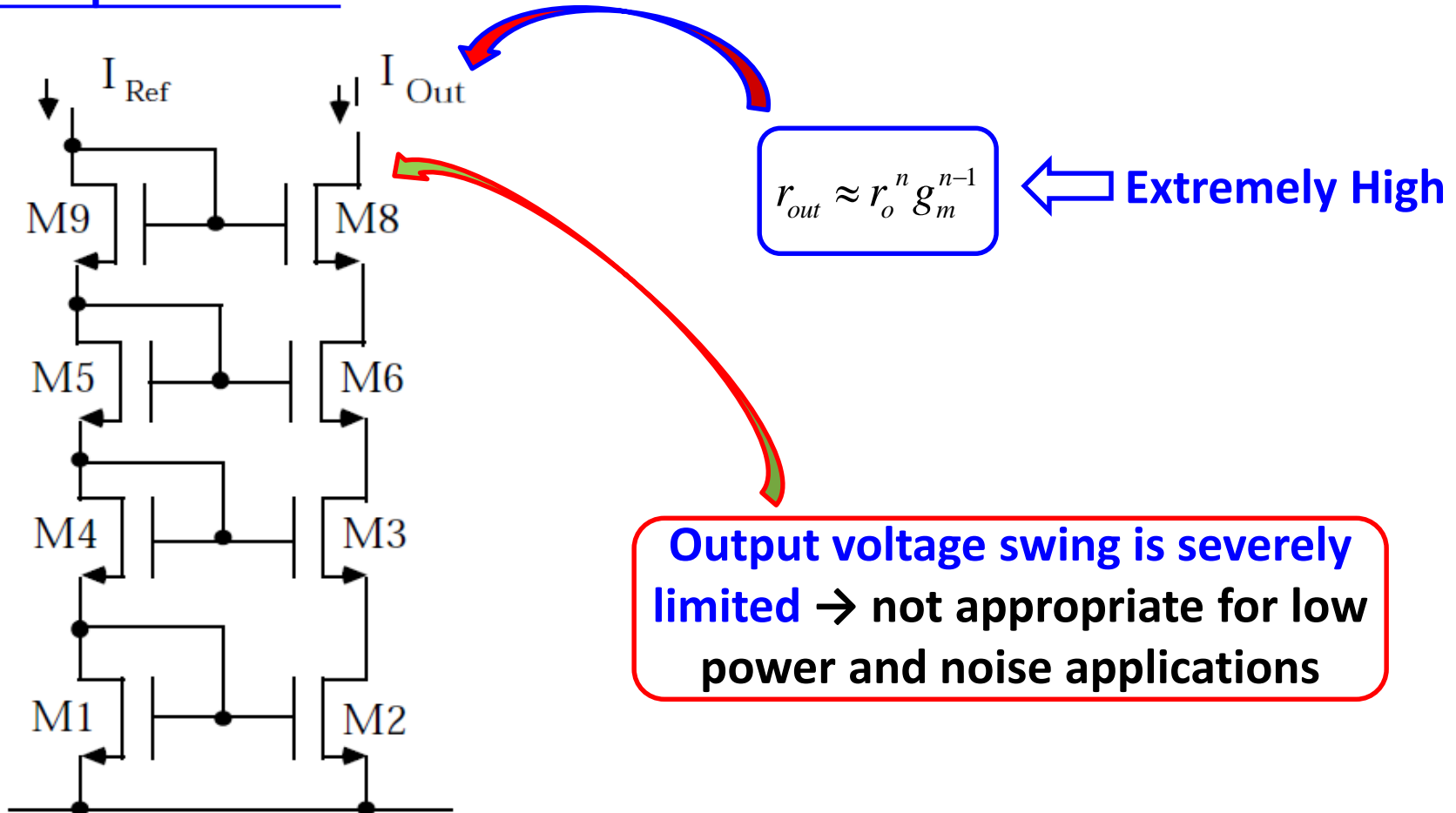


Current Mirror Configurations (contd.)

Configurations	Current Ratio	Output Swing	Output Impedance
Simple	$\frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$	V_{DSsat}	$\frac{1}{g_m} \parallel r_o$
Cascode	1	$2V_{DSsat} + V_T$	$r_o^2 \cdot g_m$
Triple Cascode	1	$3V_{DSsat} + 2V_T$	$r_o^3 \cdot g_m^2$
Wilson	$\frac{1 + \lambda V_{DS2}}{1 + \lambda V_{DS1}}$	$2V_{DSsat} + V_T$	$r_o^2 \cdot g_m$
Improved Wilson	1	$2V_{DSsat} + V_T$	$r_o^2 \cdot g_m$

Example-1

Following figure illustrates a source-degenerated current source. Calculate the output resistance at the given bias current by using the following model parameter: $\mu_n C_{ox} = 110 \mu\text{A}/\text{V}^2$, $\lambda = 0.04$ ($L=1 \mu\text{m}$) or 0.01 ($L=2 \mu\text{m}$) /V, $2|\phi_F|=0.7$, $\gamma=0.4 \text{ V}^{1/2}$

 

Example-1 (contd.)


The dc terminal conditions are:

$$I_D = 10\mu A$$

$$V_S = I_D * R = 10 * 10^{-6} \times 100 * 10^3 = 1V$$

$$V_{SB} = V_S$$

 Now the small signal model of the circuit is:



Simplification gives:

$$r_{out} = \frac{V_{out}}{i_{out}} = r + r_{out} + [(g_m + g_{mbs})r_o]r$$

Can be approximated to:

$$r_{out} = g_m r_o r$$

Example-1 (contd.)

The device parameters can be computed as:

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} \quad \rightarrow \quad g_m = \sqrt{2 \times 110 \times 10^{-6} \times \frac{2}{2} \times 10 \times 10^{-6}} \quad \rightarrow \quad \therefore g_m = 66.3 \times 10^{-6}$$

$$g_{mbs} = g \frac{\gamma}{2(2|\phi_F| + V_{SB})^{1/2}} \quad \rightarrow \quad g_{mbs} = 66.3 \times 10^{-6} \frac{0.4}{2(0.7 + 1)^{1/2}} \quad \rightarrow \quad \therefore g_{mbs} = 10.17 \times 10^{-6}$$


$$r_o = \frac{1}{\lambda I_D} \quad \rightarrow \quad r_o = \frac{1}{0.04 \times 10 \times 10^{-6}} \quad \rightarrow \quad \therefore r_o = 2.5 \times 10^6 \Omega$$

Thus: $r_{out} = 100 \times 10^3 + 2.5 \times 10^6 + \left[(66.6 \times 10^{-6} + 10.17 \times 10^{-6}) 2.5 \times 10^6 \right] 100 \times 10^3 = 21.7 \times 10^6 \Omega$

The approximated: $r_{out} = 66.6 \times 10^{-6} \times 2.5 \times 10^6 \times 100 \times 10^3 = 16.65 \times 10^6 \Omega$

Example-2

Calculate the minimum output voltage required to keep device in saturation in example-1. The model parameters: $\mu_n C_{ox} = 110 \mu\text{A}/\text{V}^2$, $\lambda = 0.04$ ($L=1 \mu\text{m}$) or 0.01 ($L=2 \mu\text{m}$) /V, $2|\phi_F|=0.7$, $\gamma=0.4 \text{ V}^{1/2}$

 

$$I_D = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right) (V_{GS} - V_T)^2$$


$$\Rightarrow V_{GS} - V_T = \sqrt{\frac{2I_D}{(\mu_n C_{ox}) \left(\frac{W}{L} \right)}}$$

$$\therefore V_{GS} - V_T = 0.302\text{V}$$

$$V_D(\text{min}) = V_S + (V_{GS} - V_T)(\text{min}) = 1 + 0.302 = 1.302\text{V}$$

 Example-3

Using the Cascode circuit shown below, design the W/L of M1 to achieve the same output resistance as the circuit in example-1. Ignore body effect.



This device should provide 100K impedance to maintain overall same output resistance


$$r_{o1} = 100 * 10^3 = \frac{1}{g_{m1}}$$

$$\Rightarrow \frac{1}{100 * 10^3} = g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_D} \rightarrow \left(\frac{W}{L}\right)_1 = \frac{1}{22}$$

Note that the terminal conditions of M2 must change to support the large gate voltage required for M1

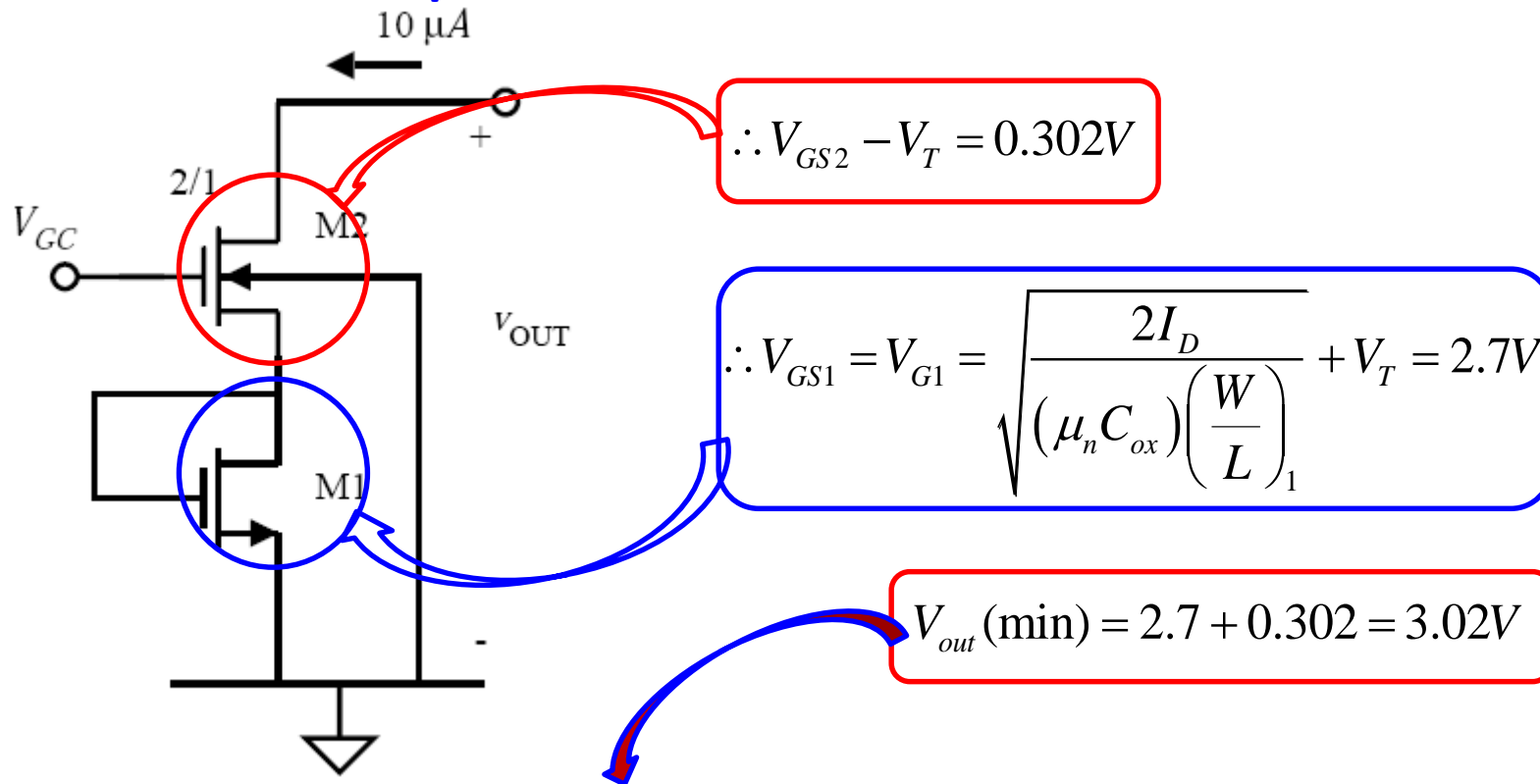Example-4


Now calculate the minimum output voltage required to keep the devices in saturation in example-3.



The minimum output voltage for circuit in example-1 is lower than the minimum output voltage for circuit in example-3, therefore is a better choice for low voltage applications

 Example-5

Calculate the output resistance, while maintaining all the devices in saturation, for the circuit given below. Assume that I_{out} is actually $10\mu A$. Ignore body effect.



Assume a near perfect current mirror (all devices have $10\mu A$ drain current)

$$r_{out} = \frac{v_{out}}{i_{out}} = r_{o1} + r_{o2} + [g_{m2}r_{o2}]r_{o1}$$

Example-5 (contd.)

$$r_{out} = \frac{v_{out}}{i_{out}} = r_{o1} + r_{o2} + [g_{m2}r_{o2}]r_{o1}$$


$$r_{o1} = r_{o2} = \frac{1}{\lambda I_D} = 2.5 * 10^6 \Omega$$

$$g_{m2} = \sqrt{2(\mu_n C_{ox}) \left(\frac{W}{L}\right)_2 I_D} = 104.9 * 10^{-6}$$

$$\therefore r_{out} = 2.5 * 10^6 + 2.5 * 10^6 + [104.9 * 10^{-6} \times 2.5 * 10^6] 2.5 * 10^6 \approx 661 * 10^6 \Omega$$

 Example-6

Consider the simple current mirror given below.



Over process, the absolute variations of physical parameters are as:

Width Variation $\pm 5\%$

Length Variation $\pm 5\%$

V_T variation $\pm 5\%$

$\mu_n C_{ox}$ Variation $\pm 5\%$

Assuming that the drain voltages are identical, what is the minimum and maximum output current measured over the process variations given above. The model parameters: $\mu_n C_{ox} = 110 \mu\text{A}/\text{V}^2$, $\lambda = 0.04$ ($L=1 \mu\text{m}$) or 0.01 ($L=2 \mu\text{m}$) /V, $2|\phi_F|=0.7$, $\gamma=0.4 \text{ V}^{1/2}$

Example-6 (contd.)

We know:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

K

$$\Rightarrow V_{GS} = \sqrt{\frac{2I_D}{K \left(\frac{W}{L}\right)}} + V_T$$

- Assuming equal V_{GS} for both the transistors, we can express the output current as:

$$i_o = \frac{1}{2} K_2 \left(\frac{W}{L}\right)_2 \left(\sqrt{\frac{2 \times I_{Ref}}{K_1 \left(\frac{W}{L}\right)_1}} + V_{T1} - V_{T2} \right)^2$$

- We can deduce from this equation that the minimum and maximum of output current will happen under respective following conditions.

	K_1	K_2	$(W/L)_1$	$(W/L)_2$	V_{T1}	V_{T2}
i_o (min)	Max	Min	Max	Min	Min	Max
i_o (max)	Min	Max	Min	Max	Max	Min