

## Problem Statements for today's lab

Q1) Design a first order BPF that operates within 20 kHz and 60 kHz. Show the design calculations and the frequency behavior in LTSpice

Q2) In the above problem statement, show the frequency behavior over a wide range of component values [i.e. by varying the components upto a certain limit] in LTSpice.

Q3) While designing a radio receiver circuit, I wanted to try something new. I wished that it would receive frequencies from 20 kHz - 60 kHz, but would eliminate the band from 35 - 45 kHz. Design such a type of circuitry for me!

N.B:- Each problem carries 10 marks.

Time :- 1:30" (9:00 A.M - 10:30 A.M)

— x — x —