

# Passive and Active Filters

---



INDRAPRASTHA INSTITUTE *of*  
INFORMATION TECHNOLOGY  
DELHI

# Passive Filters

---



- Consists of passive elements like:
  - Resistor,
  - Capacitor and
  - Inductor
- Filters can be classified as :-
  1. Low Pass Filter
  2. High Pass Filter
  3. Band Pass Filter
  4. Band Stop Filter (Band Reject/Eliminate Filter)

# Passive Low Pass Filter (LPF)




- LPF ideally allows lower frequencies and attenuates higher frequencies.
- One of the simplest form of LPF
  - Transfer Function:

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1/j\omega C}{R + 1/j\omega C}$$

$$\mathbf{H}(\omega) = \frac{1}{1 + j\omega RC}$$

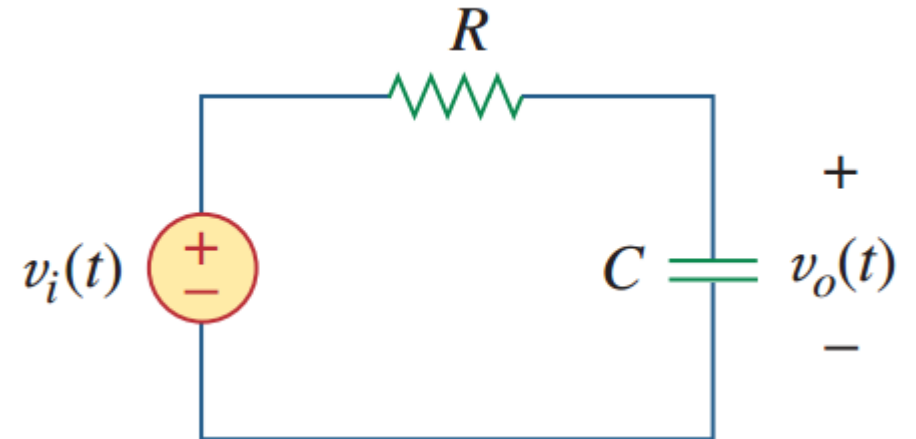- $H(0) = 1$  and  $H(\infty) = 0 \Rightarrow$  Filter is LFP




# Passive Low Pass Filter (LPF)



- $\omega_c$  is the cut-off frequency.
  - It is a frequency at which  $|H(\omega)|$  drops to 70.07% of  $|H(\omega)|_{\max}$  or becomes  $\frac{1}{\sqrt{2}}$  of  $|H(\omega)|_{\max}$ .
- So, here,  $\omega_c$  can be calculated as:

$$|H(\omega_c)| = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\omega_c = \frac{1}{RC}$$

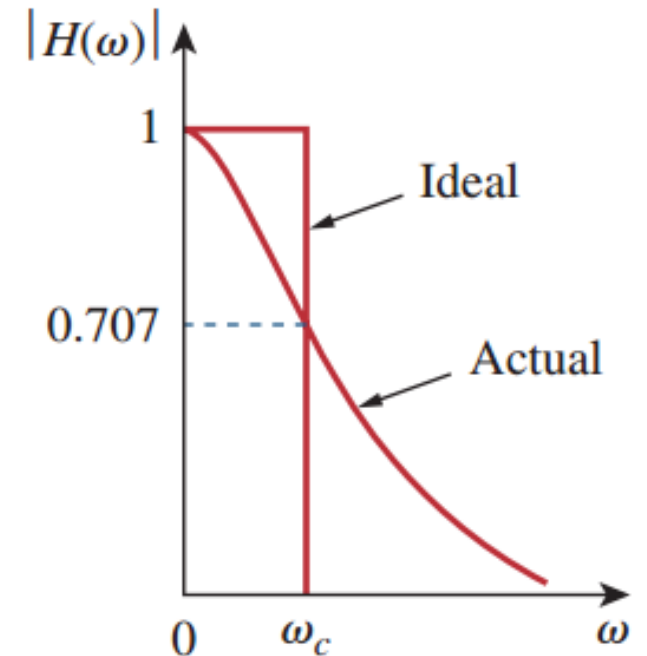

# Passive High Pass Filter (HPF)



- Ideally, HPF attenuates lower frequencies and allows higher frequencies.
- One of the simplest form of HPF



- Transfer Function:

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{R + 1/j\omega C}$$

$$\mathbf{H}(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

- $H(0) = 0$  and  $H(\infty) = 1 \Rightarrow$  Filter is HFP

$$\omega_c = \frac{1}{RC}$$

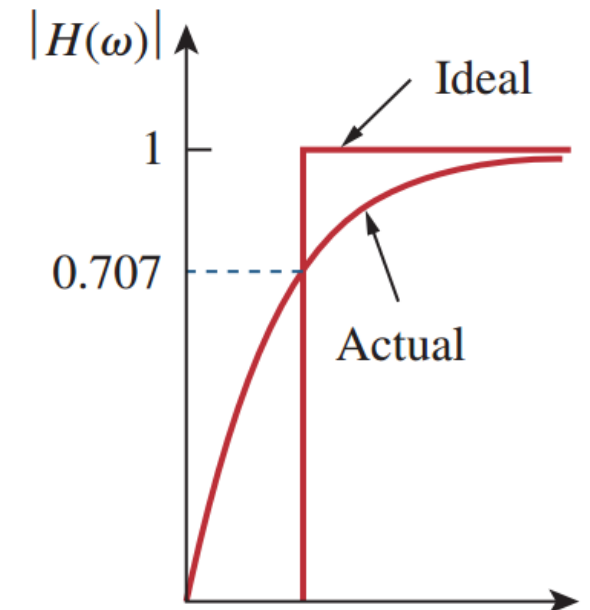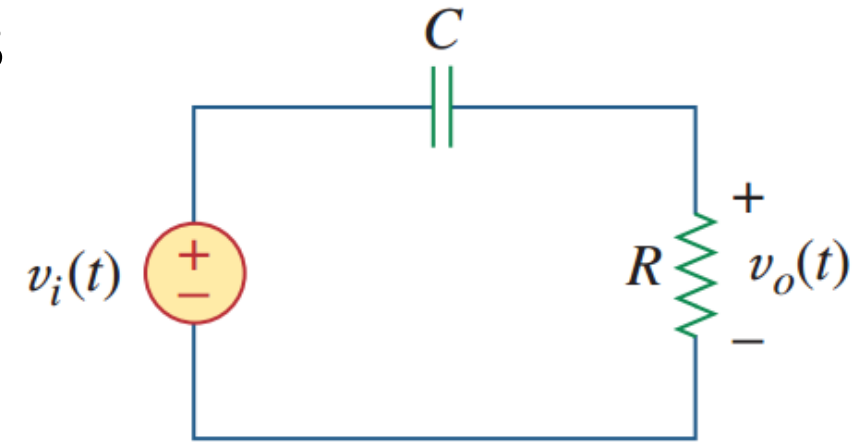

# Passive Band Pass Filter (BPF)




- BPF allows frequencies of a particular range and eliminates other frequencies.

- Typical example of BPF

- Transfer function :
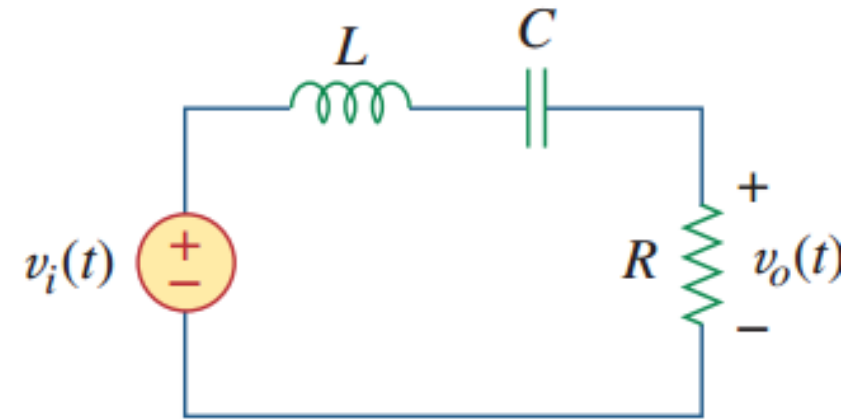
$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R}{R + j(\omega L - 1/\omega C)}$$



- Here,  $H(0) = 0$  and  $H(\infty) = 0$

- How it is BPF ?

- Resonance Frequency,  $\omega_0$  !!!!!

- $Z_{eq} = R \Rightarrow$  Filter allows  $\omega_0$  means it is a BPF

# Passive Band Pass Filter (BPF)



- Here,  $\omega_1$  and  $\omega_2$  are half power frequencies i.e. power dissipated is half of the maximum power.


$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

- Bandwidth of BPF =  $\omega_2 - \omega_1$
- Quality Factor,

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

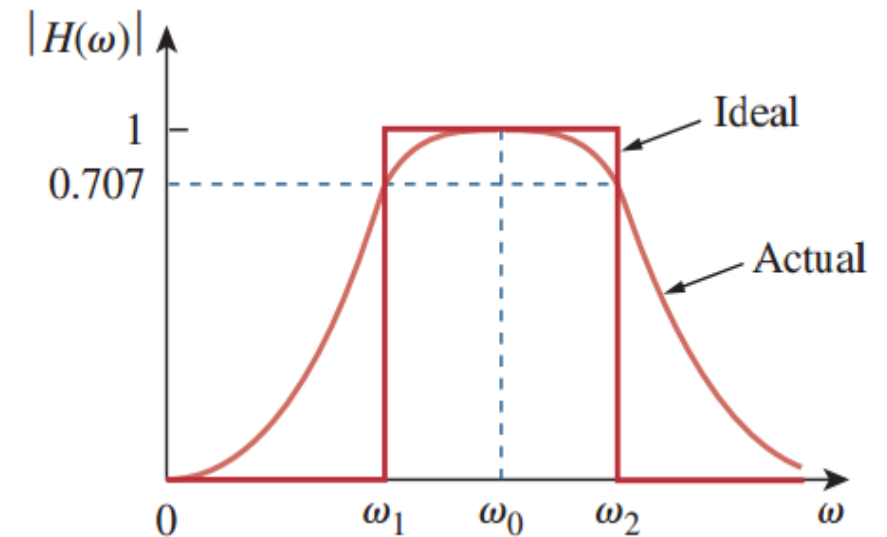Where  $\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{\omega_1 \omega_2}$



# Passive Band Stop Filter





- It rejects a particular range of frequencies and allows rest of the frequencies.
- Example of band stop filter :

- Transfer Function

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{j(\omega L - 1/\omega C)}{R + j(\omega L - 1/\omega C)}$$

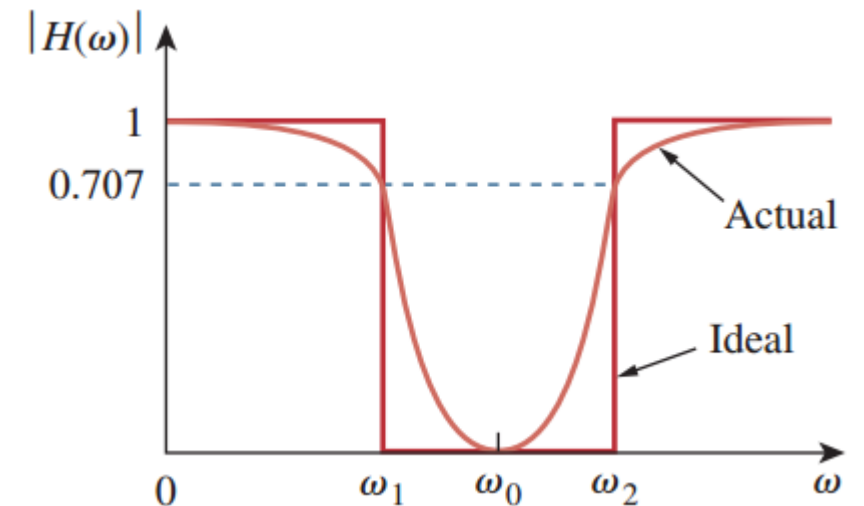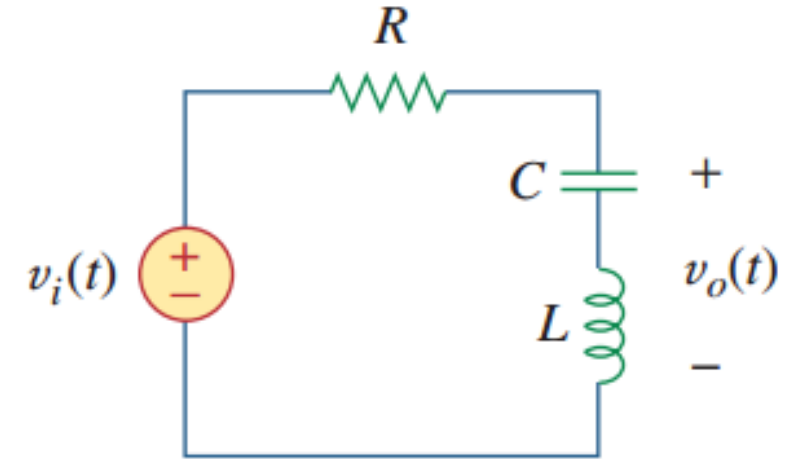- Here,  $H(0) = 1$  and  $H(\infty) = 1$ .
- But at resonance frequency,  
 $v_0 = 0 \Rightarrow$  Filters does not allow  $\omega_0$






# Practice Problem



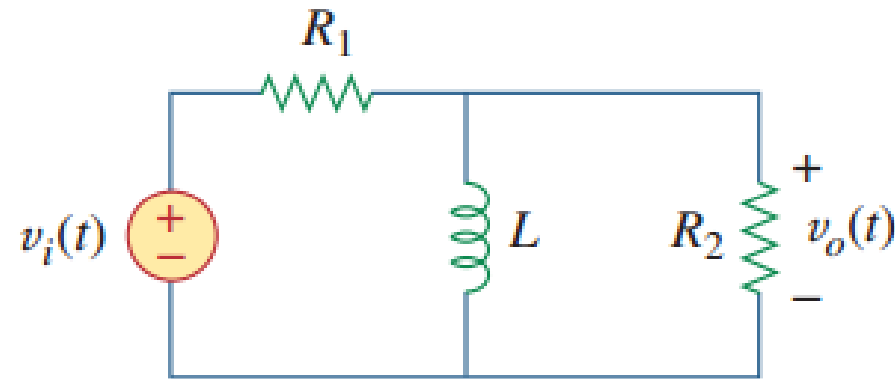1. Obtain the transfer function. Identify the type of filter the circuit represents and determine the corner frequency.  
Take  $R_1 = 100 \Omega = R_2$ ,  $L = 2 \text{ mH}$ .



# Practice Problem



2. Design a bandpass filter of the following form with a lower cutoff frequency of 20.1 kHz and an upper cutoff frequency of 20.3 kHz. Calculate  $L$ ,  $C$ , and  $Q$ . Take  $R = 20 \text{ k}\Omega$ .

