

Active filters

Basics, theory and application



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI



What are these stuffs?



- As the name suggests, active filters use ‘active’ elements as a part of their circuit
- These may consist of either opamp, BJT or any FET
- Generally, **opamps are used** in designing active filters
- Why opamps !! Guess why...



Why use an active filter



- **Less cost:** Inexpensive opamps and absence of **costly inductors** (especially at lower frequencies)
- **Gain and frequency adjustment flexibility:** Opamp **provides gain** (adjustable) -> **input signal not attenuated** as in case of passive filters
- **No loading problem:** **Excellent isolation** between stages due to **high input impedance** (opamps again) and **low output impedance**. The output can drive other circuitry without loading the source or load
- **Size:** Small in size (due to absence of **bulky 'L'**)
- **Non-floating terminals:** Active filters generally have **single ended input and output** which do not float with respect to the system power supply


Disadvantages of passive filters



- Cannot be used to **filter power** as they require power to bias themselves
- **Frequency limitation:** Opamps have **finite gain-bandwidth product (GBW)** and hence are limited in their frequency range (> 10 MHz for example)
- At high frequencies, passive filter design for rough uses is convenient because the inductor size reduces to a nice value (EHF -> **S**urface **A**coustic **W**ave filters)




The active Low Pass Filter

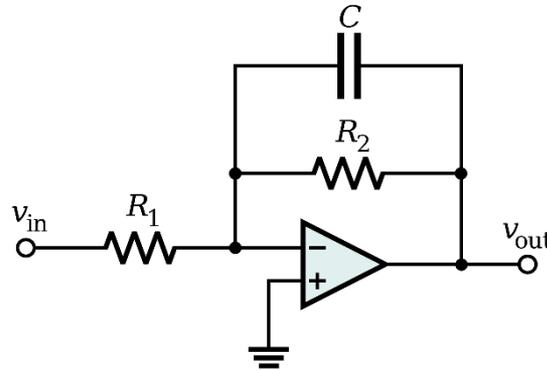


- Transfer function: $A_v = -\frac{R_2}{R_1} \left(\frac{1}{1+R_2Cs} \right)$
- We know, $s=j\omega$ (neglecting convergence factor)
- Consider two cases: at $\omega=0$ and at $\omega=\infty$
- At $\omega=0$, $A_v = -\frac{R_2}{R_1}$ and at $\omega=\infty$, $A_v = 0$
- This denotes that the circuit allows signals at low frequency to pass through and blocks signals at higher frequencies

Frequency response of the active LPF

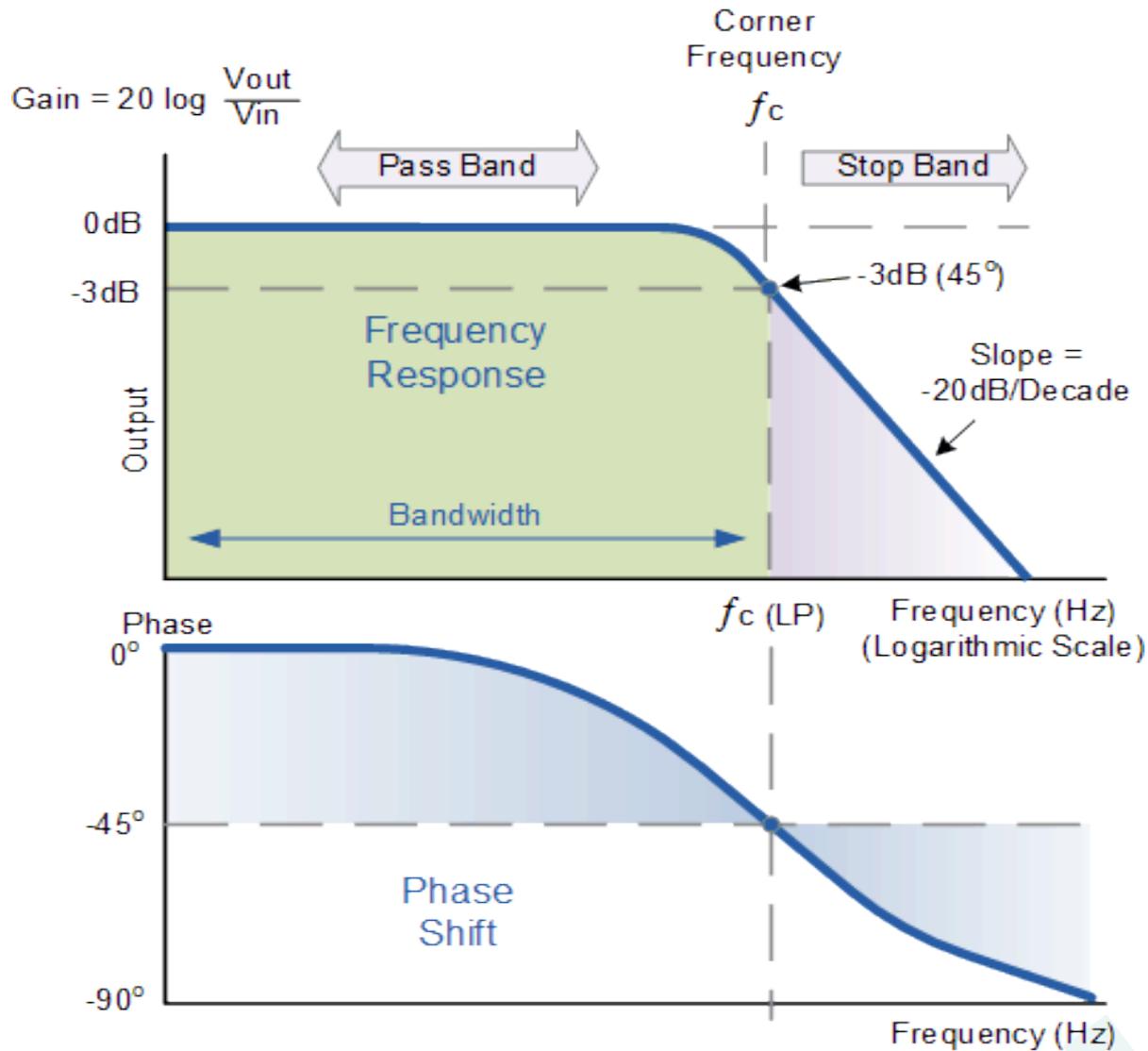

The active High Pass Filter

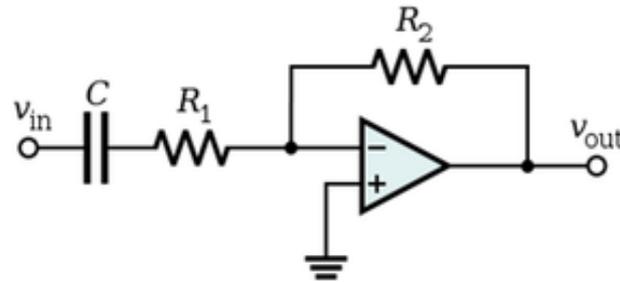


- Transfer function: $A_V = -\left(\frac{R_2}{R_1}\right) \left(\frac{Cs}{\frac{1}{R_1} + Cs}\right)$
- We know, $s=j\omega$ (neglecting convergence factor)
- Consider two cases: at $\omega=0$ and at $\omega=\infty$
- At $\omega=0$, $A_V = 0$ and at $\omega=\infty$, $A_V = -\frac{R_2}{R_1}$
- This denotes that the circuit **allows signals at high frequency to pass through** and **blocks signals at lower frequencies**


Frequency response of active HPF


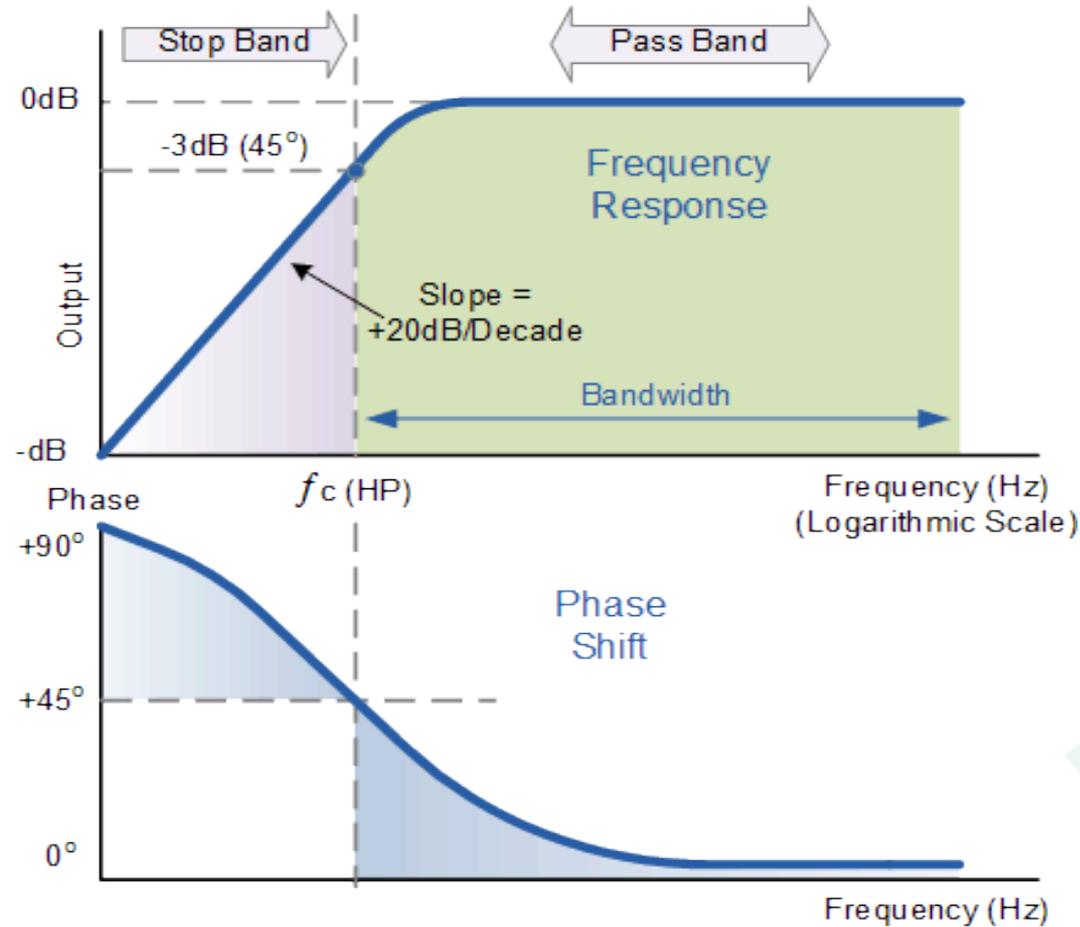
$$\text{Gain (dB)} = 20 \log \frac{V_{\text{out}}}{V_{\text{in}}}$$




The active Band Pass Filter

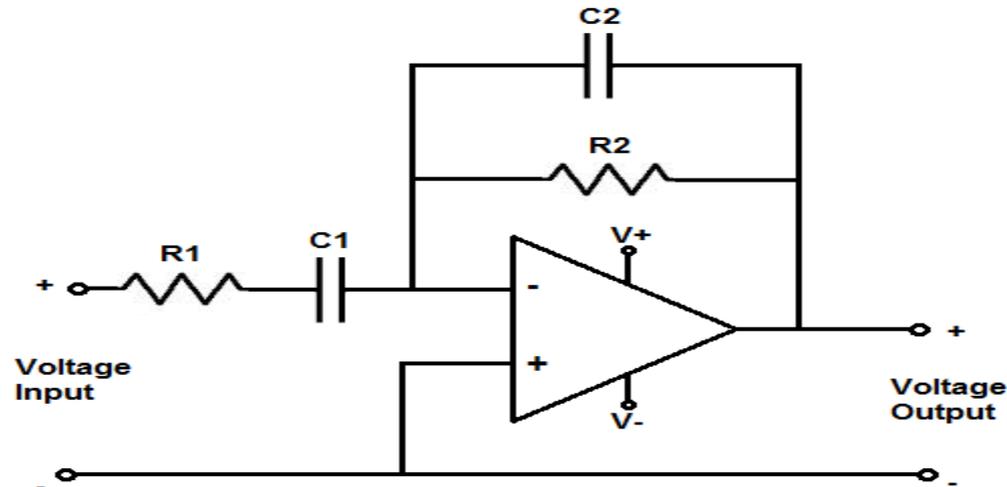

- Transfer function: $A_v = -\frac{R_2 C_1 s}{(1 + R_1 C_1 s)(1 + R_2 C_2 s)}$
- At both cases of $\omega=0$ and $\omega=\infty$, A_v turns out to be 0
- Now, if we consider an intermediate value of ω , we would see that A_v has a finite value
- This signifies that the **circuit blocks signals at both high and low frequencies, but passes the same at an intermediate frequency level**

Frequency response of active BPF

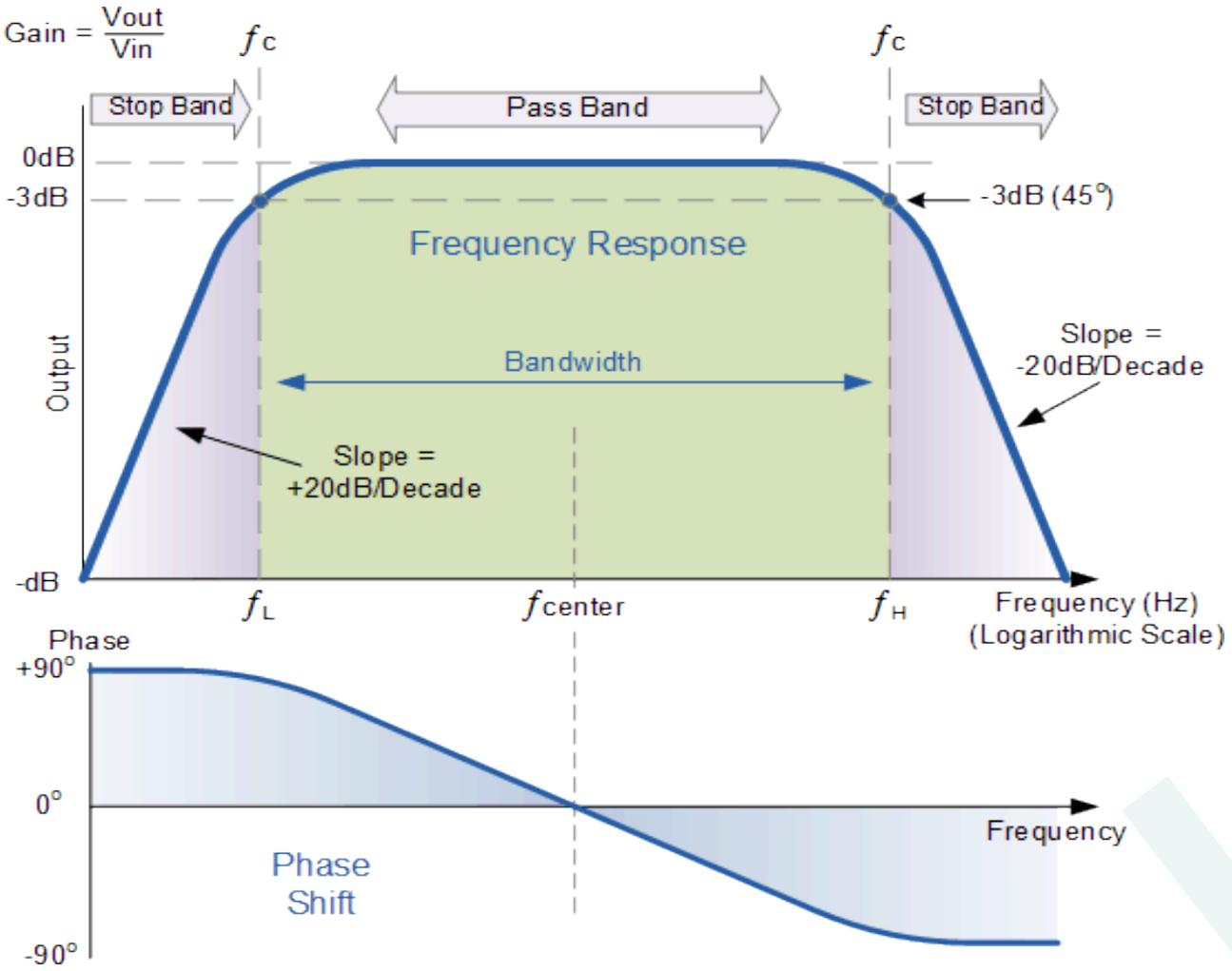

What is Bandwidth




- Bandwidth means, **the frequencies that are effectively passed by a circuit**, i.e. the circuit is operable only at those particular frequencies
- For the case of a BPF, bandwidth is **the range of frequencies that fall between the upper cutoff frequency and the lower cutoff frequency**
- Mathematically, its $(f_H - f_L)$
- The higher the Bandwidth, more frequency channels can be introduced which allows possibilities for higher rates of data transfer
- BUT, this comes with a sacrifice !! Guess what...


The Quality Factor



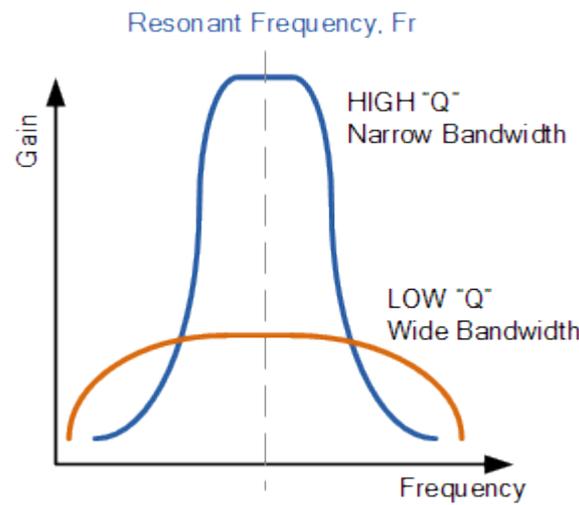- The actual width of the pass-band between the two corner frequency points determine the ‘Q’-factor of the circuit
- It measures “how selective” the circuit is towards a given spread of frequencies
- The lower the value of the Q- factor, the wider is the bandwidth of the filter (less selective); higher Q signifies narrowband circuit (highly selective)




The All Pass Filter

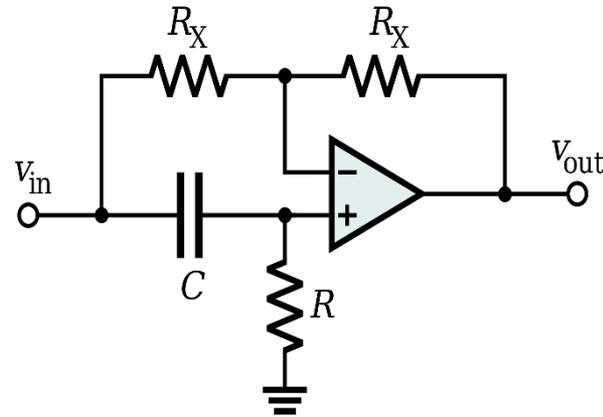

- As the name suggests, it **passes all signals**, irrespective of their frequencies
- Then what's the use of this 'seemingly useless' circuit?
- Well, it acts as a **phase shifter** which introduces a **180° phase shift** to the applied signal (phase rotator)

Frequency response of the active APF

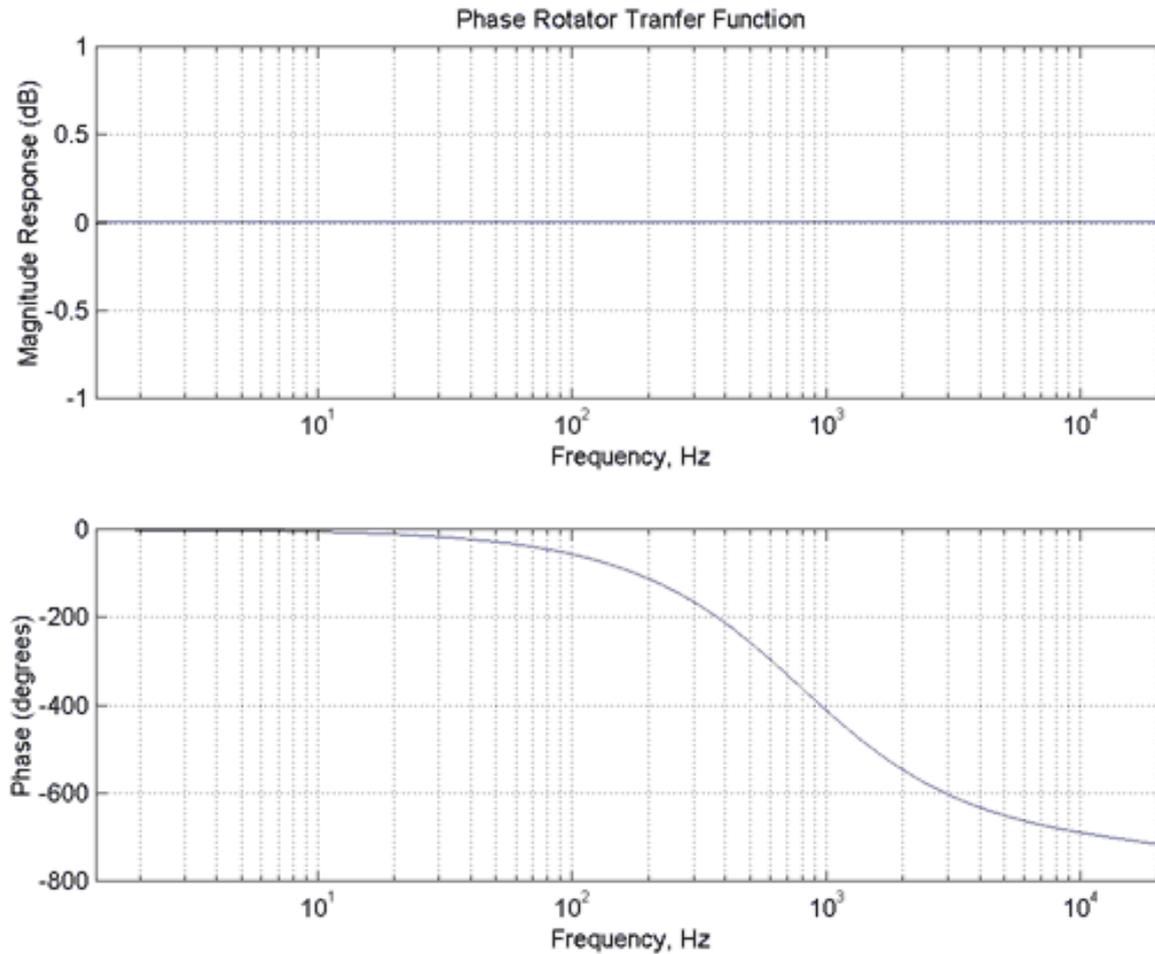

Higher order filters



- Higher order filters are necessary for a **better roll-off**
- Addition of an **extra frequency dependent element** (capacitor or inductor) **increases the order** of the circuit by one
- The roll-off rate is **$-20n$ dB/dec**, where 'n' is the order of the filter
- Rapid transition band (high roll-off) introduces disturbances or oscillations in the passband edge (Gibbs phenomenon) -> Why?



Responses of various order filters

