

## Lecture – 20

Date: 03.11.2016


- Circuit Analysis in s-domain
- State Variables
- Network Stability

## Circuit Analysis in s-domain

- Circuit analysis is relatively easy in the  $s$ -domain.
- Just need to transform a complicated set of mathematical relationships in the time domain into the  $s$ -domain where convert operators (derivatives and integrals) into simple multipliers of  $s$  and  $\frac{1}{s}$ .
- The exciting thing about it is that *all* of the circuit theorems and relationships are perfectly valid in the  $s$ -domain.

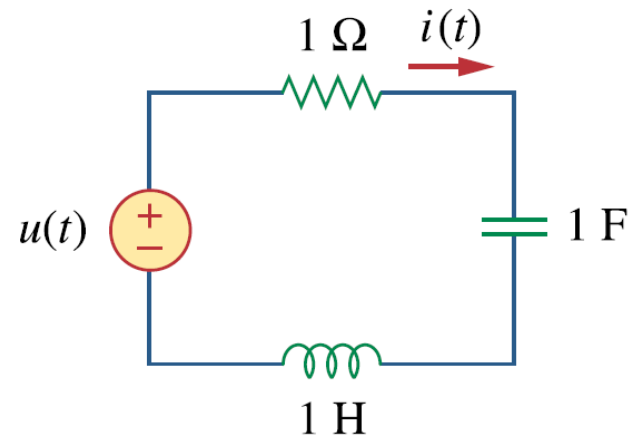
### Example – 1

Determine  $i(t)$  using Laplace Transform



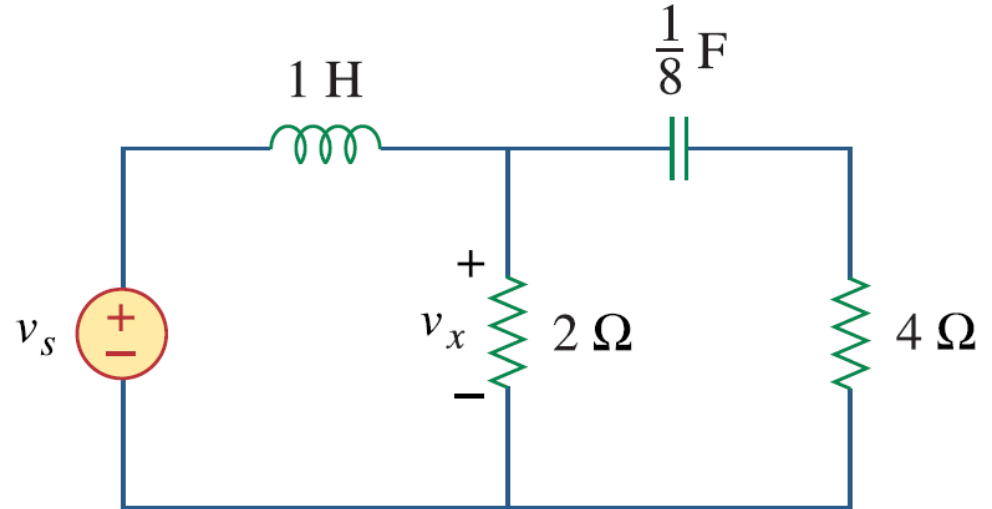
## Example – 2

Find  $v(x)$  in this circuit given  $v(s) = 4u(t)V$




## Example – 3

Find  $v_o(t)$  in this circuit.

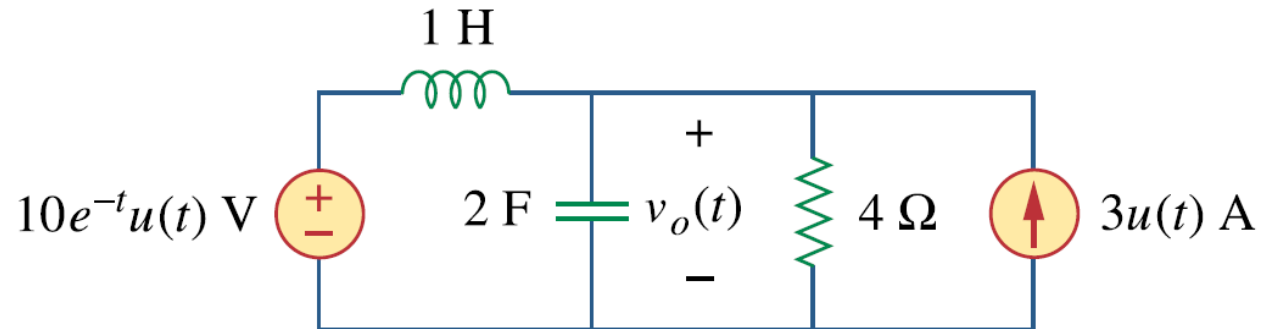
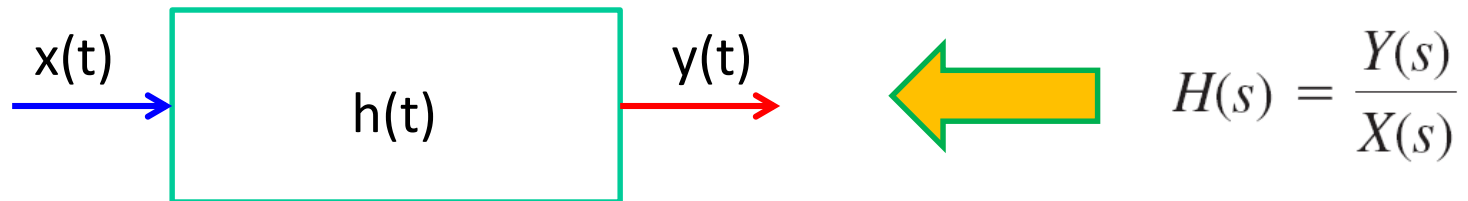
## Transfer Functions

- The transfer function  $H(s)$  is the ratio of the output response  $Y(s)$  to the input excitation  $X(s)$ , assuming all initial conditions are zero.



### Determination of Transfer Functions:

**First method:** assume any convenient input  $X(s)$  and then employ any circuit analysis technique (such as current or voltage division, nodal or mesh analysis) to find the output  $Y(s)$ , and then obtain the ratio of the two.

**Second method:** assume that the output is 1 V or 1 A as appropriate and use the basic laws of Ohm and Kirchhoff (KCL only) to obtain the input. The transfer function becomes unity divided by the input.

**Both these methods rely on the linearity property**

## Transfer Functions (contd.)


- Sometimes, the input  $X(s)$  and the transfer function  $H(s)$  is known and then:

$$Y(s) = H(s)X(s)$$

**take the inverse transform to get  $y(t)$ .**

- A special case: when the input is the unit impulse function  $x(t) = \delta(t)$  i.e.,  $X(s) = 1$

$$Y(s) = H(s)$$

  $y(t) = h(t)$

$h(t)$  represents the *unit impulse response*—it is the time-domain response of the network to a unit impulse.

Once the impulse response  $h(t)$  of a network is known, the response of the network to *any* input signal can be obtained using the above expression in the  $s$ -domain or using the convolution integral in the time domain.

## Example – 4

- The transfer function of a system is  $\frac{s^2}{3s+1}$ . Find the output when the system has an input of  $4e^{-\frac{t}{3}} u(t)$ .

## Example – 5

When the input to a system is a unit step function, the response is  $10\cos 2tu(t)$ . Obtain the transfer function of the system.

## Example – 6


A circuit is known to have its transfer function as  $H(s) = \frac{s+3}{s^2+4s+5}$

Find its output when:

- the input is a unit step function.
- the input is  $6te^{-2t} u(t)$ .
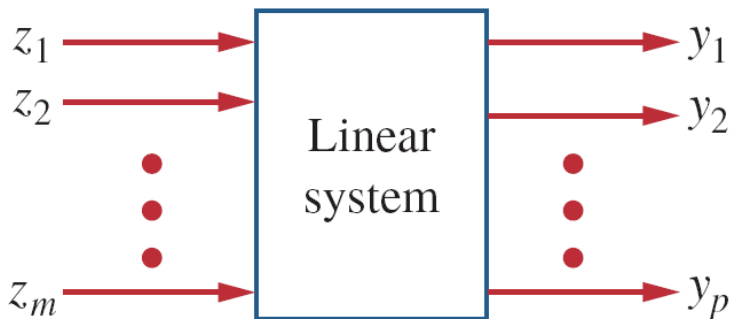
## State Variables

- Thus far we have considered techniques for analyzing systems with only one input and only one output.
- Many engineering systems have many inputs and many outputs, e.g., multiple current and voltage inputs and outputs.
- The state variable method is a very important tool in analyzing systems and understanding such highly complex systems.
- Thus, the state variable model is more general than the single-input, single-output model, such as a transfer function.



- In the state variable model, a collection of variables that describe the internal behavior of the system are specified. These variables are known as the *state variables* of the system.
- These variables determine the future of a system when the present state of the system and the input signals are known.

## State Variables (contd.)


$$\dot{\mathbf{x}} = \mathbf{A}\mathbf{x} + \mathbf{B}\mathbf{z}$$



$$\dot{\mathbf{x}}(t) =$$

$$\begin{bmatrix} x_1(t) \\ x_2(t) \\ \vdots \\ x_n(t) \end{bmatrix}$$

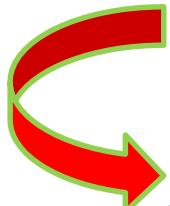state vector representing  $n$  state vectors. the dot represents the first derivative with respect to time.



$$\mathbf{z}(t) =$$

$$\begin{bmatrix} z_1(t) \\ z_2(t) \\ \vdots \\ z_m(t) \end{bmatrix}$$

input vector representing  $m$  inputs

- **A** and **B** are  $n \times n$  and  $n \times m$  respectively and matrices.

- The complete state model or state space is

$$\dot{\mathbf{x}} = \mathbf{A}\mathbf{x} + \mathbf{B}\mathbf{z}$$

$$\mathbf{y} = \mathbf{C}\mathbf{x} + \mathbf{D}\mathbf{z}$$



$$\mathbf{y}(t) =$$

$$\begin{bmatrix} y_1(t) \\ y_2(t) \\ \vdots \\ y_p(t) \end{bmatrix}$$

the output vector representing  $p$  outputs

- **C** and **D** are  $p \times n$  and  $p \times m$  respectively and matrices



## State Variables (contd.)

- Assuming zero initial conditions:

$$s\mathbf{X}(s) = \mathbf{A}\mathbf{X}(s) + \mathbf{B}\mathbf{Z}(s) \quad \longrightarrow \quad (s\mathbf{I} - \mathbf{A})\mathbf{X}(s) = \mathbf{B}\mathbf{Z}(s)$$

$$\mathbf{X}(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B}\mathbf{Z}(s)$$

- Similarly:  $\mathbf{Y}(s) = \mathbf{C}\mathbf{X}(s) + \mathbf{D}\mathbf{Z}(s)$
- Then:  $\mathbf{H}(s) = \frac{\mathbf{Y}(s)}{\mathbf{Z}(s)} = \mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + \mathbf{D}$

$\mathbf{A}$  = system matrix

$\mathbf{B}$  = input coupling matrix

$\mathbf{C}$  = output matrix


$\mathbf{D}$  = feedforward matrix

In most cases,  $\mathbf{D} = \mathbf{0}$

$$\mathbf{H}(s) = \mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B}$$
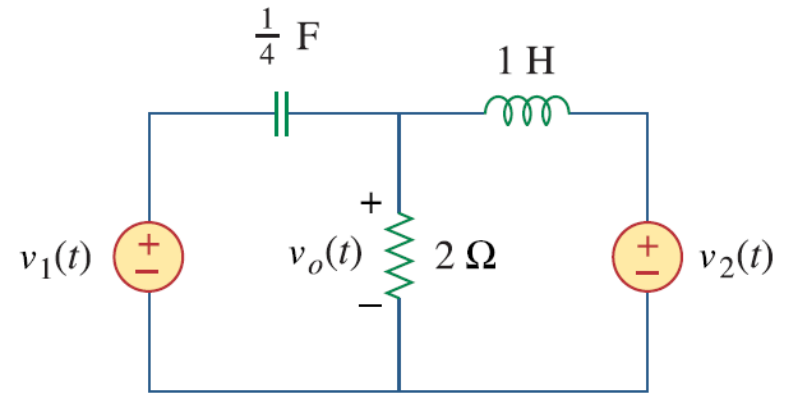
## Example – 7

Develop the state equations for this circuit.



## Example – 8

Develop the state equations for this differential equation.

$$\frac{d^2 y(t)}{dt^2} + \frac{4dy(t)}{dt} + 3y(t) = z(t)$$

## Example – 9

Given this state equation, solve for  $y_1(t)$ .


$$\dot{\mathbf{x}} = \begin{bmatrix} -2 & -1 \\ 2 & -4 \end{bmatrix} \mathbf{x} + \begin{bmatrix} 1 & 1 \\ 4 & 0 \end{bmatrix} \begin{bmatrix} u(t) \\ 2u(t) \end{bmatrix}$$

$$\mathbf{y} = \begin{bmatrix} -2 & -2 \\ 1 & -0 \end{bmatrix} \mathbf{x} + \begin{bmatrix} 2 & 0 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} u(t) \\ 2u(t) \end{bmatrix}$$
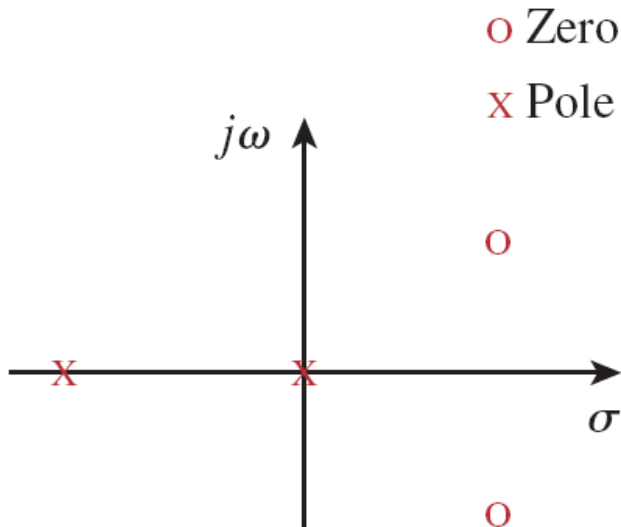
## Network Stability

- A circuit is *stable* if its impulse response  $h(t)$  is bounded (i.e.,  $h(t)$  converges to a finite value) as  $t \rightarrow \infty$ .
- Let us take:

$$H(s) = \frac{N(s)}{D(s)} \quad \rightarrow \quad H(s) = \frac{N(s)}{D(s)} = \frac{N(s)}{(s + p_1)(s + p_2) \cdots (s + p_n)}$$



$H(s)$  must meet two requirements for the circuit to be stable.

## Network Stability (contd.)

- **First**, the degree of  $N(s)$  must be less than the degree of  $D(s)$ ; otherwise, long division would produce:

$$H(s) = k_n s^n + k_{n-1} s^{n-1} + \dots + k_1 s + k_0 + \frac{R(s)}{D(s)}$$

where the degree of  $R(s)$ , the remainder of the long division, is less than the degree of  $D(s)$ .  $\rightarrow$  this will lead to unbounded  $h(t)$  as  $t \rightarrow \infty$

- **Second**, all the poles of  $H(s)$  (i.e., all the roots of  $D(s)=0$ ) must have negative real parts; in other words, all the poles must lie in the left half of the  $s$  plane.

