



## Lecture – 8

Date: 01.09.2016


- AC Circuits: Steady State Analysis

## Analysis Steps

1. Transfer the circuit to the phasor domain
2. Solve the circuit (using Mesh, Nodal techniques etc.)
3. Convert the results into time domain

## Nodal Analysis

Find  $i_x$  in the following circuit.

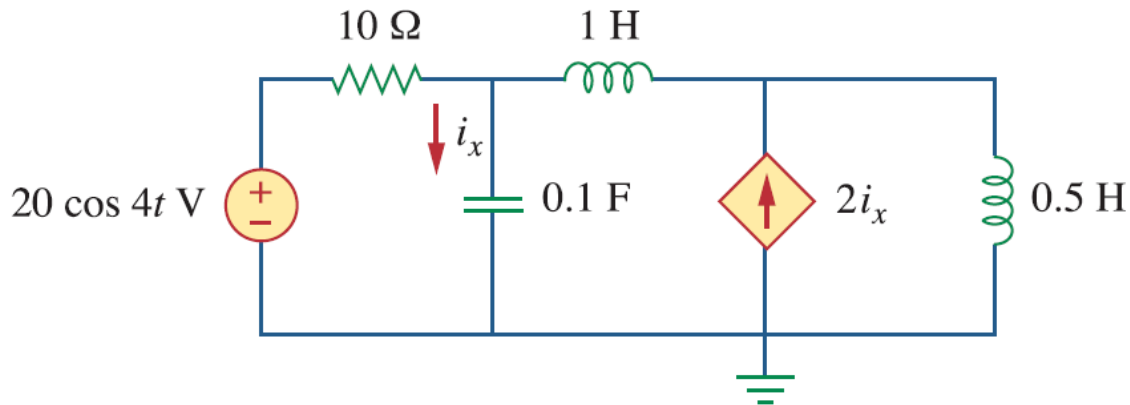

Convert the quantities to frequency domain.

## Nodal Analysis (contd.)

$$20 \cos 4t \Rightarrow 20 \angle 0^\circ, \quad \omega = 4 \text{ rad/s}$$

$$1 \text{ H} \Rightarrow j\omega L = j4$$

$$0.5 \text{ H} \Rightarrow j\omega L = j2$$

$$0.1 \text{ F} \Rightarrow \frac{1}{j\omega C} = -j2.5$$

**Freq Domain**

**KCL here**

$$\frac{20 - \mathbf{V}_1}{10} = \frac{\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4}$$

**→**

$$(1 + j1.5)\mathbf{V}_1 + j2.5\mathbf{V}_2 = 20$$


**KCL here**

$$2\mathbf{I}_x + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$

$$\frac{2\mathbf{V}_1}{-j2.5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j4} = \frac{\mathbf{V}_2}{j2}$$

**→**

$$11\mathbf{V}_1 + 15\mathbf{V}_2 = 0$$

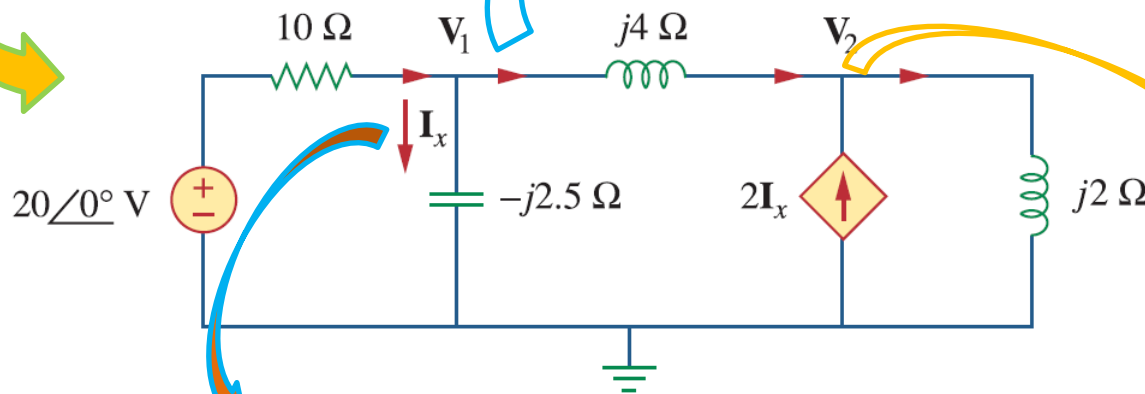

$$\mathbf{I}_x = \mathbf{V}_1 / -j2.5$$

## Nodal Analysis (contd.)

- The two nodal equations can be expressed in matrix form:

$$\begin{bmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 1 + j1.5 & j2.5 \\ 11 & 15 \end{vmatrix} = 15 - j5$$

$$\Delta_1 = \begin{vmatrix} 20 & j2.5 \\ 0 & 15 \end{vmatrix} = 300$$

$$\mathbf{V}_1 = \frac{\Delta_1}{\Delta} = \frac{300}{15 - j5} = 18.97 \angle 18.43^\circ \text{ V}$$


$$\Delta_2 = \begin{vmatrix} 1 + j1.5 & 20 \\ 11 & 0 \end{vmatrix} = -220$$

$$\mathbf{V}_2 = \frac{\Delta_2}{\Delta} = \frac{-220}{15 - j5} = 13.91 \angle 198.3^\circ \text{ V}$$

$$\mathbf{I}_x = \frac{\mathbf{V}_1}{-j2.5} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} = 7.59 \angle 108.4^\circ \text{ A}$$

$$i_x = 7.59 \cos(4t + 108.4^\circ) \text{ A}$$

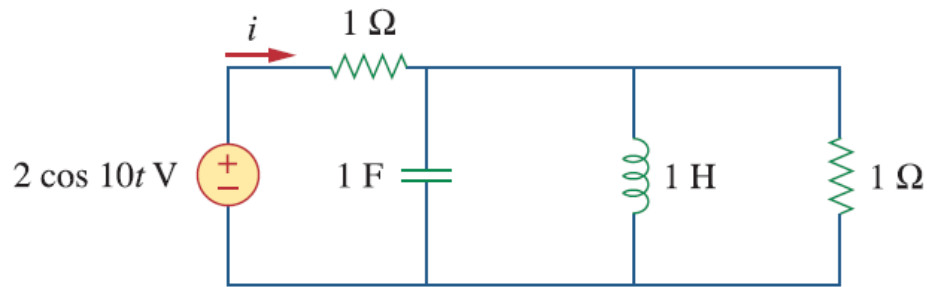
**Practice:** Find  $i$  in the following circuit.



$$i(t) = \underline{1.9704 \cos(10t + 5.653^\circ) \text{ A}}$$


## Example – 1

Determine  $v_o$  in this circuit.

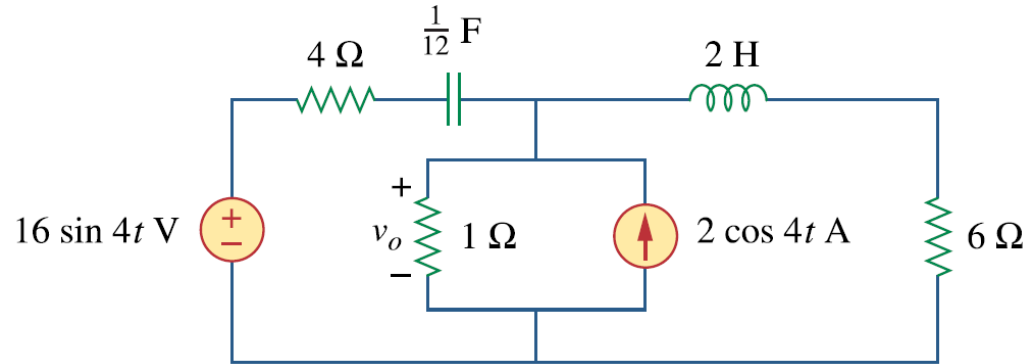


## Example – 2

Determine  $i_1$  in this circuit.

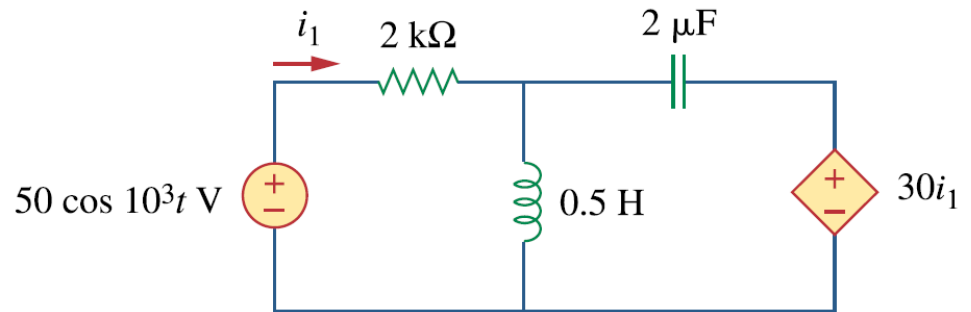

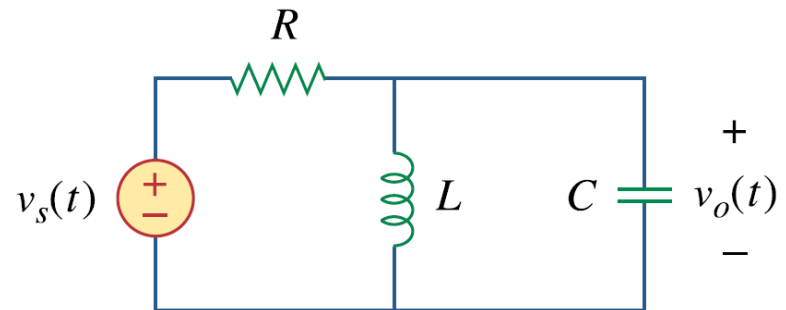
## Example – 3

In this circuit if  $v_s(t) = V_m \sin \omega t$  and  $v_o(t) = A \sin(\omega t + \varphi)$ , derive the expressions for A and  $\varphi$ .



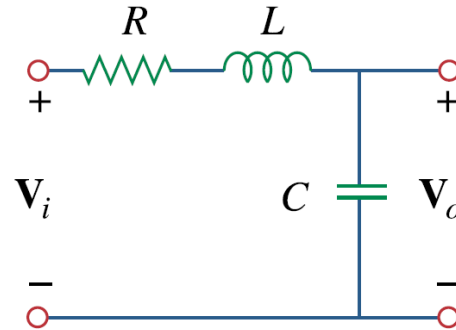
## Example – 4

Find  $V_o/V_i$  for  $\omega = 0, \omega \rightarrow \infty$   
and  $\omega^2 = 1/LC$ .



## Example – 5


Use nodal analysis to find  $V_o$ .

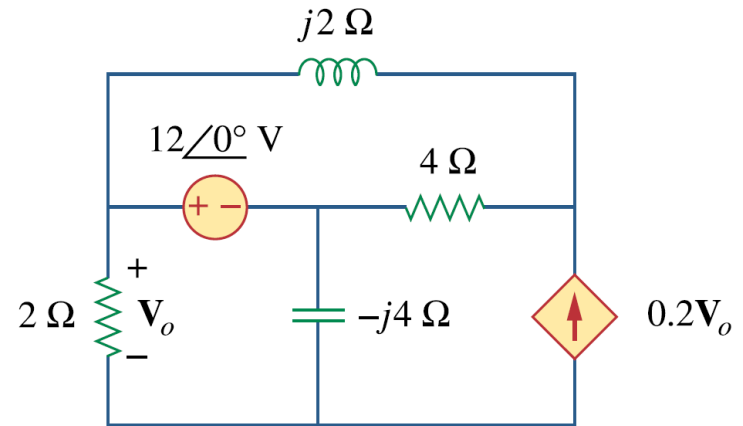

## Mesh Analysis

KVL is the basis for this.

→ Determine  $I_0$  using Mesh Analysis.

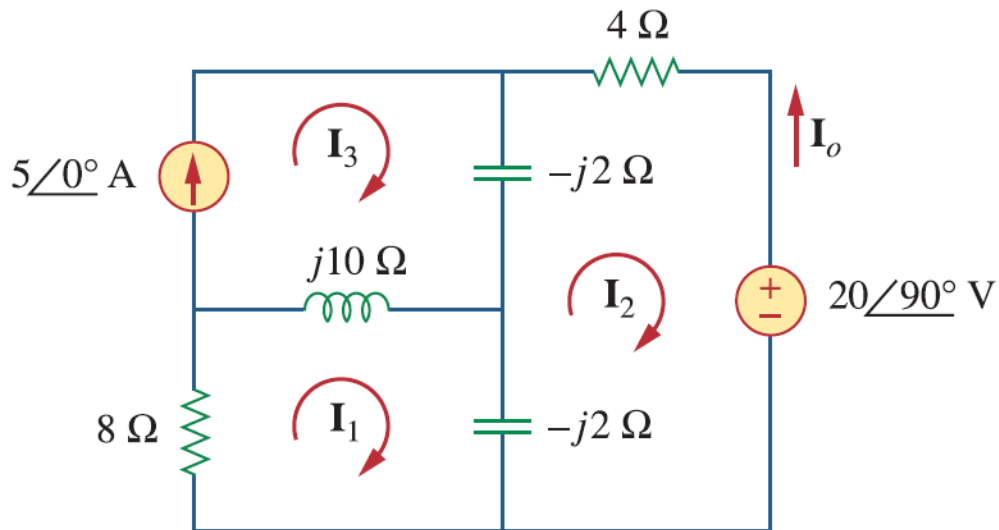

**in Loop 3:**

$$I_3 = 5$$

**KVL in Loop 1:**  $(8 + j10 - j2)I_1 - (-j2)I_2 - j10I_3 = 0$

**KVL in Loop 2:**  $(4 - j2 - j2)I_2 - (-j2)I_1 - (-j2)I_3 + 20\angle 90^\circ = 0$



## Mesh Analysis (contd.)

$$(8 + j8)\mathbf{I}_1 + j2\mathbf{I}_2 = j50$$

$$j2\mathbf{I}_1 + (4 - j4)\mathbf{I}_2 = -j20 - j10$$

$$\begin{bmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} j50 \\ -j30 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 + j8 & j2 \\ j2 & 4 - j4 \end{vmatrix} = 32(1 + j)(1 - j) + 4 = 68$$


$$\Delta_2 = \begin{vmatrix} 8 + j8 & j50 \\ j2 & -j30 \end{vmatrix} = 340 - j240 = 416.17 \angle -35.22^\circ$$

$$\mathbf{I}_2 = \frac{\Delta_2}{\Delta} = \frac{416.17 \angle -35.22^\circ}{68} = 6.12 \angle -35.22^\circ \text{ A}$$

$$\mathbf{I}_o = -\mathbf{I}_2 = 6.12 \angle 144.78^\circ \text{ A}$$


## Example – 6

- Use mesh analysis to find  $i_o$ .

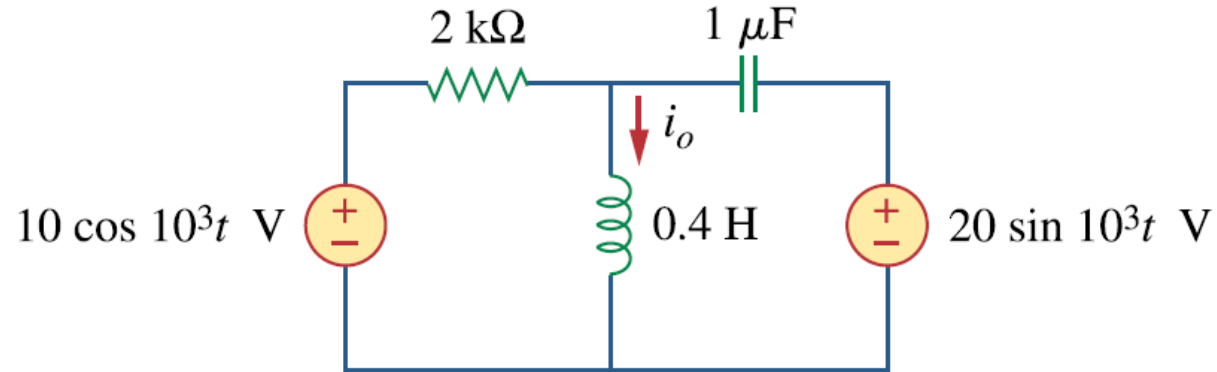

## Example – 7

- Use mesh analysis to find  $v_o$ .

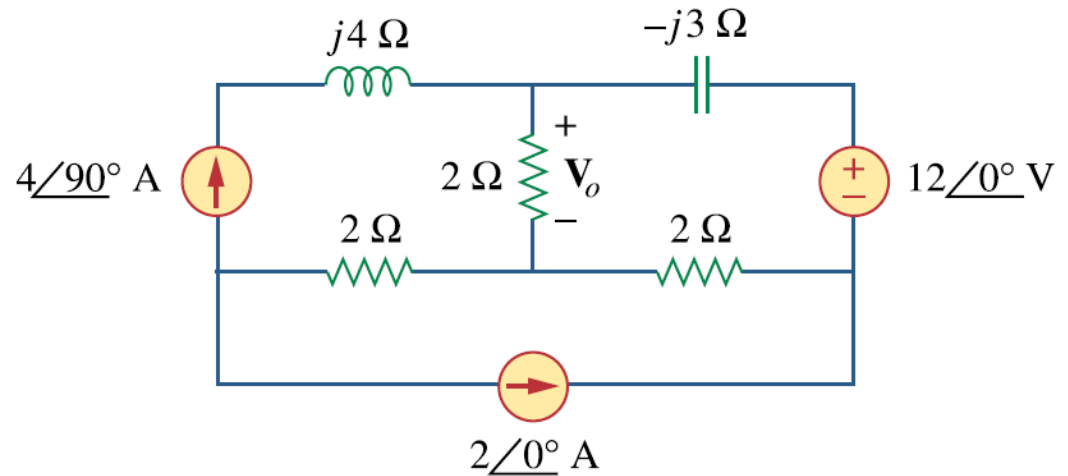


## Superposition Theorem

- These circuits are linear and hence you can apply superposition theorem.
- If sources have different frequencies then individual response must be added in the time domain.
- You can't add them in phasors as they have different  $e^{j\omega t}$ .


### Example – 8

- Use superposition to find  $i(t)$ .

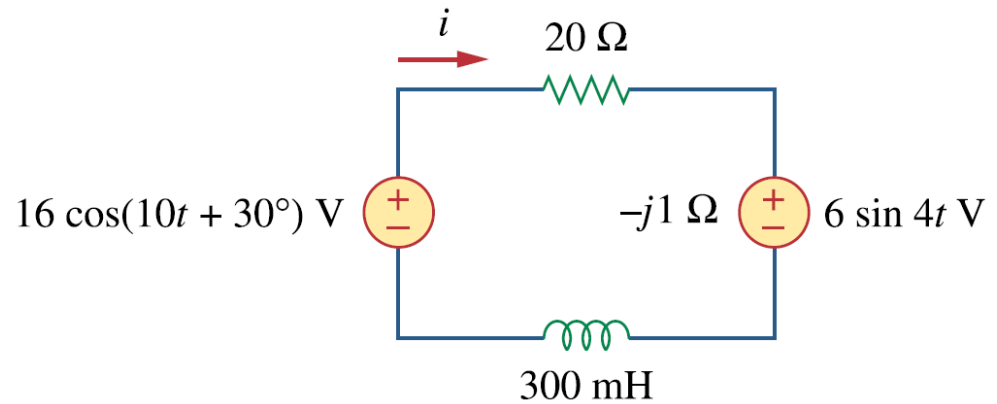

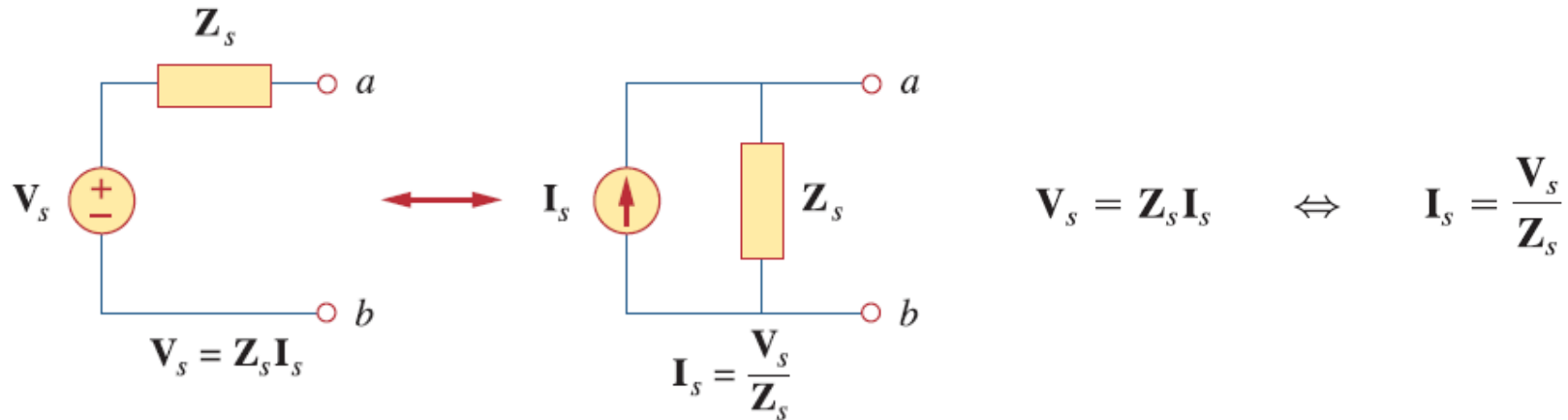
## Source Transformation

It involves transformation of **voltage source in series with an impedance** to a **current source in parallel with an impedance**, or vice versa.



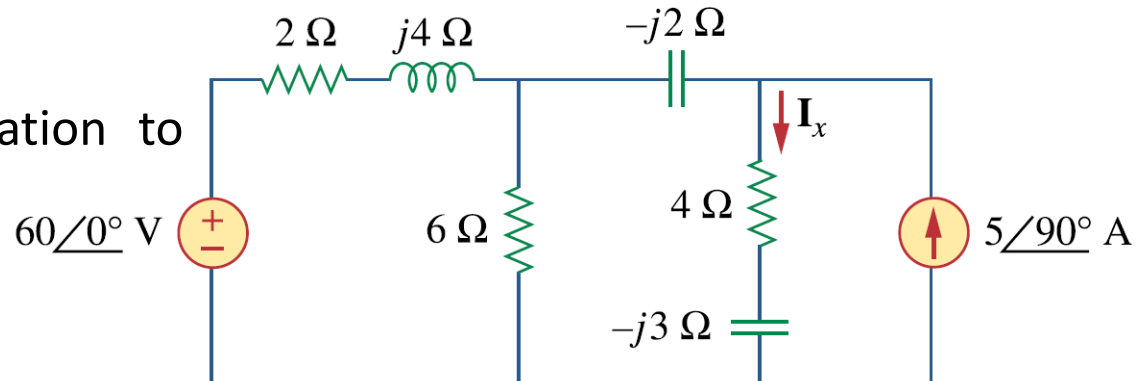
### Example – 9

- Use source transformation to find  $I_x$ .


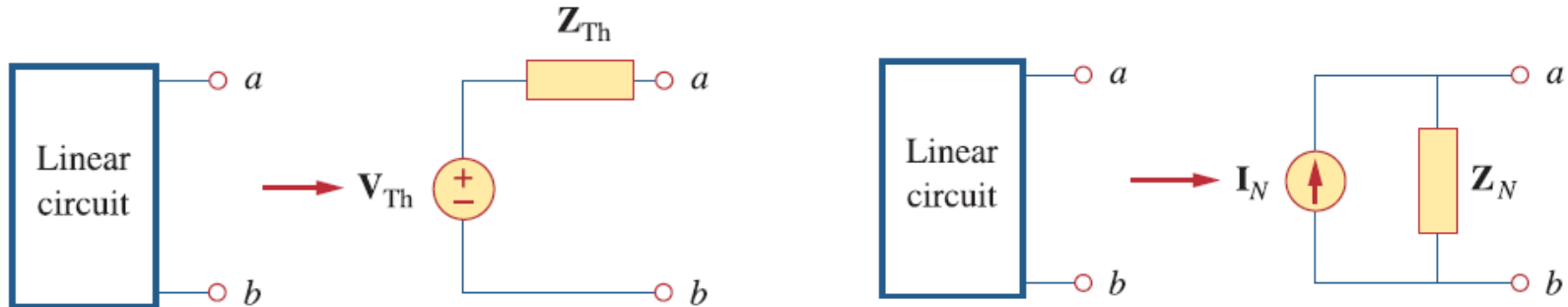
## Thevenin and Norton Equivalent Circuits


- These theorems are applied to AC circuits similar to the way it is applied to DC circuits.
- You need to work with complex numbers in AC circuits.
- For sources with different frequencies, you will have different equivalent circuit for each frequency.



$$V_{Th} = Z_N I_N, \quad Z_{Th} = Z_N$$
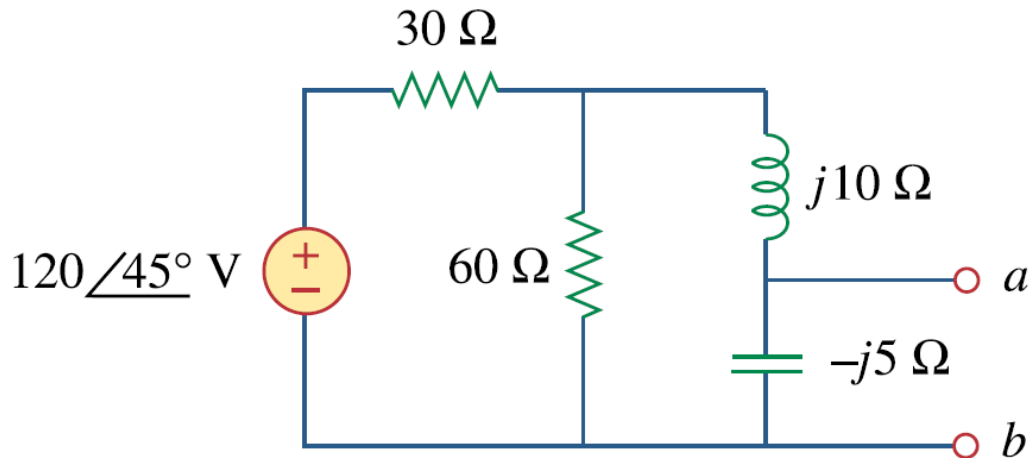
## Example – 10

- Obtain Thevenin and Norton equivalent circuits at terminal a-b.



## Example – 11

- Using Thevenin Theorem, determine  $v_o(t)$ .

